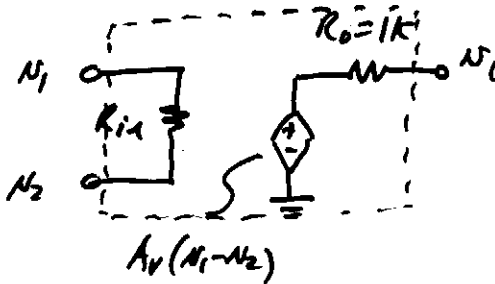



Small-Signal Model for the Voltage Amplifier (Op Amp)



$R_{in} = 25K\Omega$   
 $A_v = 10^4 V/V$   
 $R_o = 1K$



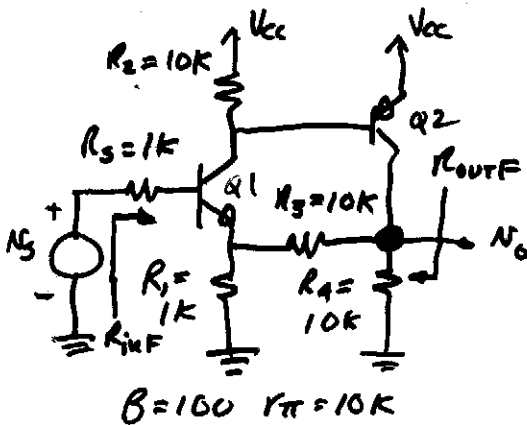
Back to Series-Shunt Transistor Feedback Example



Find  $\frac{N_O}{N_S}$ ,  $R_{inF}$ , &  $R_{outF}$  using feedback analysis methods.

$k_{vIF} = R_1 || R_3$ ,  $k_{vZF} = \frac{1}{R_1 R_3}$ ,  $k_{v2IF} = \frac{R_1}{R_1 + R_3}$   
 $\beta = \frac{1}{11}$

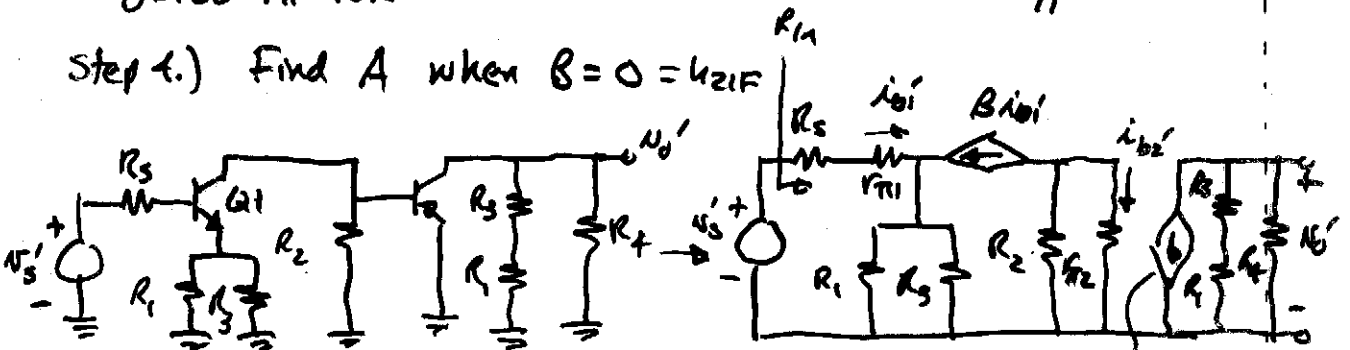Step 4.) Find A when  $\beta = 0 = k_{v2IF}$



$\frac{N'_O}{N'_S} = A = \left(\frac{N'_O}{i_{b2}'}\right) \left(\frac{i_{b2}'}{i_{b1}'}\right) \left(\frac{i_{b1}'}{N'_S}\right) \frac{1}{R_{in}}$

$= [-\beta R_4 || (R_1 + R_2)] \left[ \frac{-\beta R_2}{V_{\pi 2} + R_2} \right] \left[ \frac{1}{R_S + V_{\pi 1} + (1 + \beta) R_1 || R_3} \right]$   
 $= [-100 (5.24K)] \left[ \frac{-100 \cdot 10K}{20K} \right] \left[ \frac{1}{102.8K} \right] = 255 V/V$

5.)  $A_F = \frac{A}{1 + A\beta} = \frac{255}{1 + 255(\frac{1}{11})} = \frac{255}{1 + 23.17} = \underline{\underline{10.54 V/V}} \approx \frac{1}{\beta}$  if  $A\beta \gg 1$

$$6.) R_{in}(B=0) = h_{i1A} + h_{iNF} + R_5 = R_5 + r_{\pi 1} + (1+B)R_1 \parallel R_3 = 102.8K\Omega$$

$$R_{iNF} = R_{in}(1+AB) = 102.8K(29.17) = \underline{\underline{2.985M\Omega}}$$

$$7.) R_{out}(B=0) = \frac{1}{h_{22T} + G_L} = R_4 \parallel (R_1 + R_3) = 5.24K\Omega$$

$$R_{outF} = \frac{R_{out}}{1+AB} = \frac{5240\Omega}{29.17} = \underline{\underline{216\Omega}}$$

### General Approach for Analyzing Feedback Amplifiers

All four forms of feedback amplifiers can be analyzed in exactly the same way. Let  $x = h, g, y, z$

1.) Find  $x_{iF}$

2.) Find  $x_{oF}$

3.) Find  $x_{i2F} = B$

4.) Set  $B=0$ , find  $A$  incorporating  $x_{iF}$  and  $x_{oF}$  into the amplifier circuit.

5.)  $A_F = \frac{A}{1+AB}$

$$6.) R_{iNF} = \begin{cases} (R_S + x_{iNT})(1+AB) & \text{if series} \\ \frac{1}{(G_S + x_{iNT})(1+AB)} & \text{if shunt} \end{cases}$$

$$7.) R_{outF} = \begin{cases} \frac{1}{(G_L + x_{o2T})(1+AB)} & \text{if shunt} \\ (R_L + x_{o2T})(1+AB) & \text{if series} \end{cases}$$

Feedback Topology	Two-Port Parameters
Shunt-Shunt (Transistance Amplifier) $\frac{V_{out}}{I_{in}}$	$i_1 = y_{11} N_1 + y_{12} N_2$ $i_2 = y_{21} N_1 + y_{22} N_2$
Shunt-Series (Current Amplifier) $I_{out}/I_{in}$	$i_1 = z_{11} N_1 + z_{12} i_2$ $N_2 = z_{21} N_1 + z_{22} i_2$
Series-Series (Transconductance Amp.) $I_{out}/V_{in}$	$N_1 = g_{11} i_1 + g_{12} i_2$ $N_2 = g_{21} i_1 + g_{22} i_2$
Series-Shunt (Voltage Amplifier) $V_{out}/V_{in}$	$N_1 = h_{11} i_1 + h_{12} N_2$ $i_2 = h_{21} i_1 + h_{22} N_2$

Next is Shunt-Shunt

$$y_{11F} = \left. \frac{i_{1F}}{N_{1F}} \right|_{N_{2F}=0}$$

$$y_{22F} = \left. \frac{i_{2F}}{N_{2F}} \right|_{N_{1F}=0}$$

$$y_{12F} = \left. \frac{i_{1F}}{N_{2F}} \right|_{N_{1F}=0}$$

Example next