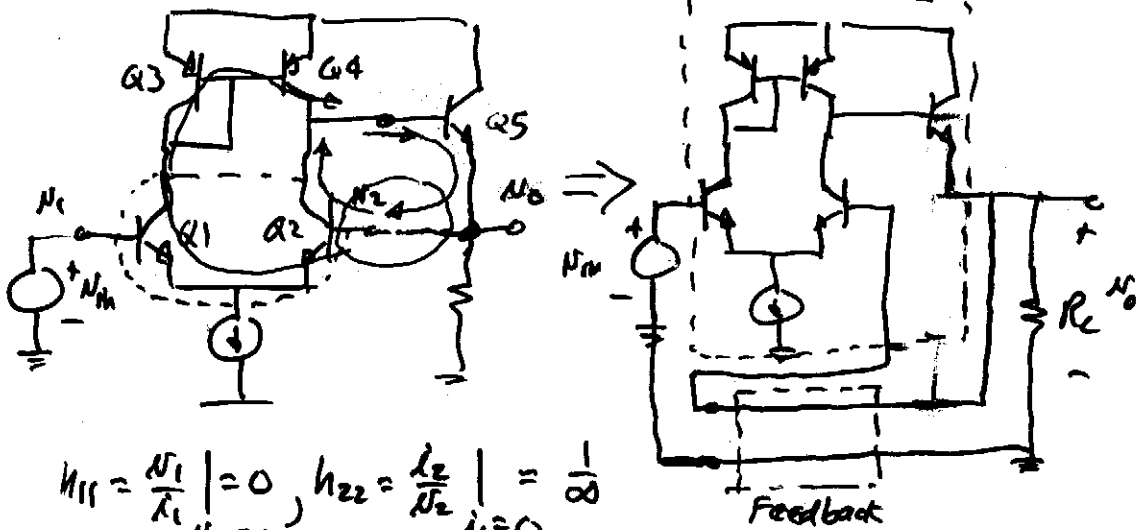



Diff. Amp. -




$$h_{11} = \frac{N_1}{i_1} \Big|_{N_2=0} = 0, \quad h_{22} = \frac{N_2}{i_2} \Big|_{i_1=0} = \frac{1}{\infty}$$

$$h_{12} = \frac{N_1}{N_2} \Big|_{i_1=0} = 1 = \beta$$


A circuit ( $\beta=0$ )

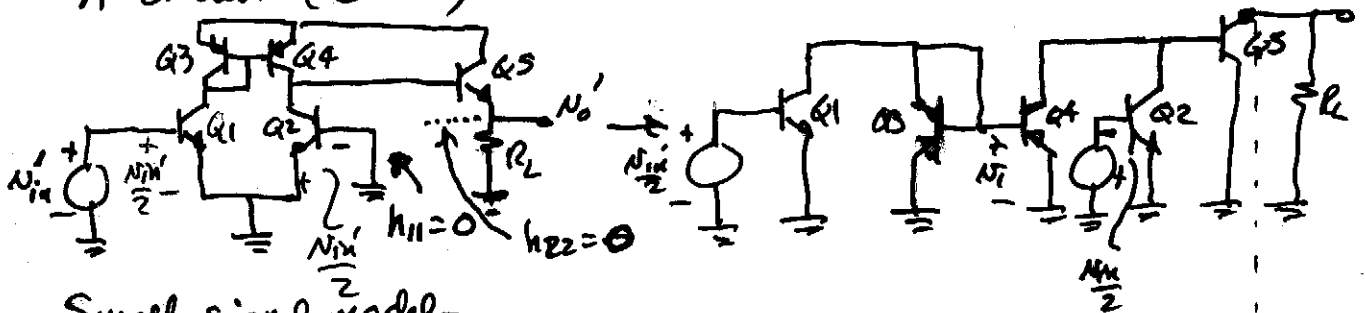

Small-signal model -

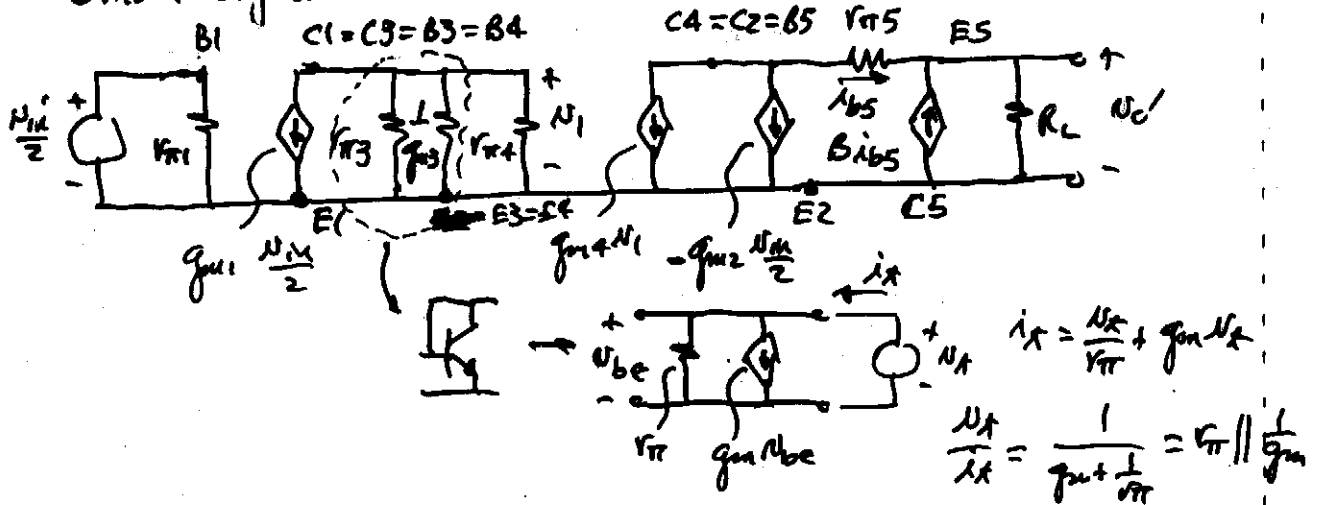

Finally,


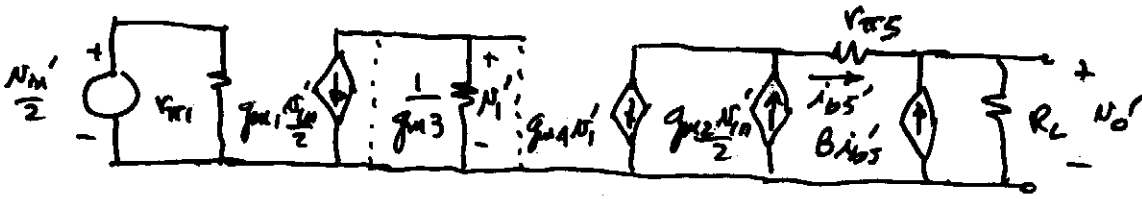


$$N_0' = i_{b5}' (1+\beta) R_L = g_{m1} N_{11}' (1+\beta) R_L$$

Shunt-Shunt

y-parameters  $\rightarrow y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0}, y_{22} = \frac{i_2}{v_2} \Big|_{v_1=0}, y_{12} = \frac{i_1}{v_2} \Big|_{v_1=0}$

Example -

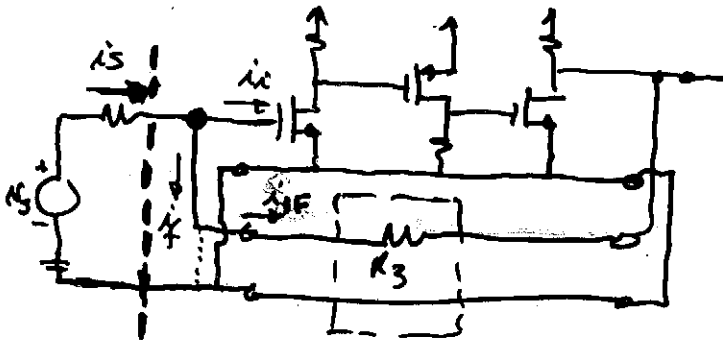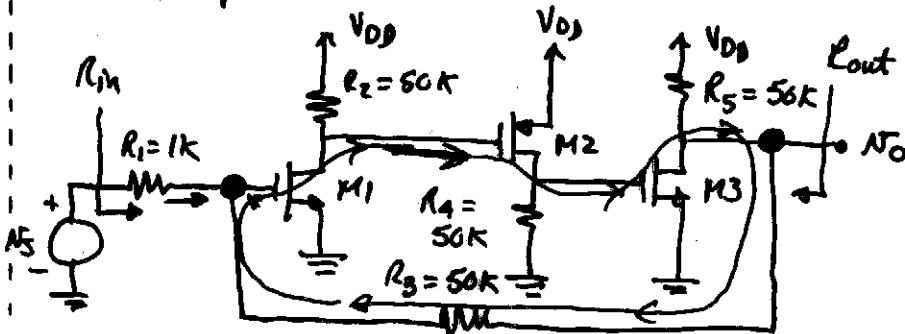

Find  $\frac{N_0}{N_5}$ ,  $R_{in}$ , and  $R_{out}$   
 if  $g_{m1} = g_{m2} = g_{m3} = 0.2 \text{ mA/V}$   
 and  $r_{ds} = \infty$

$$i_i = i_{S1} \cdot \frac{1}{2}$$

$$y_{11F} = \frac{i_{1F}}{v_{1F}} \Big|_{v_2=0} = \frac{1}{R_3} = y_{22F} \quad y_{12F} = \frac{i_{1F}}{v_{2F}} \Big|_{v_1=0} = \frac{-1}{R_3} = -\beta$$

The open-loop equivalent ckt. for A calculation -

