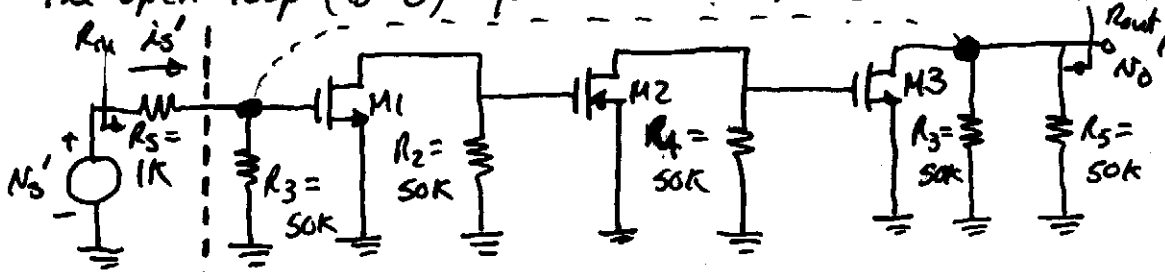


Shunt-Shunt Example - cont'd


The open-loop ( $B=0$ ) equivalent ckt. for calculation of  $A_o$ :



$$A = R_T = \frac{N_o'}{I_s'} = ?$$

Recall  $B = \left. \frac{N_o'}{I_s'} \right|_{N_i=0} = \frac{-1}{R_5} = \frac{-1}{50K\Omega}$

Small-signal model

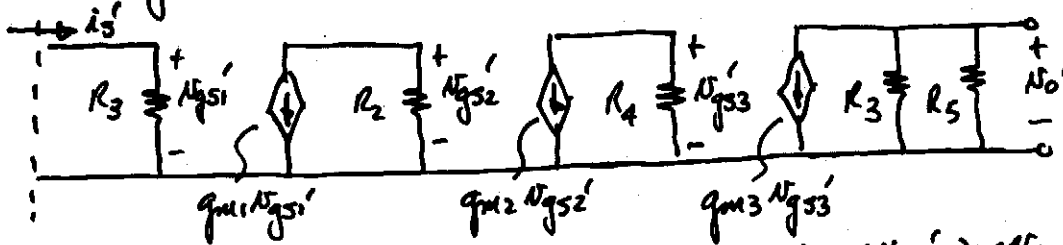

$$\frac{N_o'}{I_s'} = (-g_{m3} R_3 || R_5) (-g_{m2} R_4) (-g_{m1} R_2) (R_3) = \left( \frac{N_o'}{N_{gs3}'} \right) \left( \frac{N_{gs2}'}{N_{gs1}'} \right) \left( \frac{N_{gs1}'}{I_s'} \right)$$

$$R_T = "A" = (-0.2 \times 25) (-0.2 \times 50) (-0.2 \times 50) (50K) = -25 \times 10^6 \frac{V}{A} = -25M\Omega$$

$$5.) \left. \frac{N_o'}{I_s'} \right|_{B \neq 0} = \frac{A}{1+AB} = \frac{R_T}{1+BR_T} = \frac{-25 \times 10^6}{1 + \left(\frac{-1}{50K}\right)(-25M)} = \frac{-25 \times 10^6}{1+500} = -49.9K\Omega$$

$\left( \frac{N_o'}{I_s'} \rightarrow \frac{1}{B} \text{ if } AB \gg 1 \right)$


$$6.) R_{inF} = \frac{R_{in}}{1+AB} = \frac{R_3}{1+500} = \frac{50K}{501} = 99.8\Omega$$

$$\frac{N_s'}{I_s'} = R_5 + R_{inF} = 1K + 99.8\Omega = \underline{1099.8\Omega}$$


$$\frac{N_o'}{N_s'} = \frac{N_o'}{I_s'} \times \frac{I_s'}{N_s'} = (-49.9K\Omega) \left( \frac{1}{1099.8\Omega} \right) = \underline{-45.4 V/V}$$

$$7.) R_{out} = R_{outF} = \frac{R_{out}(B=0)}{1+AB} = \frac{25K}{501} = \underline{49.9\Omega}$$

Pitfalls of shunt input -

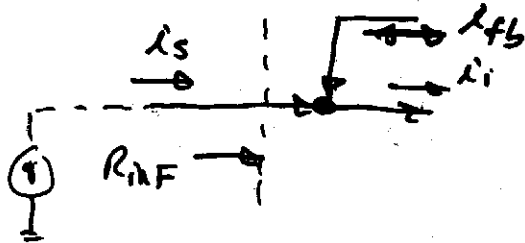

For the previous example -

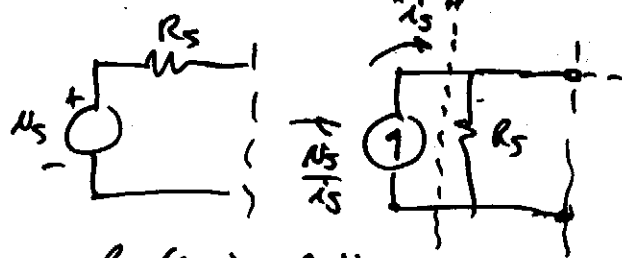

$$R_{in}(\beta=0) = R_s \parallel r_{in}$$

$$R_{in}(\beta \neq 0) = \frac{R_{in}(\beta=0)}{1 + AB} = \frac{R_s \parallel r_{in}}{1 + AB}$$

$$R_{in}(\beta \neq 0) = \frac{1k \parallel r_{in}}{501} \ll 1k$$

3rd Type of Feedback


Current Amplifier - Shunt-Series Feedback

g-parameters

$$1.) g_{11F} = \left. \frac{i_{1F}}{V_{1F}} \right|_{i_{2F}=0}$$

$$3.) g_{12F} = \left. \frac{V_{1F}}{i_{2F}} \right|_{V_{1F}=0} = \beta$$

$$2.) g_{22F} = \left. \frac{V_{2F}}{i_{2F}} \right|_{V_{1F}=0}$$

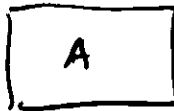

\$R\_{in}\$ with output shorted if output is shunt and open if output is series



\$R\_{out}(\beta) = \$

1.) If input is shunt, short input


2.) If input is series, open the input

$$4.) A = \frac{i_{out}}{i_{in}} = \frac{i_2}{i_1}$$

$$5.) R_{in}(\beta \neq 0) = \frac{R_{in}(\beta=0)}{1 + AB}$$

$$6.) R_{out}(\beta \neq 0) = R_{out}(\beta=0) (1 + AB) \leftarrow \text{BE CAREFUL}$$

Shunt-Series Example

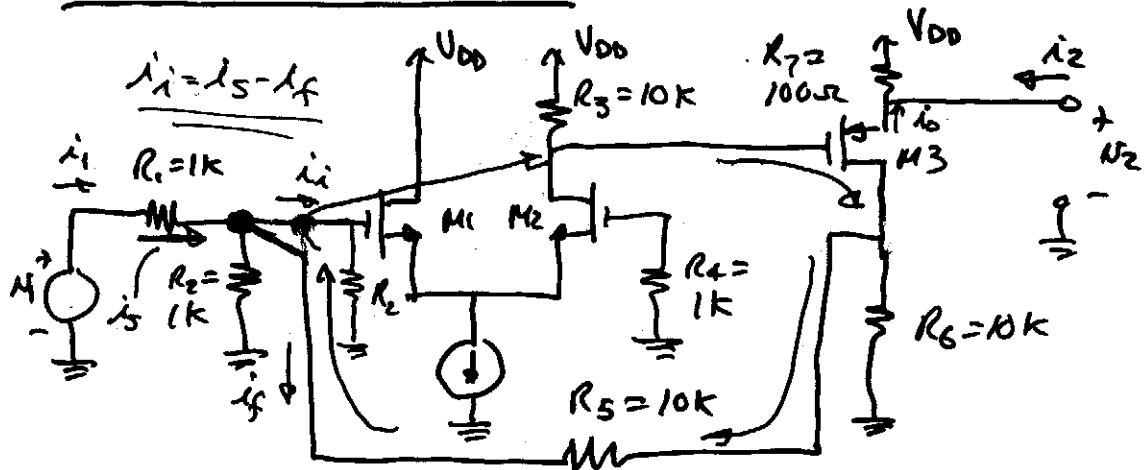

If  $g_m = 1mS$  for all MOSFETs and  $r_{ds} = \infty$ , find  $\frac{N_2}{N_1}$ ,  $\frac{N_1}{i_1}$ , and  $\frac{N_2}{i_2}$  using feedback analysis methods.