
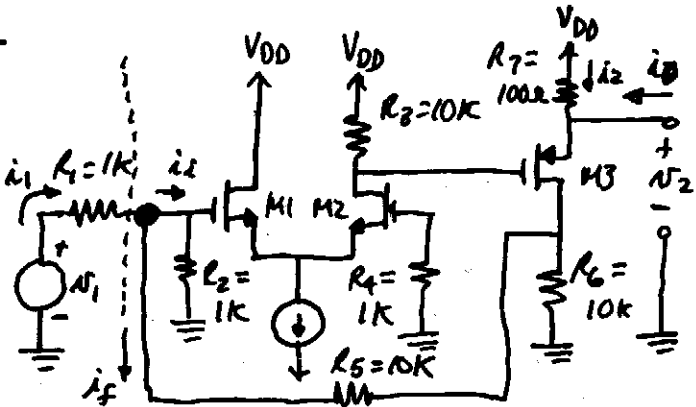


Shunt-Series Example

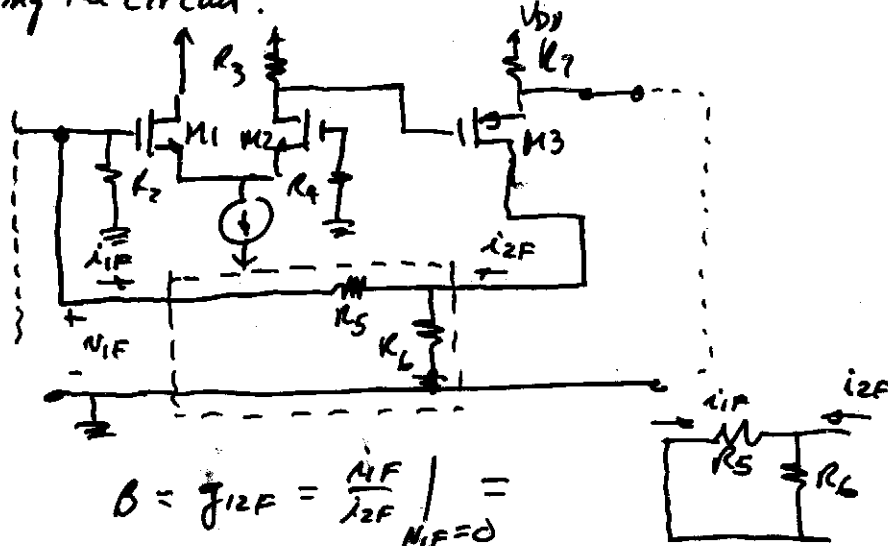If $g_m = 1\text{ms}$ and $r_{ds} = \infty$ for all MOSFETs, find $\frac{v_2}{v_1}$, $\frac{i_2}{i_1}$, and $\frac{v_2}{i_2}$ using the methods of feedback analysis.




Simplifying the circuit:




$$\beta = \frac{i_{2F}}{i_{1F}} \Big|_{v_{1F}=0} =$$

$$\therefore \beta = -\frac{R_6}{R_5 + R_6} = \frac{-10k}{20k} = -\frac{1}{2}$$

Open-loop circuit ($\beta = 0$)

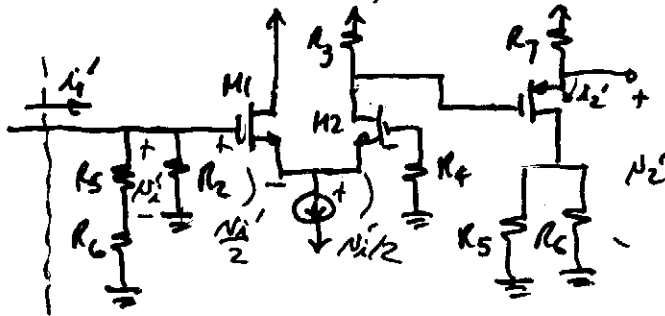

Small-signal Model of ($\beta=0$):

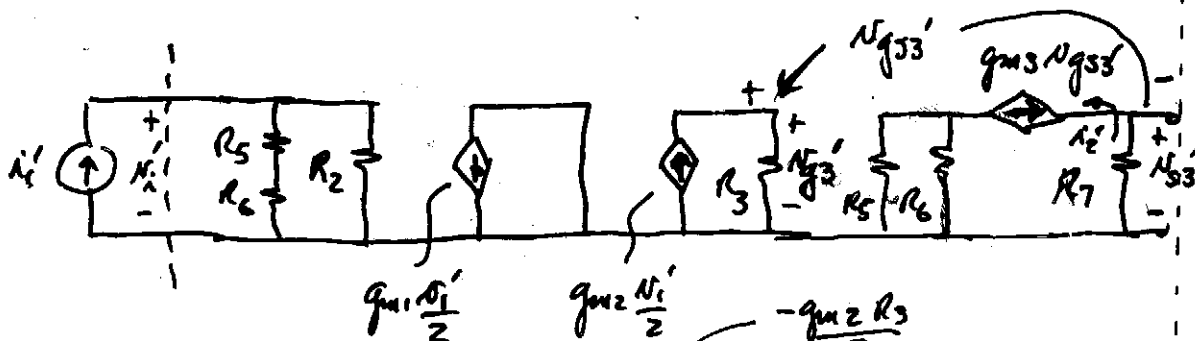

$$A = \frac{i_2'}{i_1'} = A_i = \left(\frac{i_2'}{N_{g53}'} \right) \left(\frac{N_{g53}'}{N_{g3}'} \right) \left(\frac{N_{g3}'}{i_1'} \right) \left(\frac{v_i'}{i_i'} \right) R_{2||}(R_5+R_6)$$

$$N_{g53}' = N_{g3}' - N_{53}' = N_{g3}' - g_{m3} R_7 N_{g53}'$$

$$N_{g53}' (1 + g_{m3} R_7) = N_{g3}' \rightarrow \frac{N_{g53}'}{N_{g3}'} = \frac{1}{1 + g_{m3} R_7}$$

$$\therefore A_i = \frac{i_2'}{i_1'} = (-g_{m3}) \left(\frac{1}{1 + g_{m3} R_7} \right) \left(+ \frac{g_{m2} R_5}{2} \right) (R_{2||}(R_5+R_6))$$

$$= (-1 \text{ mS}) \left(\frac{1}{1 + 0.1} \right) \left(\frac{10}{2} \right) (1 \text{ k} || 20 \text{ k}) = -4.33 \text{ A/A}$$

$$\frac{i_2'}{i_1'} = \frac{A_i}{1 + A_i B} = \frac{-4.33}{1 + (-\frac{1}{2})(-4.33)} = \frac{-4.33}{3.164} = -1.365 \text{ A/A}$$


$$R_{inF} = \frac{R_{in}}{1 + A_i B} = \frac{R_{2||}(R_5+R_6)}{3.164} = \frac{952 \Omega}{3.164} = 301 \Omega$$

$$\therefore \frac{N_1}{i_1} = R_1 + R_{inF} = 1000 + 301 = \underline{\underline{1301 \Omega}} = R^*$$


$$\frac{v_2'}{N_1} = \frac{-i_2' R_7}{i_1 R^*} = \left(\frac{i_2'}{i_1} \right) \left(\frac{-R_7}{R^*} \right) = (-1.365) \left(\frac{100 \Omega}{1301 \Omega} \right) = \underline{\underline{0.105 \text{ V/V}}}$$

$$R_{outF} = R_{out} (1 + A_i B)$$

What is R_{out} or R_{outF} ?

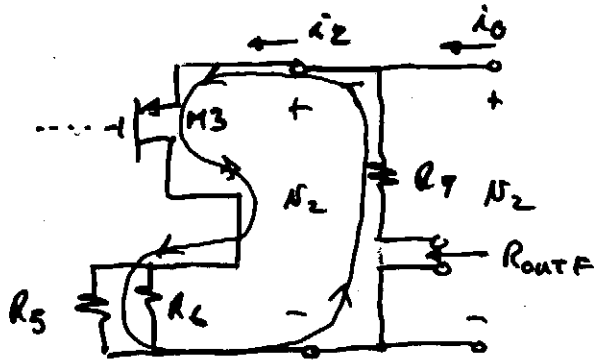

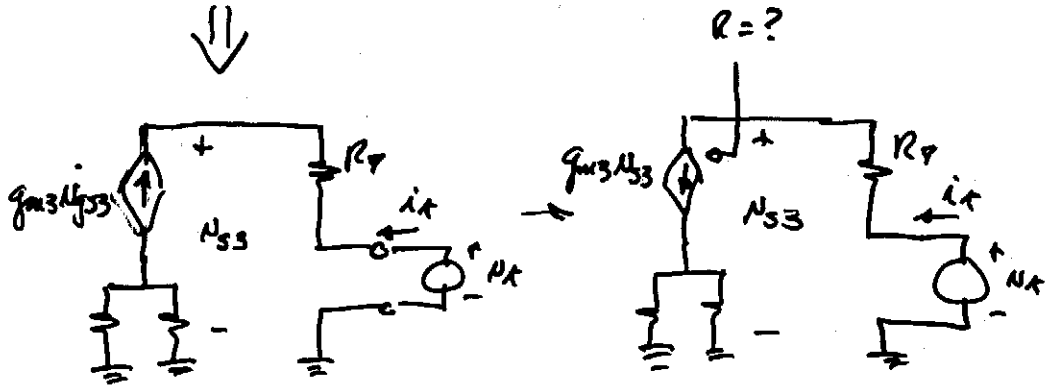R_{out} or R_{outF} is the resistance seen in series with the output loop



$$v_x = i_x R_D + v_{gs3} \quad i_x = g_{m3} v_{gs3}$$

$$v_x = i_x R_D + \frac{1}{g_{m3}} i_x \Rightarrow \frac{v_x}{i_x} = 100 + 1000 = 1.1k$$

$$R_{out} = R_D + \frac{1}{g_{m3}} \quad R_{outF} = R_{out} (1 + A_i B)$$

$$R_{outF} = 1.1k (3.164) = 3.48k\Omega$$

