
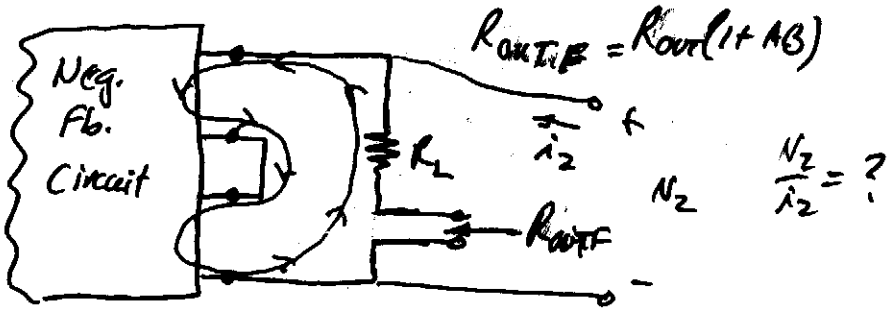


Series output - Output resistance

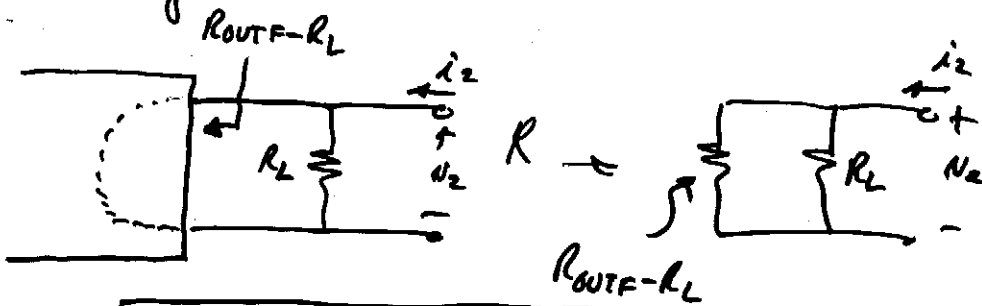

Redrawing -



$$\frac{N_2}{i_2} = R_L \parallel (R_{OUT} - R_L)$$


Series-Series Feedback (Transconductance Amplifiers)

z-parameters -

$$\frac{I_{out}}{V_{in}} \quad A = G_T$$


$$Z_{12F} = \frac{N_{1F}}{i_{2F}} \Big|_{i_{1F}=0} = B$$

Example -

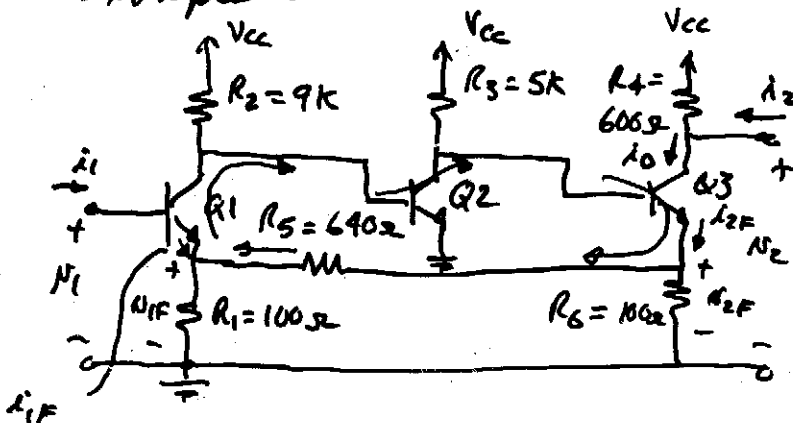

If $h_{fe} = B = 100$
 and $I_{c1} = 0.6 \text{ mA}$,
 $I_{c2} = 1 \text{ mA}$, and
 $I_{c3} = 4 \text{ mA}$, find
 $\frac{N_2}{N_1}$, $\frac{N_1}{i_1}$, and $\frac{N_2}{i_2}$
 using methods of
 neg. fb. analysis.



$\beta = ?$

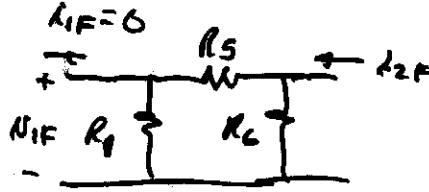

$$\beta = \left. \frac{N_{IF}}{i_{2F}} \right|_{N_{IF}=0} = \frac{R_2}{R_1 + R_2 + R_5} R_1 = 11.9 \Omega$$

Probably $\frac{i_o}{i_i} \approx \frac{1}{11.9 \Omega}$

$\beta = 0$

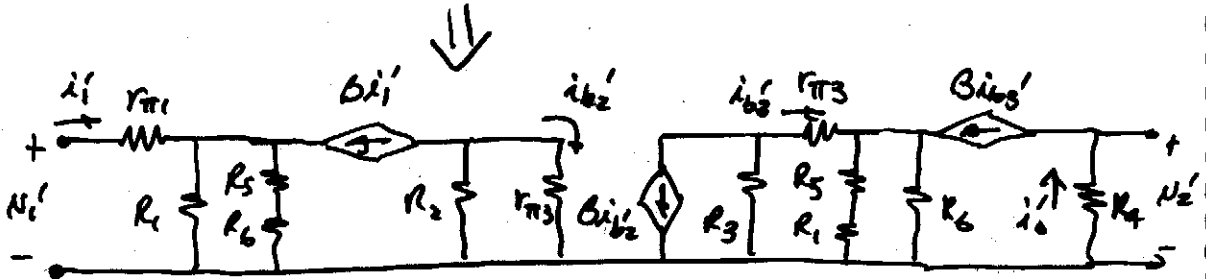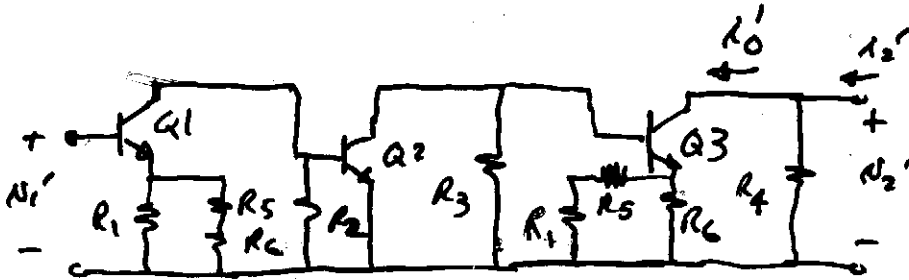

$$r_{\pi 1} = \frac{100 \cdot 25}{0.6} = 4.16 \text{ k}\Omega, \quad r_{\pi 2} = \frac{100 \cdot 25}{1} = 2.5 \text{ k}\Omega, \quad r_{\pi 3} = \frac{100 \cdot 25}{6} = 625 \Omega$$

$$\frac{i_o'}{i_i'} = \left(\frac{i_{o3}'}{i_{b3}'} \right) \left(\frac{i_{b3}'}{i_{b2}'} \right) \left(\frac{i_{b2}'}{i_i'} \right) = A$$

$$= (\beta) \left(\frac{-\beta R_3}{R_3 + r_{\pi 3} + (1+\beta)[R_6 \parallel (R_1 + R_5)]} \right) \left(\frac{-\beta R_2}{R_2 + r_{\pi 2}} \right) \left(\frac{1}{r_{\pi 1} + (1+\beta)[R_1 \parallel (R_5 + R_6)]} \right)$$

$$A = (100) (-34.43) (-78.3) \left(\frac{1}{12.97 \text{ k}\Omega} \right) = 20.78 \text{ A/V}$$

$\beta \neq 0$

$$\frac{i_o}{i_i} = \frac{A}{1 + AB} = \frac{20.78}{1 + (20.78)(11.9)} = \frac{20.78}{1 + 247.2} = \frac{20.78}{248.2} = 0.0837 \text{ A/V} \approx \frac{1}{11.9 \Omega}$$

$$R_{in}(\beta = 0) = r_{\pi 1} + (1+\beta)[R_1 \parallel (R_5 + R_6)] = 12.97 \text{ k}\Omega$$


$$o.c. R_{inF} = \frac{N_i}{i_i} = 12.97 \text{ k}\Omega (1 + AB) = 12.97 \text{ k}\Omega (248.2) = \underline{\underline{3.22 \text{ M}\Omega}}$$

$$\frac{N_2}{N_1} = \frac{-i_o R_4}{N_1} = \left(\frac{i_o}{i_i} \right) (-R_4) = (0.0837) (-600) = \underline{\underline{-50.2 \text{ V/V}}}$$

$$R_{out}(B=0) = \infty$$

$$R_{outF} = R_{out}(B=0)(1+AB) = \infty$$

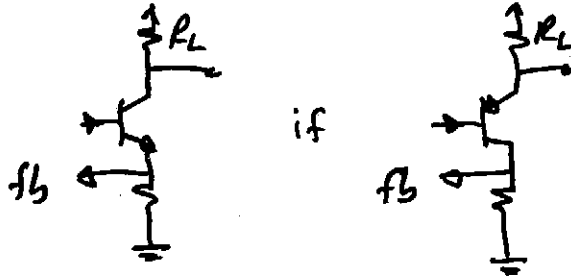
$$\frac{N_2}{\lambda_2} = (R_{outF} - R_f) \parallel R_f = \infty \parallel R_f = R_f = \underline{\underline{600\Omega}}$$




EXAMPLE OF FEEDBACK TOPOLOGY IDENTIFICATION

Use the rules of identifying feedback topologies to create the four different negative feedback topologies using the identical starting structure.


1. Voltage-Voltage (Series-Shunt)

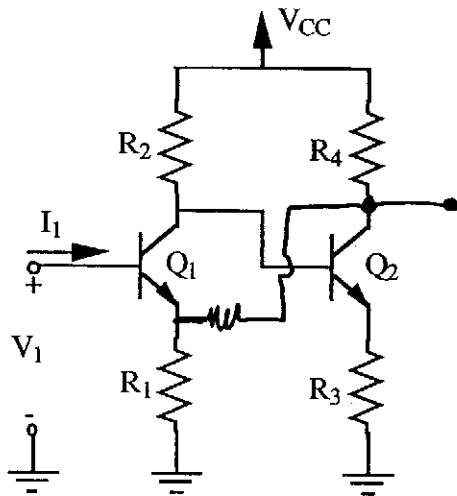

2. Current-Voltage (Shunt-Shunt)

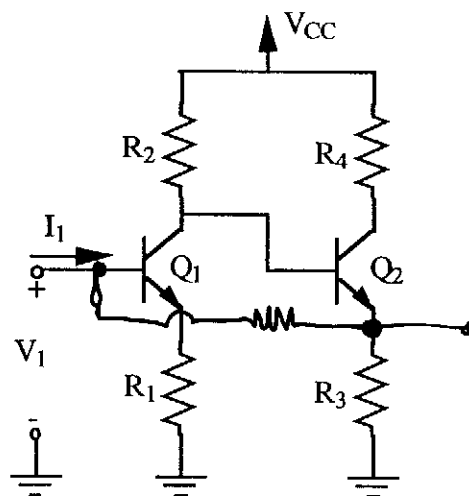

3. Voltage-Current (Series-Series)

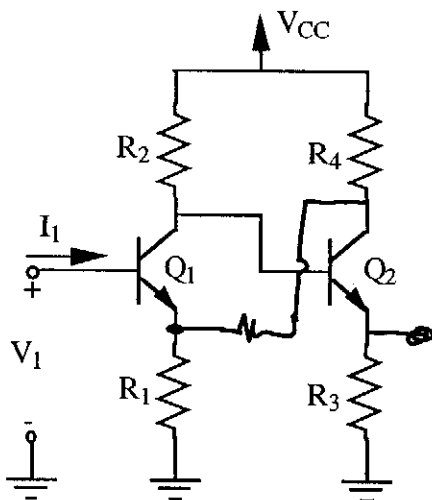

4. Current-Current (Shunt-Series)

