

Feedback Applications


18.8-Using feedback (negative) to control the frequency response.

Summary-

- 1.) Influence on resistance - shunt ↓, series ↑
- 2.) $A_F \approx \frac{1}{\beta}$ as loop gain $AB \gg 1$
- 3.) Method of identifying and analyzing fb. ckts.

Influence of -fb on frequency response -


Neg. fb ckt:

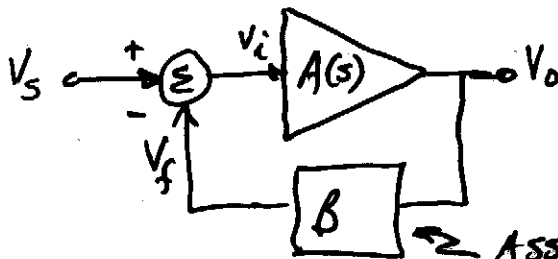

Assume β is not a function of frequency

$$A(s) = \frac{A_o \omega_n s}{(s + \omega_L)(s + \omega_H)}$$
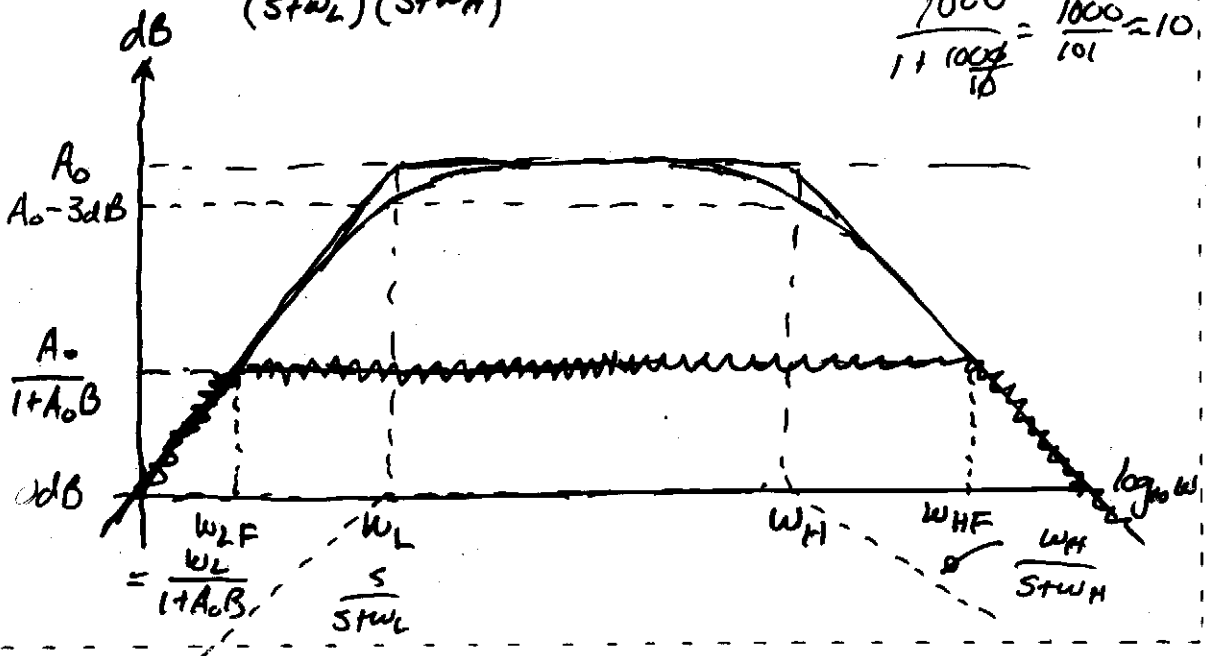
$$\frac{1000}{1 + \frac{1000s}{10}} = \frac{1000}{101} \approx 10$$



Approximate $A(s)$ as

1.) Low frequency response ($\omega < \omega_H$)

$$A(s) = \frac{A_0 \omega_H s}{(s + \omega_L)(s + \omega_H)} \rightarrow \frac{A_0 s}{s + \omega_L}$$

$$A_F(s) = \frac{A(s)}{1 + B A(s)} = \frac{1}{\frac{1}{A(s)} + B} = \frac{1}{\frac{s + \omega_L}{A_0 s} + B} = \frac{A_0 s}{s + \omega_L + s A_0 B}$$

$$A_F(s) = \frac{A_0 s}{s(1 + A_0 B) + \omega_L} = \left(\frac{A_0}{1 + A_0 B} \right) \left(\frac{s}{s + \frac{\omega_L}{1 + A_0 B}} \right)$$

$$= A_{0F} \frac{s}{s + \omega_{LF}}$$

$$\omega_{LF} = \frac{\omega_L}{1 + A_0 B} \quad \left\{ \begin{array}{l} A_{0F} = \frac{A_0}{1 + A_0 B} \end{array} \right.$$

2.) High frequency response ($\omega > \omega_L$)

$$A(s) = \frac{A_0 \omega_H s}{(s + \omega_L)(s + \omega_H)} \rightarrow \frac{A_0 \omega_H}{s + \omega_H}$$

$$A_F(s) = \frac{1}{\frac{1}{A(s)} + B} = \frac{1}{\frac{s + \omega_H}{A_0 \omega_H} + B} = \frac{A_0 \omega_H}{s + \omega_H + \omega_H A_0 B} = \frac{A_0 \omega_H}{s + \omega_H (1 + A_0 B)}$$

$$A_F(s) = \frac{A_0}{1 + A_0 B} \frac{\omega_H (1 + A_0 B)}{s + \omega_H (1 + A_0 B)} = A_F(0) \frac{\omega_{HF}}{s + \omega_{HF}}$$

$$\left\{ \begin{array}{l} A_F(0) = A_{0F} = \frac{A_0}{1 + A_0 B} \\ \omega_{HF} = \omega_H (1 + A_0 B) \end{array} \right.$$

18.9 Calculation of the Loop Gain of a Feedback Circuit

Why do we want to find the loop gain?

- 1.) Estimate the influence of feedback on impedance

$$\text{Shunt: } R_{inF} = \frac{R_{in}}{1 + \text{Loop Gain}} \quad \& \quad R_{outF} = \frac{R_{out}}{1 + \text{Loop Gain}}$$

$$\text{Series: } R_{inF} = R_{in}(1 + \text{Loop Gain}) \quad \& \quad R_{outF} = R_{out}^*(1 + \text{Loop Gain})$$

* R_{out} & R_{outF} is the resistance in series with the loop.

- 2.) To find the stability of the loop. I.e. will neg. fb. become pos. fb. and oscillate?