


Quiz 12-

Series at the output and shunt or series at the input

Calculating the loop gain (AB) -


- 1.) Direct method
- 2.) Successive voltage and current injection

Direct method -

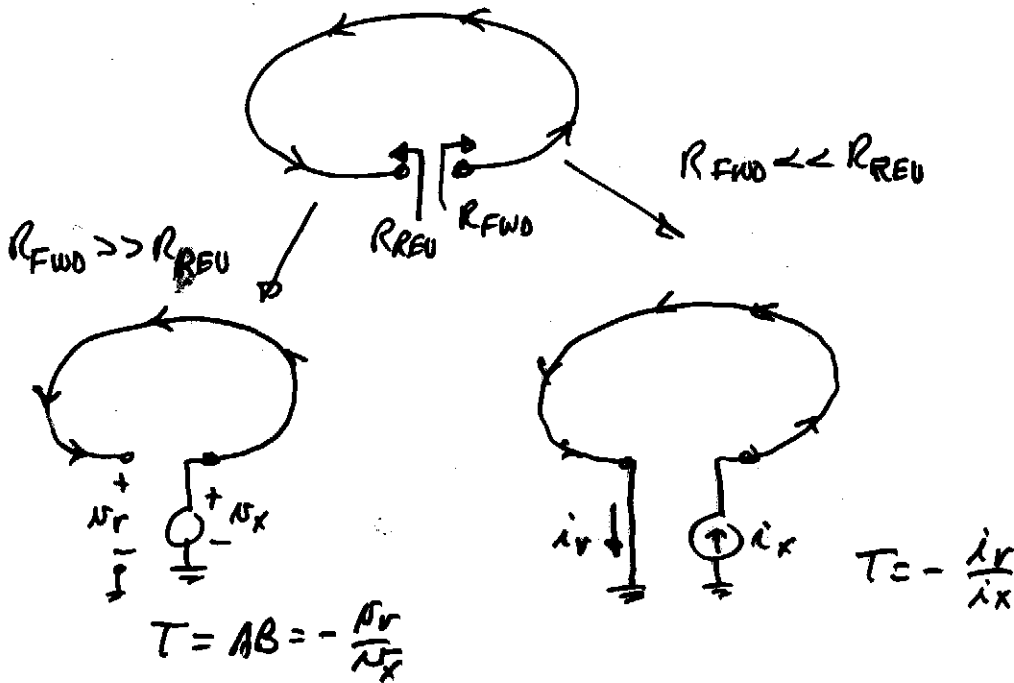

1.) Op Amp Example -



Find the open-loop gain -

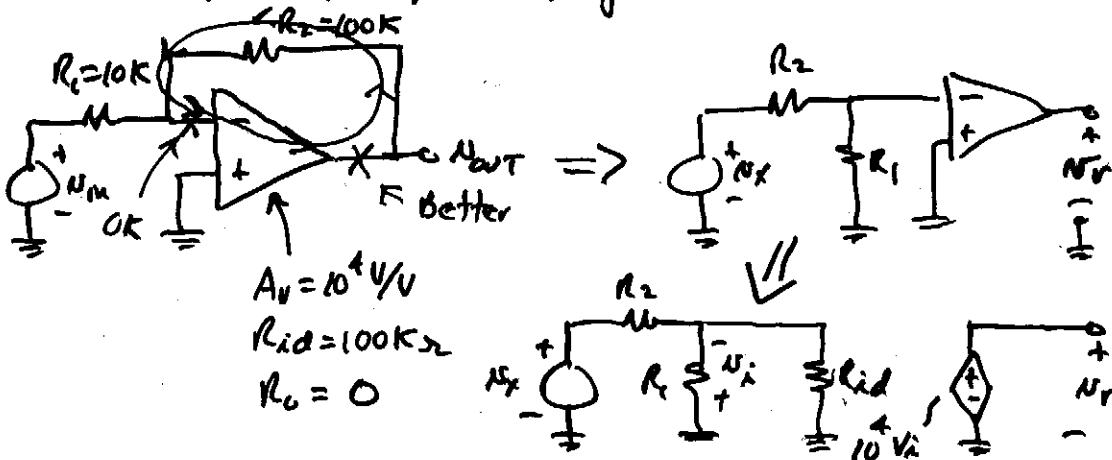

$$N_r = 10^4 N_x = -10^4 \left( \frac{R_1 R_{id}}{R_2 + R_1 R_{id}} \right) N_x = -10^4 \left( \frac{9.09}{109.09} \right) = -83.33$$

$$T = |AB| = - \frac{N_r}{N_x} = \underline{\underline{83.33 \text{ V/V}}}$$

Quiz 11

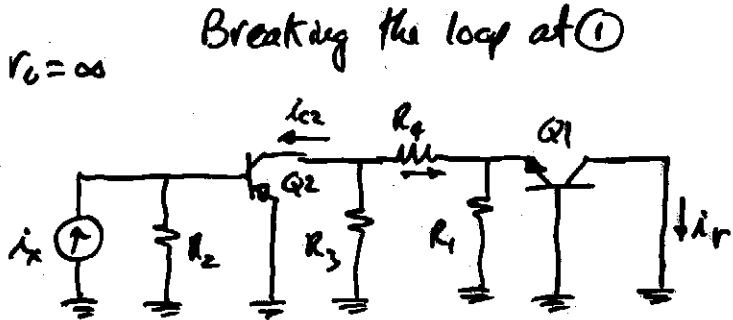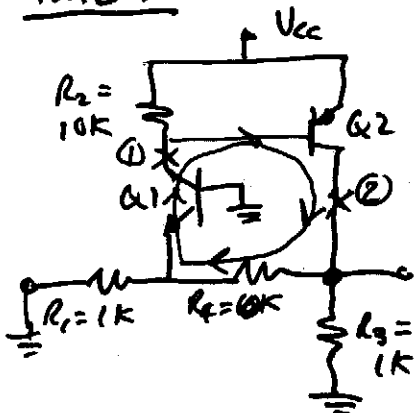

$$i_r = i_{cc2} \left[ \frac{-R_3}{R_3 + R_4 + R_1 \parallel \frac{1}{\beta_{Q1}}} \right] \left[ \frac{R_1}{R_1 + \frac{1}{\beta_{Q1}}} \right] \left( \frac{\beta}{1+\beta} \right)$$

$$i_x = \frac{R_2}{R_2 + r_{o2}}$$

$$\begin{aligned} -\frac{i_r}{i_x} &= \left[ \frac{R_3}{R_3 + R_4 + R_1 \parallel \frac{1}{\beta_{Q1}}} \right] \left( \frac{R_1}{R_1 + \frac{1}{\beta_{Q1}}} \right) \left( \frac{\beta}{1+\beta} \right) \left( \frac{R_2}{R_2 + r_{o2}} \right) \\ &= \left( \frac{1k}{11k + 0.2k} \right) \left( \frac{1k}{1.25k} \right) \left( \frac{100}{101} \right) \left( \frac{10k}{35k} \right) \\ &= 2.526 \left( \frac{1}{125} \right) = ?? \end{aligned}$$

STABILITY OF FEEDBACK AMPLIFIERS


$$A_F(s) = \frac{A(s)}{1 + \underbrace{A(s)B(s)}_{\text{Loop gain}}} = \frac{A(s)}{1 + \underbrace{T(s)}_{\text{Loop gain}}}$$

Approaches to Determining Stability

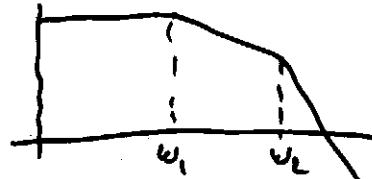
1.) Nyquist Plot

Plot  $T(j\omega)$  or  $A(j\omega)B(j\omega)$  on a complex frequency plane from  $\omega = -\infty$  to  $\omega = +\infty$ . If this plot encloses the  $-1$  point, the amplifier is unstable.

$$T(s) = \frac{A_0}{\left(\frac{s}{\omega_1} + 1\right)\left(\frac{s}{\omega_2} + 1\right)}$$



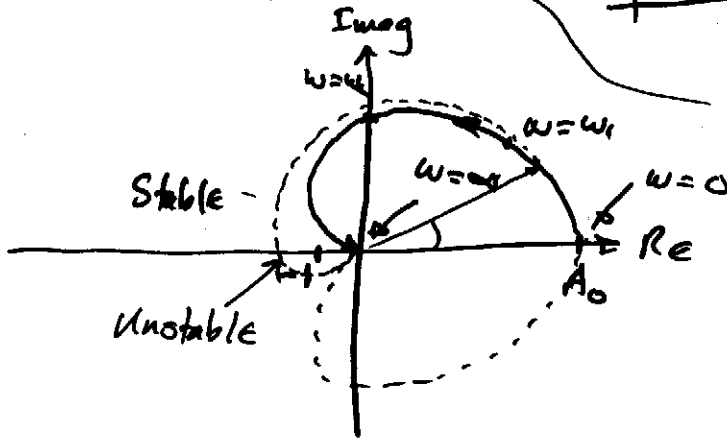
$$T(j\omega) = \frac{A_0}{\left(1 + j\frac{\omega}{\omega_1}\right)\left(1 + j\frac{\omega}{\omega_2}\right)}$$



2.) Bode Plot

Plot  $|T(j\omega)|$  and  $\text{Arg}[T(j\omega)]$

$$\frac{A(s)}{1+T(s)}$$

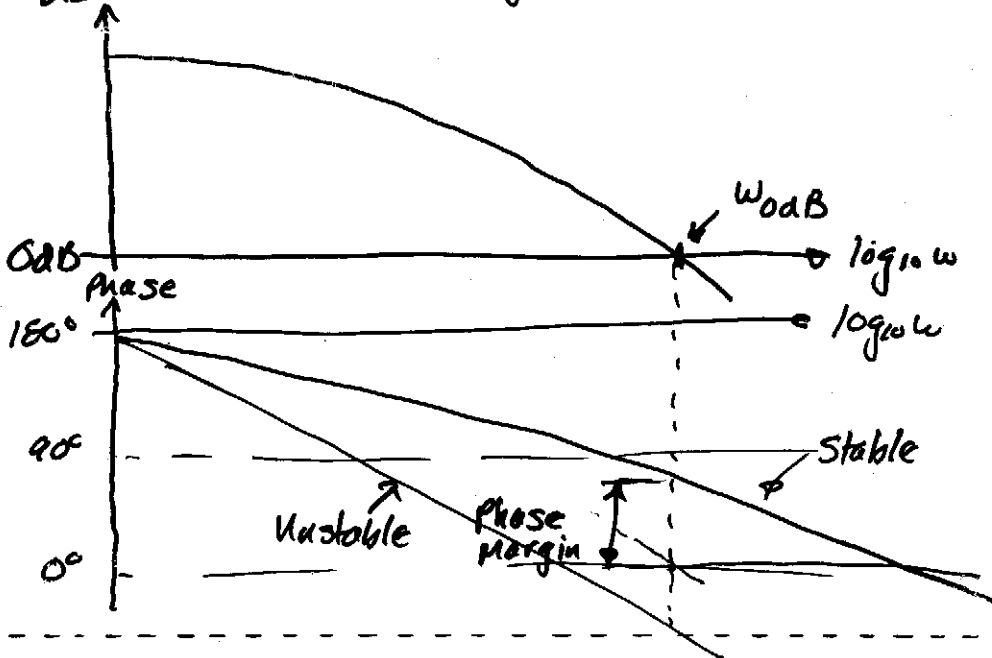

### Bode Criteria-

A feedback amplifier is stable if


a.)  $\text{Arg}[T(j\omega_{0dB})] > 0^\circ$

The loop phase shift must be less than  $180^\circ$  when the loop magnitude is 1 (0dB).

or

b.)  $|T(j\omega_{0^\circ})| < 1$

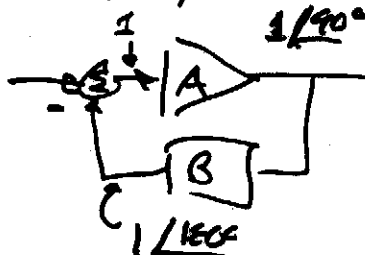The loop magnitude must be less than 1 when the phase shift of the loop is  $180^\circ$ .



Example -

$$T(j\omega) = \frac{10^3}{(1 + j\frac{\omega}{100})(1 + j\frac{\omega}{105})}$$

