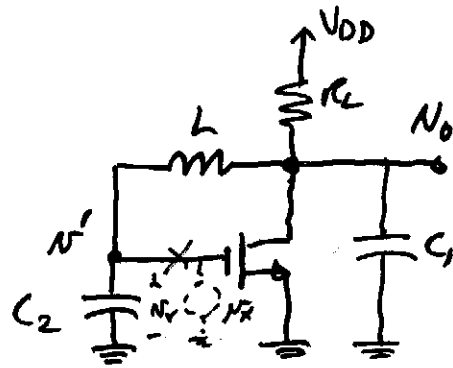



Example of an LC Oscillator

An LC oscillator is shown.  
Find an expression for the frequency of oscillation and the value of  $g_m R_L$  necessary to oscillate.



Assume that the value of  $r_{E5} = \infty$ .

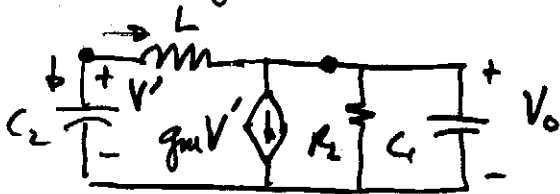Small-signal model - (Determinant = 0) approach



$$g_m V' + G_L V_0 + s C_1 V_0 + \frac{(V_0 - V')}{sL} = 0$$

$$s C_2 V' + \frac{(V' - V_0)}{sL} = 0$$

$$s C_2 V' + \frac{V'}{sL} = \frac{V_0}{sL} \rightarrow V_0 = (1 + s^2 L C_2) V'$$

$$g_m V' + (G_L + s C_1 + \frac{1}{sL})(1 + s^2 L C_2) V' - \frac{V'}{sL} = \Delta = 0$$

Assuming a non-zero value of  $V'$ , then

$$g_m + (G_L + s C_1 + \frac{1}{sL})(1 + s^2 L C_2) - \frac{1}{sL} = 0$$

$$g_m + G_L + s C_1 + \frac{1}{sL} + s^2 L C_2 G_L + s^3 L C_1 C_2 + s C_2 - \frac{1}{sL} = 0$$

$$[g_m + G_L - \omega^2 L C_2 G_L] + j\omega [C_1 + C_2 - \omega^2 L C_1 C_2] = 0$$

$$g_m + G_L = \omega^2 L C_2 G_L$$


$$\omega_{osc} = \sqrt{\frac{C_1 + C_2}{L C_1 C_2}} = \frac{1}{\sqrt{L \frac{C_1 C_2}{C_1 + C_2}}}$$

$$g_m + G_L = L C_2 G_L \left( \frac{C_1 + C_2}{L C_1 C_2} \right) = G_L \left( 1 + \frac{C_2}{C_1} \right) = g_L + G_L \frac{C_2}{C_1}$$



$$g_m = G_L \frac{C_2}{C_1} \rightarrow \boxed{g_m R_L = \frac{C_2}{C_1}}$$

12.12- Nonlinear Circuits using Op Amp


Rectification

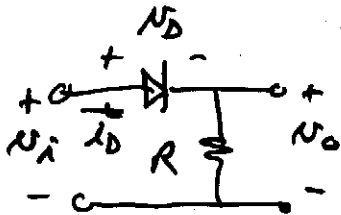

$$N_o = N_i - N_D$$

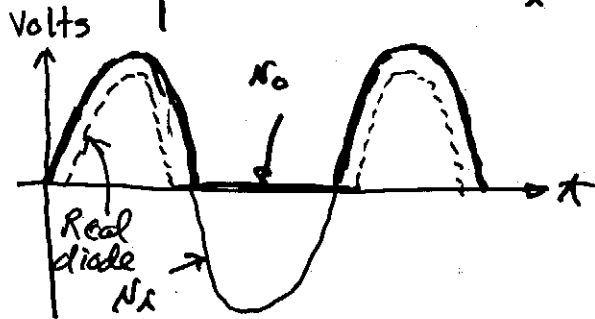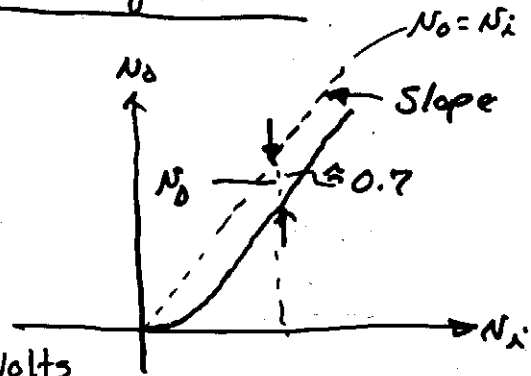

"Super Diode"

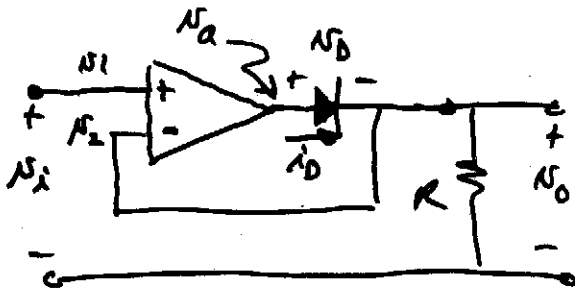

Assume that  $A_N \gg 1$

$$N_o = N_a - N_D$$

$$N_a = A_N(N_i - N_o)$$

$$N_o = A_N(N_i - N_o) - N_D$$

$$N_o = A_N(N_i - N_o) - N_D = A_N N_i - A_N N_o - N_D$$

$$N_o(1 + A_N) = A_N N_i - N_D$$

$$N_o = \frac{A_N}{1 + A_N} N_i - \frac{N_D}{1 + A_N} \xrightarrow{A_N \rightarrow \infty} N_i$$

If  $A_N \rightarrow \infty \rightarrow \underline{\underline{N_o = N_i}}$

Principle?