

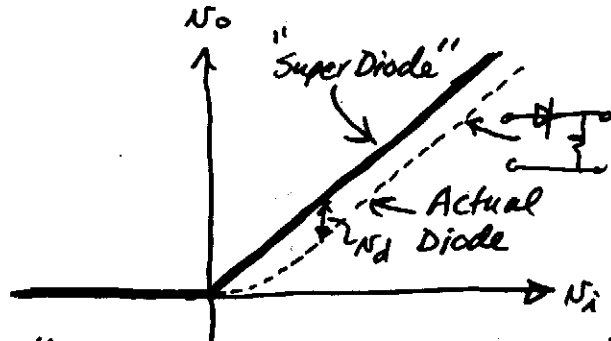


Nonlinear Circuits using the Op Amp

"Super Diode"

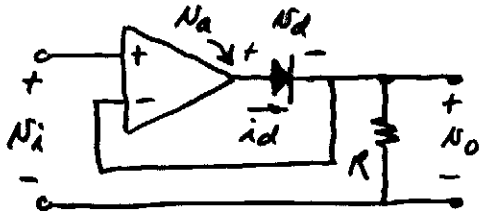

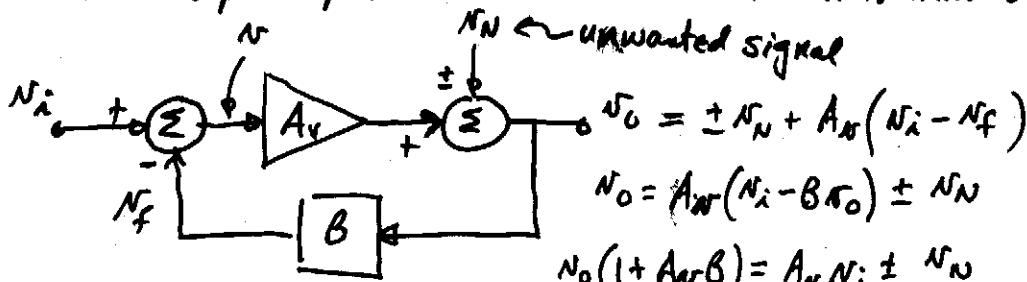What is the principle behind this circuit which makes it work?



$$N_o = \pm N_n + A_v(N_i - N_f)$$

$$N_o = A_v(N_i - B N_o) \pm N_n$$

$$N_o(1 + A_v B) = A_v N_i \pm N_n$$

$$N_o = \frac{A_v N_i \pm N_n}{1 + B A_v}$$


As $A_v B \gg 1$,

$$N_o = \frac{N_i \pm \frac{N_n}{B}}{1 + B A_v} = \frac{N_i}{B} \quad \text{In the "superdiode" } B=1$$


$$\text{so } N_o = N_i$$

Practical Application of the above ideas -

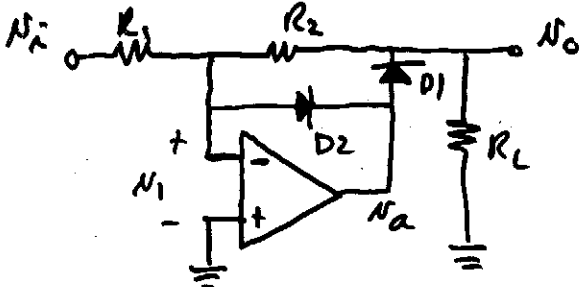(Problem is in the "super diode", the op amp does not have feedback when the diode is off.)




Note that D1 and D2 cannot both be on.

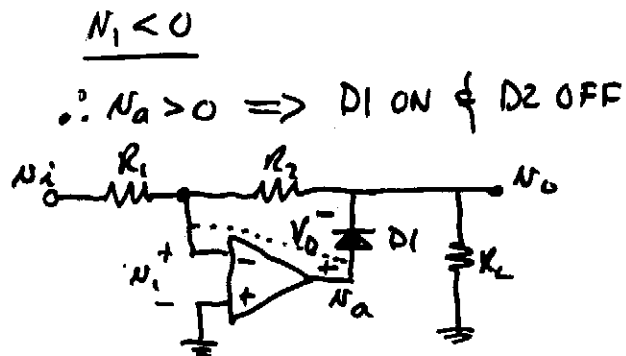

$N_i < 0$
 $\therefore N_o > 0 \Rightarrow D1 \text{ ON } \& D2 \text{ OFF}$

Cont'd

$$N_0 = N_a - V_D = -A_N N_1 - V_D$$
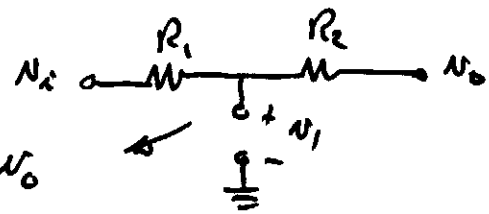
$$N_1 = ? \quad N_1 = \frac{R_2}{R_1 + R_2} N_i + \frac{R_1}{R_1 + R_2} N_0$$


$$N_0 = -A_N \left[\frac{R_2}{R_1 + R_2} N_i + \frac{R_1}{R_1 + R_2} N_0 \right] - V_D$$


$$N_0 \left[1 + \frac{A_N R_1}{R_1 + R_2} \right] = -A_N \frac{R_2}{R_1 + R_2} N_i - V_D$$

$$N_0 = \left(-\frac{R_2}{R_1} \right) \frac{A_N \frac{R_1}{R_1 + R_2}}{1 + A_N \frac{R_1}{R_1 + R_2}} - \frac{V_D}{1 + A_N \frac{R_1}{R_1 + R_2}}$$

$A_N \frac{R_1}{R_1 + R_2} \gg 1$


$$N_0 = -\frac{R_2 N_i}{R_1} - \frac{V_D}{1 + A_N \frac{R_1}{R_1 + R_2}}$$

$$N_0 \approx -\frac{R_2 N_i}{R_1}$$

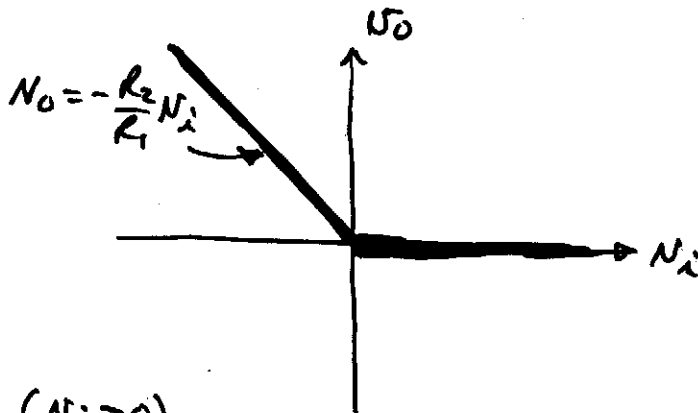

$N_i > 0$ ($N_i > 0$)



D1 OFF, D2 ON

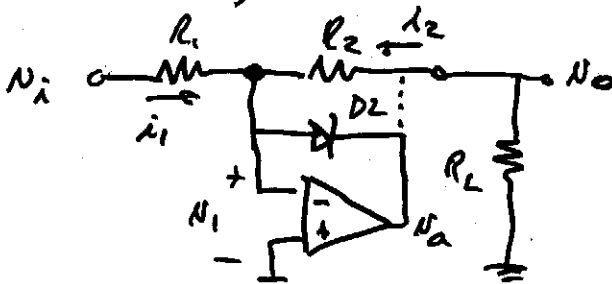

$$i_1 = \frac{N_i}{R_1}, \quad i_2 = \frac{N_0}{R_2} = 0$$

$$N_0 = 0$$

Reverse the Direction of the Diodes

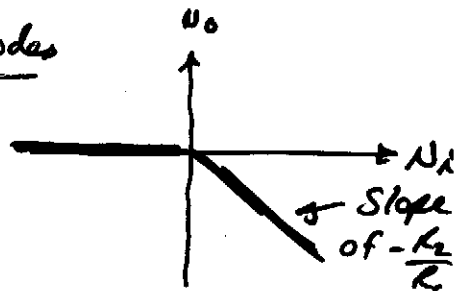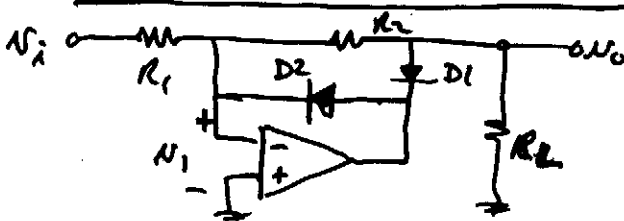

Example

Design an op amp circuit which gives $N_o = -(N_{in})$ using the previous practical op amp diode circuits

