

QUIZ NO. 1

NAME _____ Score _____ /10

If $\beta_F = 100$ and $V_{BEQ} = 0.6\text{V}$, solve for the dc values of I_B , I_C , I_E , V_B , V_C , and V_E of the transistor circuit shown.

