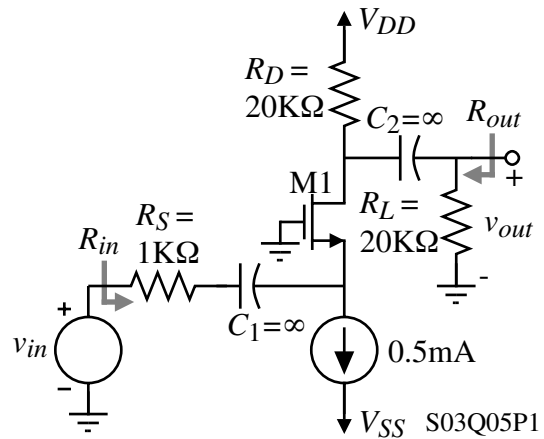



QUIZ NO. 5 - SOLUTION

(Average score = xx/10 of those students taking the quiz.)

A NMOS common-gate amplifier is shown. Assume the parameters of the transistor are $K_N = 1\text{mA/V}^2$, $V_{TN} = 1\text{V}$, and $\lambda = 0$. (a.) Find the small signal model parameter values for g_m and r_{ds} . (b.) Find an algebraic expression for the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} . (c.) Numerically evaluate the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} .

Solution

1.) Small-signal model:

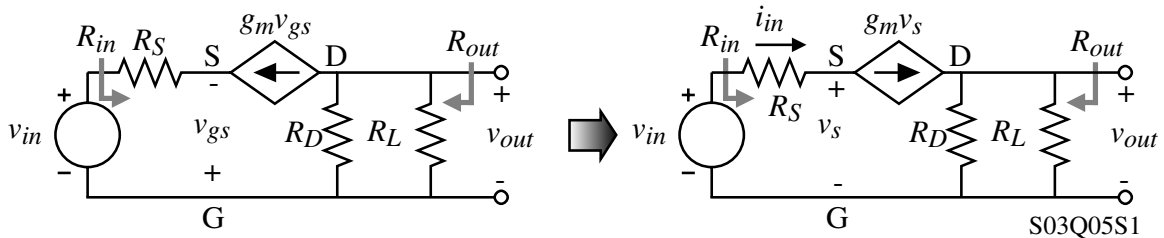2.) Find g_m and r_{ds} : $g_m = \sqrt{2K_N I_D} = \sqrt{2 \cdot 1 \cdot 0.5} = 1\text{mS}$ and $r_{ds} = \infty$ (ignore V_{DS})3.) Find R_{in} , R_{out} , and v_{out}/v_{in} . $R_{in} = ?$

$$v_{in} = g_m R_S v_s + v_s \quad \text{and} \quad i_{in} = g_m v_s$$

$$\therefore R_{in} = \frac{v_{in}}{i_{in}} = \frac{g_m R_S v_s + v_s}{g_m v_s} = R_S + \frac{1}{g_m} = 1\text{k}\Omega + 1\text{k}\Omega = \underline{\underline{2\text{k}\Omega}}$$

 $R_{out} = ?$

$$R_{out} = R_D \parallel R_L = \underline{\underline{10\text{k}\Omega}}$$

Voltage gain = ?

$$\frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_s} \frac{v_s}{v_{in}} = (g_m R_{out}) \left(\frac{1}{1 + g_m R_S} \right) = (10) \left(\frac{1}{1 + 1 \cdot 1} \right) = \underline{\underline{\pm 5\text{V/V}}}$$