

**QUIZ NO. 8 - SOLUTION**



(Average score = 6.4/10 of those taking the quiz.)

A BJT amplifier is shown. Assume that the BJT has the small signal parameters of  $\beta_F = 100$ ,  $V_T = 25\text{mV}$ , and  $V_A = \infty$ .

- Find the midband voltage gain of this amplifier,  $V_{out}/V_{in}$ .
- Find the value of the lower -3dB frequency,  $f_L$ , in Hz, using any method that is appropriate.

Solution

Small-signal model for this problem:

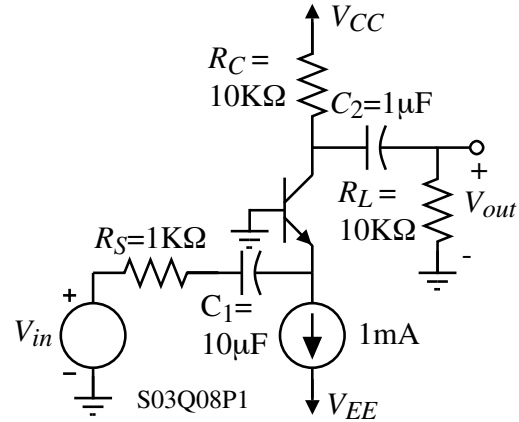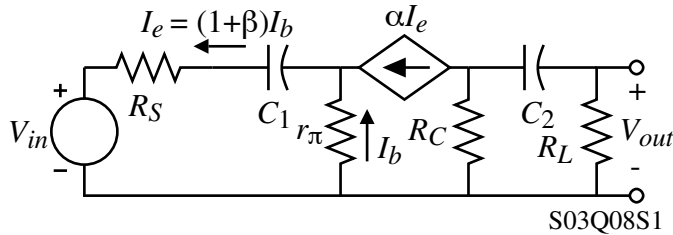

$$g_m = \frac{1\text{mA}}{25\text{mV}} = 40\text{mS}$$

$$r_\pi = \frac{\beta_F}{g_m} = 2.5\text{k}\Omega$$

Use the direct approach:

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \left( \frac{V_{out}}{I_e} \right) \left( \frac{I_e}{V_{in}} \right) = \left( \frac{-\alpha_F R_C R_L}{R_C + R_L + \frac{1}{sC_2}} \right) \left( \frac{-1}{R_S + \frac{1}{sC_1} + \frac{1}{g_m}} \right) \\ &= \left( \frac{\alpha_F R_C R_L}{R_C + R_L} \right) \left( \frac{g_m}{1 + g_m R_S} \right) \left( \frac{s}{s + \frac{1}{C_2(R_C + R_L)}} \right) \left( \frac{s}{s + \frac{1}{C_1 \left( R_S + \frac{1}{g_m} \right)}} \right) \end{aligned}$$

$$\therefore MBG = \left( \frac{\alpha_F R_C R_L}{R_C + R_L} \right) \left( \frac{g_m}{1 + g_m R_S} \right) = (5\text{K}) \left( \frac{40\text{mS}}{1 + 40} \right) = \frac{200}{41} = \underline{\underline{+4.878\text{V/V}}}$$

$$\omega_1 = \frac{1}{C_1 \left( R_S + \frac{1}{g_m} \right)} = \frac{10^6}{10(1000 + 25)} = 97.56 \text{ rads/sec.}$$

$$\omega_2 = \frac{1}{C_2(R_C + R_L)} = \frac{10^6}{1(20\text{K})} = 50 \text{ rads/sec.}$$

Since  $\omega_1$  and  $\omega_2$  are within an octave of each other then there is no dominant root so that we will simply sum the roots which is identical with the short-circuit time constant approach to give,  $\omega_L$  as,

$$\omega_L \approx \omega_1 + \omega_2 = 147.56 \text{ rads/sec.} \rightarrow f_L \approx \underline{\underline{23.5 \text{ Hz}}}$$