

**QUIZ NO. 9 - SOLUTION**

(Average score = 7.1/10 of the number of students taking this quiz.)


A NMOS amplifier is shown. Assume that the small-signal parameters of the MOSFET are  $g_m =$

1mS,  $r_{ds} = \infty$ ,  $C_{gs} = 9\text{pF}$ , and  $C_{gd} = 1\text{pF}$ .

a.) Find the midband voltage gain of this amplifier,  $V_{out}/V_{in}$ .

b.) Find the value of the upper -3dB frequency,  $f_H$ , in HZ, first using the Miller approximation and secondly using the open-circuit time constant approach.


c.) Which of the two answers for  $f_L$  in part b.) is the most accurate and why?

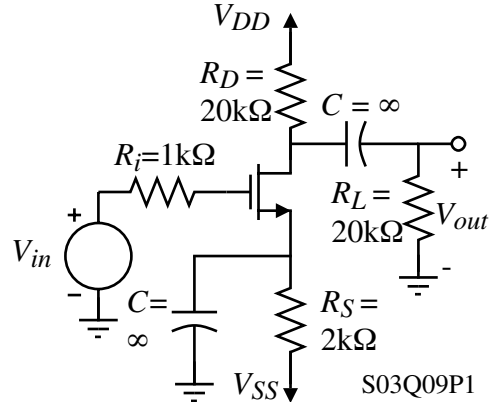Solution

a.) The small-signal model for all three parts of this problem is shown.

The MBG is easily found by inspection as,
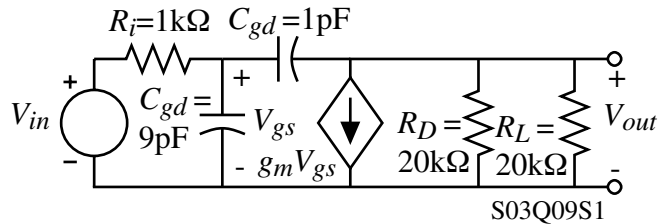
$$\frac{V_{out}(0)}{V_{in}(0)} = -g_m(R_D \parallel R_L) = \underline{\underline{-10 \text{ V/V}}}$$



b.) The Miller approximation gives the following capacitance between gate and source.

$$C_{eq} = C_{gs} + (1 - \text{MBG}) C_{gd} = 9\text{pF} + (1 + 10)1\text{pF} = 20\text{pF}.$$

$$\therefore \omega_H = \frac{1}{R_S C_{eq}} = \frac{1}{1\text{K} \cdot 20\text{pF}} = 50 \text{ Mrads/sec.} \quad \rightarrow \quad f_H = \frac{50 \times 10^6}{2\pi} = \underline{\underline{7.96\text{MHz}}}$$

The OCTC approach requires finding  $R_{cgsO}$  and  $R_{cgdO}$ . These are found as,

$$R_{cgsO} = R_i = 1\text{k}\Omega$$

$$R_{cgdO} = ?$$

$$V_t = V_{gs} + (I_t + g_m V_{gs})10\text{k}\Omega$$

$$= I_t R_i + (I_t + g_m I_t R_i)10\text{k}\Omega$$

$$\therefore R_{cgdO} = \frac{V_t}{I_t} = R_i + (1 + g_m R_i)10\text{k}\Omega = 1\text{k}\Omega + (1 + 1)10\text{k}\Omega = 21\text{k}\Omega$$

$$\therefore \omega_H = \frac{1}{R_{cgsO} C_{gs} + R_{cgdO} C_{gd}} = \frac{1}{1\text{K} \cdot 9\text{pF} + 21\text{K} \cdot 1\text{pF}} = \frac{1000}{30} \times 10^6 = 33.3 \times 10^6 \text{ rads/sec.}$$

$$\text{Thus, } f_H = \frac{33.3 \times 10^6}{2\pi} = \underline{\underline{5.3\text{MHz}}}$$

c.) The answer given by the OCTC method is more correct because the impedance of  $C_{gd}$  at  $\omega_H$  for the Miller approach turns out to be  $(1/50 \times 10^6 \cdot 10^{-12}) = 20\text{k}\Omega$  which is not that much greater than  $R_L \parallel R_D = 10\text{k}\Omega$ .

