



QUIZ NO. 10 - SOLUTION

(Average Score = 6.7/10 of those who took the quiz)

A series-shunt feedback amplifier is shown. Use the methods of feedback analysis to find the numerical values of v_2/v_1 , v_1/i_1 , and v_2/i_2 . Assume that all transistors are matched and that $g_m = 1\text{mS}$ and $r_{ds} = \infty$.


Solution

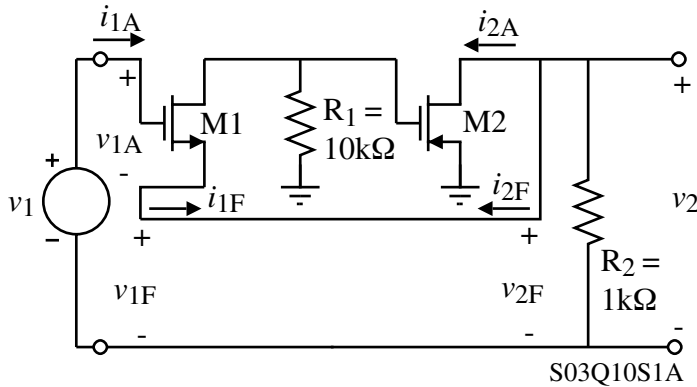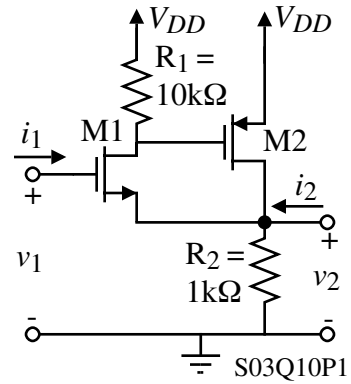The circuit can be redrawn as shown to identify more clearly the A circuit and the feedback circuit.



$$\beta = h_{12F} = \frac{v_{1F}}{v_{2F}} \Big|_{i_{1F}=0} = 1(\text{V/V})$$

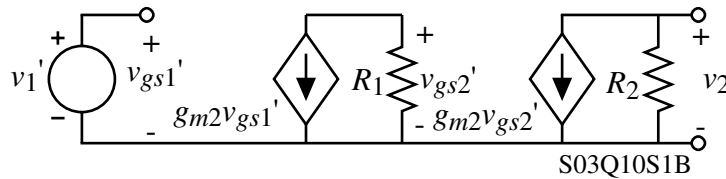The small-signal model for the open-loop calculation of A.



$$A_{\beta=0} \Big| = \frac{v_2'}{v_1'} = \left(\frac{v_2'}{v_{gs2}'} \right) \left(\frac{v_{gs2}'}{v_{gs1}'} \right) \left(\frac{v_{gs1}'}{v_1'} \right) = (-g_{m2}R_2)(-g_{m1}R_1)(1) = (-10)(-1)(1) = 10 \text{ V/V}$$

$$A_F = \frac{v_2}{v_1} = \frac{A}{1+A\beta} = \frac{10}{1+10(1)} = \frac{10}{11} = \underline{0.909 \text{ V/V}}$$

Because $h_{11T} = \infty$, $R_{in} = v_1/i_1 = \underline{\underline{\infty}}$

The open-loop output resistance is,

$$R_o = R_2 = 1000\Omega$$

$$\therefore R_{out} = \frac{v_2}{i_2} = \frac{R_o}{1+A\beta} = \frac{1000\Omega}{11} = \underline{91 \Omega}$$