

## QUIZ NO. 11

NAME \_\_\_\_\_ Score \_\_\_\_\_ /10

A shunt-shunt feedback amplifier is shown. Use the methods of feedback analysis to find the numerical values of  $v_2/v_1$ ,  $v_1/i_1$ , and  $v_2/i_2$ .

Assume that all transistors are matched and that  $V_T = 25\text{mV}$ ,  $\beta$  (of the BJT) = 100,  $I_{C1} = I_{C2} = 100\mu\text{A}$ , and  $r_o = \infty$ .

