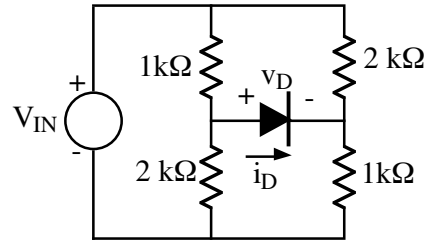



**Homework Assignment No. 1**

Due on Monday, January 12, 2004

- 1.) (a.) Find the dc current,  $I_{DQ}$ , and the dc voltage,  $V_{DQ}$ , of the diode in the circuit shown if  $V_{IN}$  is +10V. Assume the large signal model for the diode is a short circuit when  $v_D \geq 0V$  and an open circuit when  $v_D \leq 0V$ . (b.) Repeat part (a.) if  $V_{IN} = -10V$ .




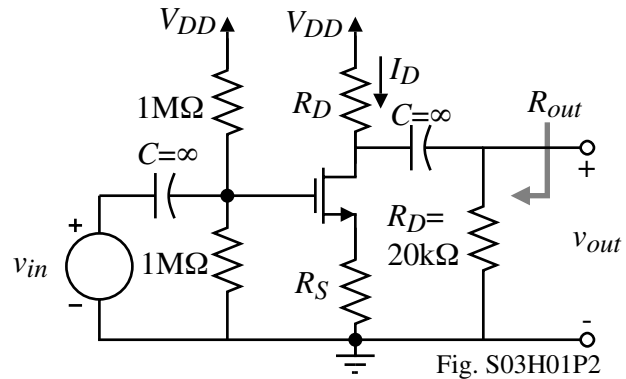- 2.) An enhancement NMOS amplifier is shown. The following questions are independent of each other (i.e. the answer of one is *not* used in the next question).




- (a.) If  $I_D = 0.5mA$ ,  $V_T = 1V$ , and  $K = 0.5mA/V$ , find  $g_m$ .
- (b.) If  $g_m = 0.5mA/V$  and  $r_o = \infty$ , find an algebraic expression for  $R_{out}$  and  $A_v = v_{out}/v_{in}$ .
- (c.) Design  $R_D$  and  $R_S$  to give  $R_{out} = 10k\Omega$  and  $A_v = -10V/V$  if  $g_m = 2mA/V$  and  $r_o = \infty$ .

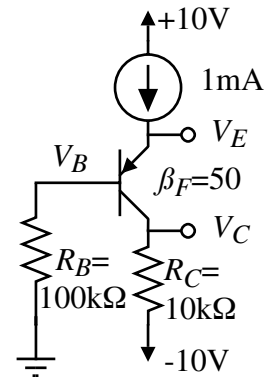- 3.) A pnp BJT circuit is shown. (a.) Find the dc values of  $I_E$ ,  $I_C$ ,  $I_B$ ,  $V_E$ ,  $V_C$  and  $V_B$  if  $\beta = 50$  and  $V_{EB(on)} = 0.65V$ . (b.) For what value of  $R_C$  does the BJT become saturated? (Recall that saturation of a BJT corresponds to the *BE* and *BC* junctions forward biased.)




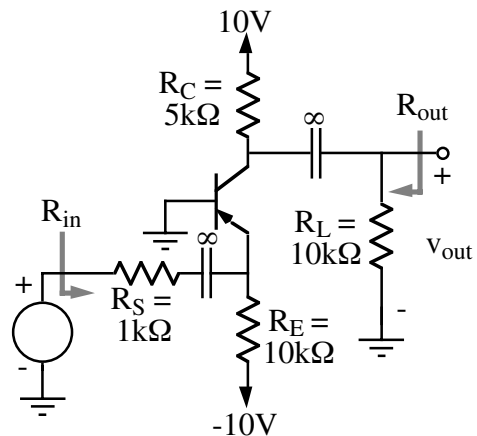- 4.) For the transistor shown,  $\beta = 100$ ,  $r_{\pi} = 2.5k\Omega$ , and  $g_m = 0.04S$ . Draw the small signal model and find the numerical values of the small signal voltage gain,  $v_{out}/v_{in}$ , the input resistance,  $R_{in}$ , and the output resistance,  $R_{out}$ .




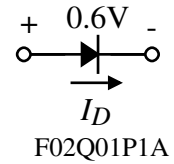5.) The following questions give the dc voltages at the terminals of an active device. You are to calculate the designated dc current.


a.) Find the diode current,  $I_D$ , where  $I_S = 100\text{fA}$  and  $V_T = 0.025\text{V}$  (2 pts).



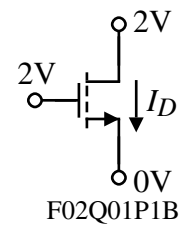b.) Find the drain-source current,  $I_{DS}$ , where  $K_n' = 25\mu\text{A}/\text{V}^2$ ,  $V_{TN} = 1\text{V}$  and  $W/L = 10$  (2 pts).



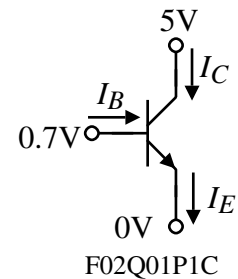c.) Find the collector, emitter, and base currents,  $I_C$ ,  $I_E$ , and  $I_B$  if  $I_S = 100\text{fA}$ ,  $V_T = 0.025\text{V}$  and  $\beta_F = 100$  (4 pts).



d.) Repeat (b.) if  $V_D = 1\text{V}$  and  $V_G = 3\text{V}$  (2 pts).