

**Homework Assignment No. 3 - Solution**

1.) The differential amplifier below uses an ideal op amp. Find the values of  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  if the single-ended input resistances,  $R_{in1}$  and  $R_{in2}$  are to be  $100\text{k}\Omega$  and the output voltage is to be  $v_{out} = 10(v_1 - v_2)$ .

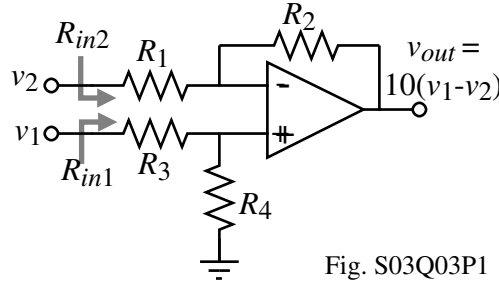


Fig. S03Q03P1

**Solution**

The first step is to find  $v_{out}$  as a function of  $v_1$  and  $v_2$  and to find  $R_{in1}$  and  $R_{in2}$ .

The output voltage can be found by using superposition applied to the inputs  $v_1$  and  $v_2$ .

The result is,

$$v_{out} = \left( \frac{v_{out}}{v_1} \right)_{v_2=0} + \left( \frac{v_{out}}{v_2} \right)_{v_1=0} = \left( \frac{R_1+R_2}{R_1} \right) \left( \frac{R_4}{R_3+R_4} \right) v_1 - \left( \frac{R_2}{R_1} \right) v_2$$

$R_{in1} = R_3 + R_4$  (remember to set  $v_2$  to zero in this calculation – only one excitation at a time)

$R_{in2} = R_1$  (remember to set  $v_1$  to zero in this calculation – only one excitation at a time)

From the input resistance results, we can write that,

$$R_3 + R_4 = 100\text{k}\Omega \text{ and } \underline{R_1 = 100\text{k}\Omega}$$

Substituting these values in the voltage gain expression gives,

$$v_{out} = \left( \frac{R_1+R_2}{100\text{k}\Omega} \right) \left( \frac{R_4}{100\text{k}\Omega} \right) v_1 - \left( \frac{R_2}{100\text{k}\Omega} \right) v_2 = 10(v_1 - v_2)$$

This gives us  $\underline{R_2 = 1\text{M}\Omega}$ . Substituting this back into the voltage gain expression gives,


$$v_{out} = \left( \frac{1100\text{k}\Omega}{100\text{k}\Omega} \right) \left( \frac{R_4}{100\text{k}\Omega} \right) v_1 - 10 v_2 = 10(v_1 - v_2) \rightarrow R_4 = \frac{1000\text{k}\Omega}{11} = \underline{90.9\text{k}\Omega}$$

Since the sum of  $R_3$  and  $R_4$  must equal  $100\text{k}\Omega$ , we get

$$R_3 = 100\text{k}\Omega - 90.9\text{k}\Omega = \underline{9.1\text{k}\Omega}$$

Substituting these values back into the top three equations satisfies the requirements.

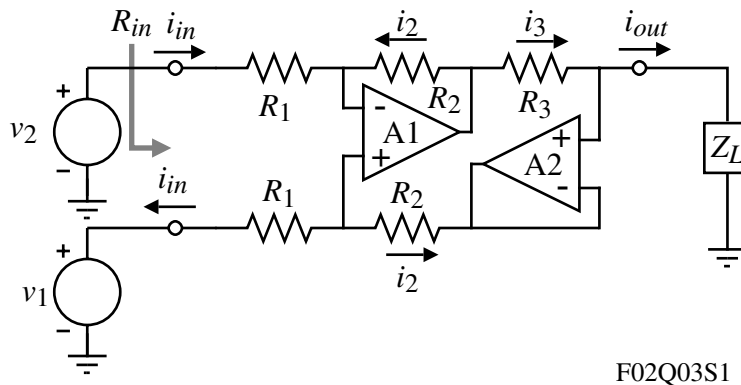2.) Assume that the op amps are ideal and find  $i_{out}$  as a function of the inputs,  $v_1$  and  $v_2$ . Find the input resistance defined as  $R_{in} = (v_2 - v_1)/i_{in}$ .



F02Q03S1

### Solution

From the circuit we can write the following equations based on an ideal op amp:

$$i_{out} = i_3, \quad v_2 - v_1 = 2R_1 i_{in}, \quad i_2 R_2 + i_2 R_2 = i_3 R_3, \quad i_{in} = -i_2$$

$$\therefore i_{out} = i_3 = \frac{2R_2 i_2}{R_3} = \frac{2R_2}{R_3} (-i_{in}) = \frac{2R_2}{R_3} \left( -\frac{v_2 - v_1}{2R_1} \right) = \frac{R_2}{R_1 R_3} (v_1 - v_2)$$

$$\boxed{i_{out} = \frac{R_2}{R_1 R_3} (v_1 - v_2)}$$

The input resistance,  $R_{in}$  is seen to be equal to  $2R_1$ .  $\boxed{R_{in} = 2R_1}$

3.) Problem 11.38 (12.24) of the text

Applying op-amp assumption 1 to the circuit on the next page, the voltage at the top of  $R_2$  is  $v_{O2}$ , and applying op-amp assumption 2,

$$\frac{\mathbf{v}_s}{R_1} = -\frac{\mathbf{v}_{O2}}{R_2} \quad \text{or} \quad \mathbf{v}_{O2} = -\mathbf{v}_s \frac{R_2}{R_1}$$


Since the op-amp input currents are zero, and

$$\mathbf{i} = \frac{\mathbf{v}_s}{R_1}, \quad \mathbf{v}_{O1} = -\mathbf{i}R_2 - \mathbf{i}R_3 = -\left(\frac{R_2}{R_1} + \frac{R_3}{R_1}\right)\mathbf{v}_s$$

Alternatively, the voltage at the bottom of  $R_2$  is zero, so

$$\mathbf{v}_{O1} = \left(1 + \frac{R_3}{R_2}\right)\mathbf{v}_{O2} = \left(1 + \frac{R_3}{R_2}\right)\left(-\frac{R_2}{R_1}\right)\mathbf{v}_s = -\left(\frac{R_2}{R_1} + \frac{R_3}{R_1}\right)\mathbf{v}_s$$

See next page for figure

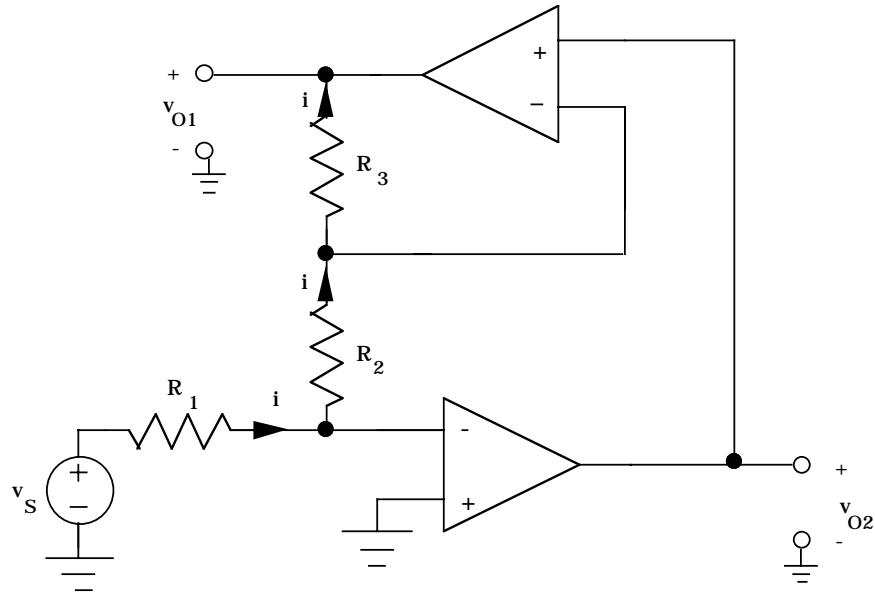

4.) Problem 11.39 of the text.

$$V_O = -V_{REF} \left( \frac{R}{4R} + \frac{R}{8R} \right) = -3.2 \left( \frac{1}{4} + \frac{1}{8} \right) = -1.2 \text{ V}$$

$$V_O = -V_{REF} \left( \frac{R}{2R} + \frac{R}{16R} \right) = -3.2 \left( \frac{1}{2} + \frac{1}{16} \right) = -1.8 \text{ V}$$

0000	0.000 V	1000	-1.60 V
0001	-0.200 V	1001	-1.80 V
0010	-0.400 V	1010	-2.00 V
0011	-0.600 V	1011	-2.20 V
0100	-0.800 V	1100	-2.40 V
0101	-1.00 V	1101	-2.60 V
0110	-1.20 V	1110	-2.80 V
0111	-1.40 V	1111	-3.00 V

5.) Problem 11.98 (12.74) of the text.

$$\beta = \frac{2\text{k}\Omega}{2\text{k}\Omega + 40\text{k}\Omega} = \frac{1}{21} \quad | \quad A\beta = \frac{10^5}{21} = 4760 \gg 1$$

$$(a) \quad A_V = -\frac{R_2}{R_1} = -\frac{40\text{k}\Omega}{2\text{k}\Omega} = -20 \quad | \quad f_H = \beta f_T = \frac{3 \times 10^6 \text{ Hz}}{21} = 143 \text{ kHz}$$

$$(b) \quad A_V = (-20)^3 = -8000 \text{ (78dB)} \quad | \quad f_{H3} = 0.51 f_H = 72.9 \text{ kHz}$$