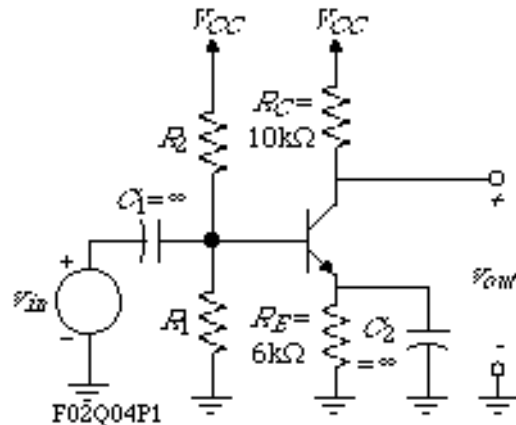


Homework Assignment No. 5 - Solution

1.) An NPN BJT common-emitter inverting amplifier is shown. Assume the parameters of the transistor are $\beta_F = 100$, $V_T = 25\text{mV}$, and $V_A = 100\text{V}$. (a.) If $I_C = 0.5\text{mA}$ and $V_{CE} = 3\text{V}$, find the small signal model parameter values for g_m , r_π , and r_o . (b.) Find an algebraic expression for the small signal voltage gain, v_{out}/v_{in} . (c.) Numerically evaluate the small signal voltage gain, v_{out}/v_{in} .




Solution

(a.) $g_m = \frac{I_C}{V_T} = \frac{0.5\text{mA}}{25\text{mV}} = \underline{20\text{mS}}$

$r_\pi = \beta_F \frac{V_T}{I_C} = \frac{100}{20\text{mS}} = \underline{5\text{k}}$

$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{102}{0.5\text{mA}} = \underline{204\text{k}}$

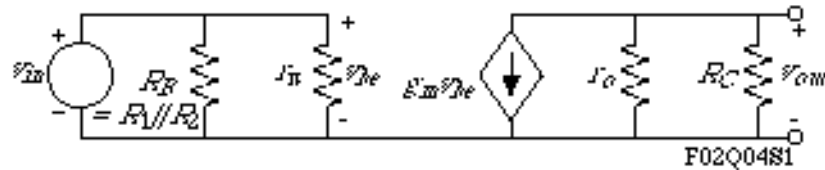(b.) To find the small signal voltage gain, we must first develop a small signal model. This model is given below:



$$\frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_{be}} = -g_m(r_o \parallel R_C)$$

(c.) The numerical value of this gain is

$\frac{v_{out}}{v_{in}} = -20\text{mS}(204\text{k} \parallel 10\text{k}) = -20\text{mS}(9.53\text{k}) = \underline{-190.65 \text{ V/V}}$

2.) Problem 13.102 (13.91) of the text.

$g_m = \sqrt{2 \cdot 500 \frac{\mu\text{A}}{\text{V}^2} (100\mu\text{A})(1 + 0.02(5))} = 332\mu\text{S} \quad | \quad r_o = \frac{50 + 5\text{V}}{100\mu\text{A}} = 550\text{k}$

$A_v = - \frac{6.8\text{M}}{6.8\text{M} + 0.1\text{M}} (332\mu\text{S})(550\text{k} \parallel 50\text{k} \parallel 120\text{k}) = -10.9$

3.) Problem 13.111 (13.100) of the text. [$A_v = -4.60 \text{ V/V}$]

$g_m = \frac{2}{3} \sqrt{1\text{mA}(1\text{mA})[1 + 0.015(9)]} = 710\mu\text{S} \quad | \quad r_o = \frac{1}{0.015} + 9\text{V} = \frac{0.015}{1\text{mA}} = 75.7\text{k}$


$A_v = - \frac{1\text{M}}{1\text{M} + 10\text{k}} (710\mu\text{S})(75.7\text{k} \parallel 7.5\text{k} \parallel 160\text{k}) = -4.60\text{V/V}$

4.) Problem 13.118 (13.108) of the text.

$$R_{in} = R_G = 6.8M \quad | \quad R_{out} = 50k \parallel r_o$$

$$r_o = \frac{(50 + 5)V}{0.1mA} = 550k \quad | \quad R_{out} = 50k \parallel 550k = 45.8k$$

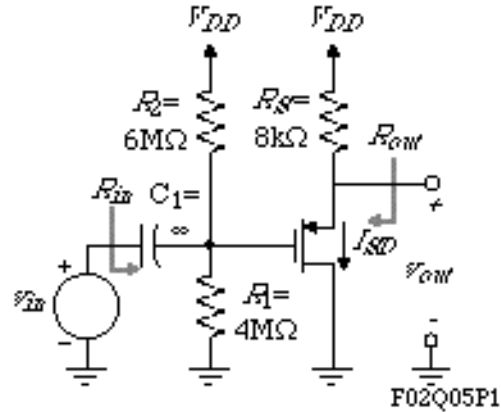
5.) A PMOS common-drain amplifier is shown. Assume the parameters of the transistor are $k_F = 0.5mA/V^2$, $V_{TP} = -1V$, and $\lambda = 0$. (a.) If $I_{SD} = 0.5mA$, find the small signal model parameter values for g_m and r_o . (b.) Find an algebraic expression for the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} . (c.) Numerically evaluate the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} .



Solution

(a.) $g_m = \sqrt{2I_{SD}k_P} = \sqrt{2 \cdot 0.5 \cdot 0.5} \text{ mS} = \underline{0.707\text{mS}}$ and $r_o = \underline{\hspace{2cm}}$

(b.) First we need a small signal model.

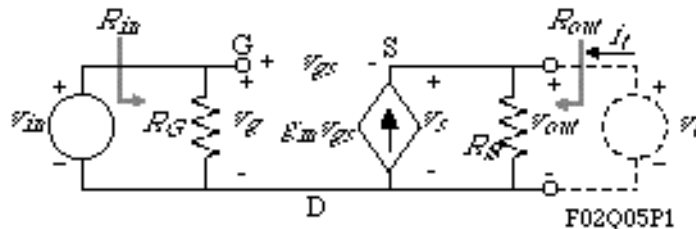

Obviously, $R_{in} = R_G = R_1 \parallel R_2$. For R_{out} we apply the voltage source, v_t , and set $v_{in} = 0$ and solve for v_t/i_t which equivalent to R_{out} .

$$i_t = G_S v_t - g_m v_{gs} = G_S v_t - g_m(v_g - v_s) = G_S v_t - g_m(0 - v_s)$$

$$= G_S v_t + g_m v_s = G_S v_t + g_m v_t = (G_S + g_m) v_t$$

$$R_{out} = \frac{v_t}{i_t} = \frac{1}{G_S + g_m} = \frac{R_S}{1 + g_m R_S} \quad \boxed{R_{out} = \frac{R_S}{1 + g_m R_S}}$$

The output voltage can be expressed as,

$$v_{out} = g_m R_S v_{gs} = g_m R_S (v_g - v_s) = g_m R_S (v_{in} - v_{out})$$

$$v_{out}(1 + g_m R_S) = g_m R_S v_{in} \quad \boxed{\frac{v_{out}}{v_{in}} = \frac{g_m R_S}{1 + g_m R_S}}$$

(c.) $R_{in} = R_G = R_1 \parallel R_2 = \underline{2.4M}$, $R_{out} = \frac{8k}{1 + 0.707 \cdot 8} = \underline{1.2k}$ and $\frac{v_{out}}{v_{in}} = \frac{0.707 \cdot 8}{1 + 0.707 \cdot 8} = \underline{0.85V/V}$