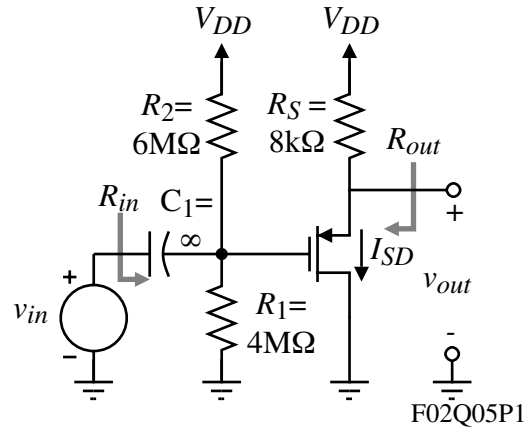



**Homework Assignment No. 6 - Solution**

- 1.) A PMOS common-drain amplifier is shown. Assume the parameters of the transistor are  $k_F = 0.5\text{mA/V}^2$ ,  $V_{TP} = -1\text{V}$ , and  $\lambda = 0$ . (a.) If  $I_{SD} = 0.5\text{mA}$ , find the small signal model parameter values for  $g_m$  and  $r_o$ . (b.) Find an algebraic expression for the small signal input resistance,  $R_{in}$ , the output resistance,  $R_{out}$ , and the voltage gain,  $v_{out}/v_{in}$ . (c.) Numerically evaluate the small signal input resistance,  $R_{in}$ , the output resistance,  $R_{out}$ , and the voltage gain,  $v_{out}/v_{in}$ .

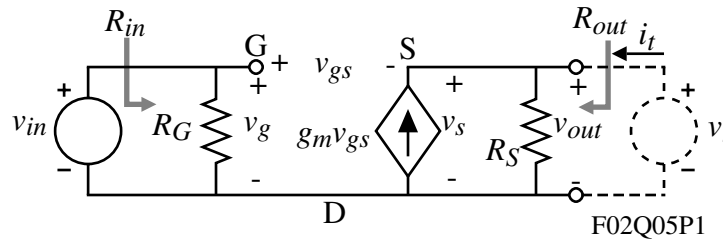**Solution**

(a.)  $g_m = \sqrt{2I_{SD}k_P} = \sqrt{2 \cdot 0.5 \cdot 0.5} \text{ mS} = \underline{0.707\text{mS}}$  and  $r_o = \underline{\underline{\infty}}$

- (b.) First we need a small signal model.



Obviously,  $R_{in} = R_G = R_1 \parallel R_2$ . For  $R_{out}$  we apply the voltage source,  $v_t$ , and set  $v_{in} = 0$  and solve for  $v_t/i_t$  which equivalent to  $R_{out}$ .

$$\begin{aligned} \therefore i_t &= G_S v_t - g_m v_{gs} = G_S v_t - g_m (v_g - v_s) = G_S v_t - g_m (0 - v_s) \\ &= G_S v_t + g_m v_s = G_S v_t + g_m v_t = (G_S + g_m) v_t \end{aligned}$$

$$\therefore R_{out} = \frac{v_t}{i_t} = \frac{1}{G_S + g_m} = \frac{R_S}{1 + g_m R_S} \rightarrow \boxed{R_{out} = \frac{R_S}{1 + g_m R_S}}$$

The output voltage can be expressed as,

$$v_{out} = g_m R_S v_{gs} = g_m R_S (v_g - v_s) = g_m R_S (v_{in} - v_{out})$$

$$\therefore v_{out}(1 + g_m R_S) = g_m R_S v_{in} \rightarrow \boxed{\frac{v_{out}}{v_{in}} = \frac{g_m R_S}{1 + g_m R_S}}$$

(c.)  $R_{in} = R_G = R_1 \parallel R_2 = \underline{2.4\text{M}\Omega}$ ,  $R_{out} = \frac{8\text{k}\Omega}{1 + 0.707 \cdot 8} = \underline{1.2\text{k}\Omega}$  and  $\frac{v_{out}}{v_{in}} = \frac{0.707 \cdot 8}{1 + 0.707 \cdot 8} = \underline{0.85\text{V/V}}$

2.) Problem 14.16 (no equivalent problem in first ed.) of the text.

**14.16**

$$V_{EQ} = 12 \frac{62k\Omega}{20k\Omega + 62k\Omega} = 9.07V \quad | \quad R_{EQ} = 20k\Omega \parallel 62k\Omega = 15.1k\Omega$$

$$I_B = \frac{(12 - 0.7 - 9.07)V}{15.1k\Omega + (75 + 1)3.9k\Omega} = 7.16\mu A \quad | \quad I_C = 537 \mu A \quad | \quad V_{EC} = 12 - 3900I_E - 8200I_C = 5.47 V$$

$$\text{Active region is correct.} \quad | \quad r_\pi = \frac{75(0.025V)}{537\mu A} = 3.49k\Omega \quad | \quad V_A \text{ not specified, choose } r_o = \infty$$

$$R_{in} = 15.1k\Omega \parallel 3.49k\Omega = 2.83 k\Omega \quad | \quad R_{out} = r_o \parallel 8.2k\Omega = 8.2 k\Omega \quad | \quad g_m = 40I_C = 21.5 mS$$

$$R_L = r_o \parallel 8.2k\Omega \parallel 100k\Omega = 8.2k\Omega \parallel 100k\Omega = 7.58k\Omega$$

$$A_v = -g_m R_L \left( \frac{R_{in}}{R_I + R_{in}} \right) = -(21.5mS)(7.58k\Omega) \left( \frac{2.83k\Omega}{1k\Omega + 2.83k\Omega} \right) = -120$$

$$A_i = \frac{R_B}{R_B + r_\pi} (-\beta_o) \frac{R_{out}}{R_{out} + R_3} = \frac{15.1k\Omega}{15.1k\Omega + 3.49k\Omega} (-75) \frac{8.2k\Omega}{8.2k\Omega + 100k\Omega} = -4.62$$

$$v_{be} = v_i \frac{R_{in}}{R_I + R_{in}} = v_i \frac{2.83k\Omega}{1k\Omega + 2.83k\Omega} = 0.739v_i \quad | \quad v_i = \frac{5.00mV}{0.739} = 6.76 mV$$

$$A_v \cong -10V_{CC} = -10(12) = -120. \quad | \quad \text{The voltage gain is identical to the rule - of - thumb estimate.}$$

3.) Problem 14.19 (14.15) of the text.

**14.19**

$$V_{GS} = -(11k\Omega)I_D = -(11k\Omega)(20mA) \left( 1 - \frac{V_{GS}}{-4} \right)^2 \rightarrow V_{GS} = -3.50V, \quad I_D = -\frac{V_{GS}}{11k\Omega} = 318 \mu A$$

$$V_{DS} = 20 - I_D(11k\Omega + 39k\Omega) = 4.10V \quad | \quad \text{Active region operation is correct.}$$

$$g_m = \frac{2}{|-4|} \sqrt{20mA(318\mu A)} = 1.26mS \quad | \quad \text{Assume } \lambda = 0, r_o = \infty. \quad | \quad R_L = 39k\Omega \parallel 500k\Omega = 36.2k\Omega$$

$$R_{in} = R_G = 1.00 M\Omega \quad | \quad R_{out} = 39k\Omega$$

$$A_v = -\frac{g_m R_L}{1 + g_m R_S} \left( \frac{R_{in}}{R_I + R_{in}} \right) = -\frac{1.26mS(36.2k\Omega)}{1 + 1.26mS(11k\Omega)} \left( \frac{1M\Omega}{500k\Omega + 1M\Omega} \right) = -3.07$$

$$A_i = -R_G \left( \frac{g_m}{1 + g_m R_S} \right) \left( \frac{R_D}{R_D + R_3} \right) = -10^6 \left[ \frac{1.26mS}{1 + 1.26mS(11k\Omega)} \right] \left( \frac{39k\Omega}{39k\Omega + 500k\Omega} \right) = -6.14$$

$$v_{gs} = \frac{R_{in}}{R_I + R_{in}} v_i = 1.00v_i \quad | \quad V_{GS} - V_P = -3.5 - (-4) = 0.500V$$

$$v_{gs} \leq 0.2(V_{GS} - V_P)(1 + g_m R_S) \quad | \quad v_i \leq 0.2(0.5)[1 + 1.26mS(11k\Omega)] = 1.49 V$$

4.) Problem 14.27 (14.21) of the text.

**14.27**

$$V_{EQ} = 18 \frac{51k\Omega}{51k\Omega + 100k\Omega} = 6.08V \quad | \quad R_{EQ} = 51k\Omega || 100k\Omega = 33.8k\Omega$$

$$I_B = \frac{(6.08 - 0.7 + 18)V}{33.8k\Omega + (126)(4.7k\Omega)} = 37.3\mu A \quad | \quad I_C = 4.67mA \quad | \quad V_{CE} = 36 - 2000I_C - 4700I_E = 4.54V$$

$$\text{Active region is correct.} \quad | \quad r_\pi = \frac{125(0.025V)}{4.67mA} = 669\Omega \quad | \quad r_o = \frac{(50 + 4.54)V}{4.67mA} = 11.7k\Omega$$

$$R_B = R_1 || R_2 = 51k\Omega || 100k\Omega = 33.8k\Omega \quad | \quad R_L = R_3 || R_E || r_o = 24k\Omega || 4.7k\Omega || 11.7k\Omega = 2.94k\Omega$$

$$R_{in} = R_B || [r_\pi + (\beta_o + 1)R_L] = 33.8k\Omega || [669\Omega + (126)2.94k\Omega] = 31.0k\Omega$$

$$A_v = + \frac{(\beta_o + 1)R_L}{r_\pi + (\beta_o + 1)R_L} \left( \frac{R_{in}}{R_I + R_{in}} \right) = \frac{126(2.94k\Omega)}{0.669k\Omega + 126(2.94k\Omega)} \left( \frac{31.0k\Omega}{500\Omega + 31.0k\Omega} \right) = 0.982$$

$$v_{be} = v_i \left( \frac{R_{in}}{R_I + R_{in}} \right) \left( \frac{r_\pi}{r_\pi + (\beta_o + 1)R_L} \right) = \left( \frac{31.0k\Omega}{500\Omega + 31.0k\Omega} \right) \left[ \frac{0.669k\Omega}{0.669k\Omega + 126(2.94k\Omega)} \right] = 1.77 \times 10^{-3} v_i$$

$$v_i \leq \frac{0.005V}{1.77 \times 10^{-3}} = 2.82V \quad | \quad R_{out} = R_E || \frac{(R_B || R_I) + r_\pi}{\beta_o + 1} = 4.7k\Omega || \frac{(33.8k\Omega || 500\Omega) + 669\Omega}{126} = 9.22\Omega$$

5.) Problem 14.28 (14.23) of the text

**14.28**

$$V_{GS} = 5V \quad | \quad I_D = \frac{4 \times 10^{-4}}{2} (5 - 1)^2 = 3.2mA \quad | \quad V_{DS} = 5 - (-5) = 10V \quad - \text{Pinchoff region}$$

$$\text{operation is correct.} \quad | \quad g_m = \sqrt{2(4 \times 10^{-4})(3.2mA)[1 + 0.02(10)]} = 1.75mS$$

$$r_o = \frac{1}{0.02} + 10 \frac{V}{3.2mA} = 18.8k\Omega \quad - \text{Cannot neglect!} \quad | \quad R_L = 18.8k\Omega || 100k\Omega = 15.8k\Omega$$

$$R_{in} = R_G = 1M\Omega \quad | \quad R_{out} = \frac{1}{g_m} || r_o = 555\Omega$$

$$A_v = + \frac{R_{in}}{R_I + R_{in}} \left( \frac{g_m R_L}{1 + g_m R_L} \right) = + \frac{1M\Omega}{10k\Omega + 1M\Omega} \left( \frac{1.75mS(15.8k\Omega)}{1 + 1.75mS(15.8k\Omega)} \right) = 0.956$$

$$v_{gs} = v_i \left( \frac{R_{in}}{R_I + R_{in}} \right) \left( \frac{1}{1 + g_m R_L} \right) = v_i \left( \frac{10^6\Omega}{10^4\Omega + 10^6\Omega} \right) \left[ \frac{1}{1 + 1.75mS(15.8k\Omega)} \right] = 0.0346 v_i$$

$$v_i \leq \frac{0.2(5 - 1)}{0.0346} = 23.2V \quad \text{But, } v_{DS} \text{ must exceed } v_{GS} - V_{TN} \cong V_{GS} - V_{TN} = 4V \text{ for pinchoff.}$$

$$V_{DS} = 10 - v_o = 10 - 0.956v_i \geq 4 \rightarrow v_i \leq 6.28V \quad - \text{Limited by the Q-point voltages}$$