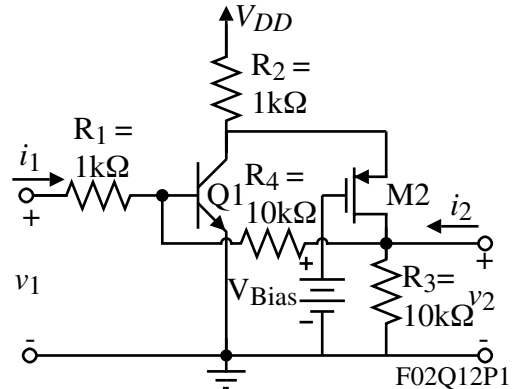


**Homework Assignment No. 12**


Due on Monday, April 5, 2004

- 1.) Problem 18.23 (18.16) of the text.
- 2.) A shunt-shunt feedback amplifier is shown. Use the methods of feedback analysis to find the numerical values of  $v_2/v_1$ ,  $v_1/i_1$ , and  $v_2/i_2$ . For Q1, assume that  $h_{fe} = 100$ ,  $g_m = 50\text{mS}$  and  $r_o = \infty$ . For M2, assume that  $g_m = 1\text{mS}$  and  $r_{ds} = \infty$ .




- 3.) For each of the MOSFET amplifiers shown below, show how to connect a single resistor from the output to the input that achieves a series-shunt, series-series, shunt-shunt and shunt-series negative feedback amplifier. For each of the four configurations, identify on the schematic the correct variables (voltage or current) for  $x_s$ ,  $x_f$ ,  $x_i$ , and  $x_o$ . The outputs should be at the drain or source of M3.


Series-Shunt

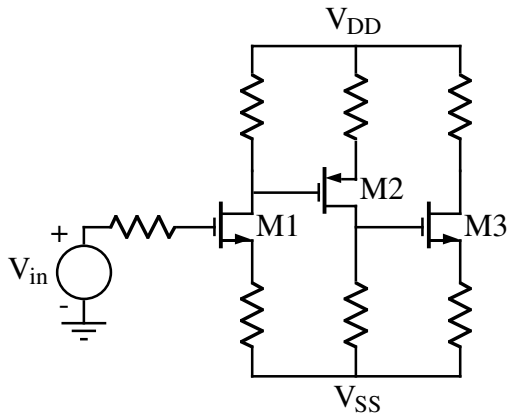


Shunt-Series

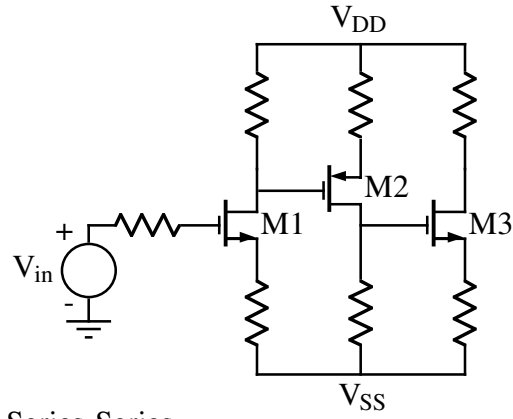

Shunt-Shunt

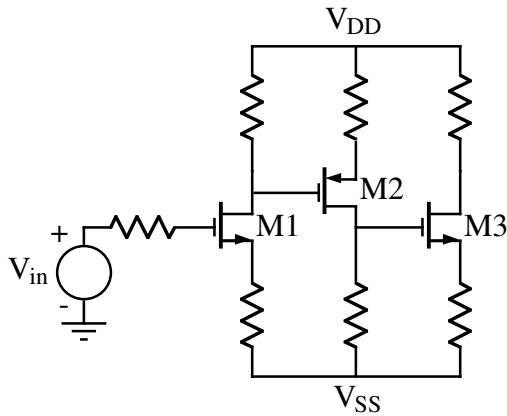

Series-Series

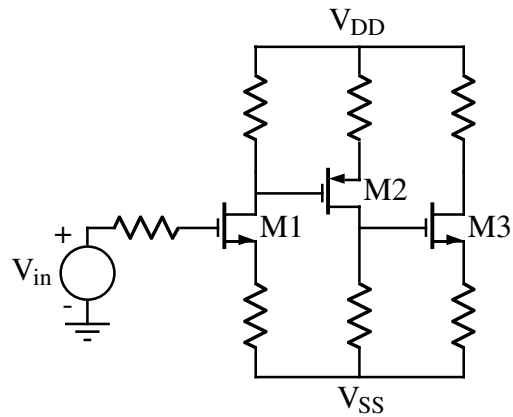

- 4.) Problem 18.29 (18.22) of the text.

**Please note that there are numerous feedback problems you can work (answers only are provided) on the class website.**

