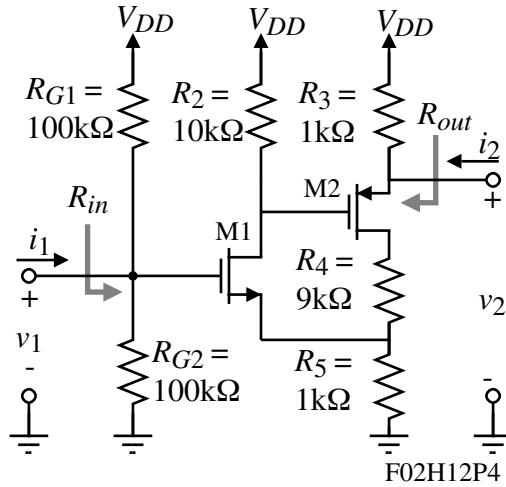


Homework Assignment No. 13

Due on Monday, April 12, 2004


1.) Use the method of feedback analysis to find the numerical values of v_2/v_1 , $R_{in} = v_1/i_1$, and $R_{out} = v_2/i_2$. Assume that all transistors are matched and that $g_{m1} = g_{m2} = 1\text{mS}$. Neglect r_{ds} of the transistors.



Ans. [$v_2/v_1 = -0.714\text{V/V}$, $v_1/i_1 = 50\text{k}\Omega$, and $v_2/i_2 = 857\Omega$]

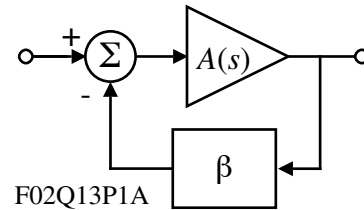2.) The amplifier in the feedback circuit shown has a transfer function of

$$A(s) = \frac{100}{\frac{s}{10^5} + 1}$$



What value of β will increase the upper -3dB frequency by a factor of 10 for the closed loop gain? What is the closed loop, low frequency gain?

Problems in () correspond to the first edition.

- 3.) Problem 18.40 (18.35) of the text.
- 4.) Problem 18.59 (18.32 there is some difference between 1st and 2nd edition) of the text.
- 5.) Problem 18.62 (18.30) of the text.