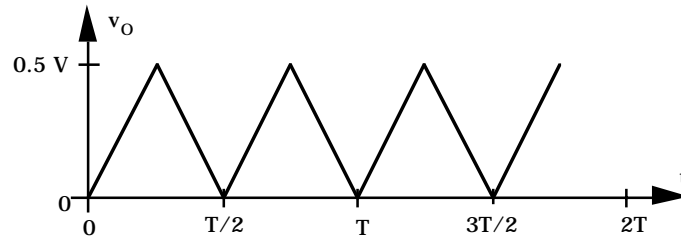


**Homework Assignment No. 15**

1.) Problem 12.61 (12.122) of the text.

For  $R_3 = R_2$ ,

2.) Problem 12.67 (12.128) of the text.

$$\text{For } V_o = 4.3 + 0.6 = 4.9V : V_+ = 4.9 \frac{4.3k\Omega}{4.3k\Omega + 39k\Omega} = 0.487 V$$

$$\text{For } V_o = -4.3 - 0.6 = -4.9V : V_+ = -4.9 \frac{4.3k\Omega}{4.3k\Omega + 39k\Omega} = -0.487 V$$

$$V_N = 0.487 - (-0.487) = 0.974 V$$

3.) Problem 12.69 (12.130) of the text.

$$\text{For } v_o = +12V : V_+ = 6 \frac{24k\Omega}{3.4k\Omega + 24k\Omega} + 12 \frac{3.4k\Omega}{3.4k\Omega + 24k\Omega} = 6.74 V$$

$$\text{For } v_o = 0V : V_+ = 6 \frac{24k\Omega}{3.4k\Omega + 24k\Omega} = 5.26 V$$

$$v(t) = V_F - (V_F - V_I) \exp\left(-\frac{t}{RC}\right)$$

$$6.74 = 12 - (12 - 5.26) \exp\left(-\frac{T_1}{RC}\right) \rightarrow T_1 = 6200(3.3 \times 10^{-8}) \ln \frac{6.74}{5.26} = 50.7 \mu s$$


$$5.26 = 0 - (0 - 6.74) \exp\left(-\frac{T_2}{RC}\right) \rightarrow T_2 = 6200(3.3 \times 10^{-8}) \ln \frac{6.74}{5.26} = 50.7 \mu s$$

$$f = \frac{1}{50.7 \mu s + 50.7 \mu s} = 9.86 \text{ kHz}$$

4.) Problem 12.70 (12.131) of the text.

$f = 0$ . The circuit does not oscillate.  $V_o = 0$  is a stable state.

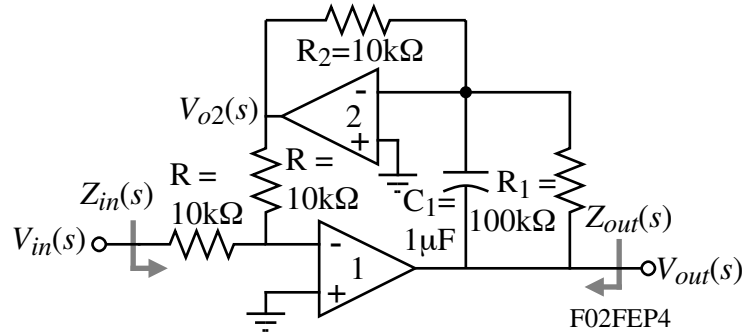5.) If the op amps shown are ideal (infinite voltage gain, infinite differential input resistance, and zero output resistance) find the voltage transfer function,  $V_{out}(s)/V_{in}(s)$ , the input impedance,  $Z_{in}(s)$ , and the output impedance,  $Z_{out}(s)$ . Sketch an asymptotic plot for the magnitude and phase shift of the voltage transfer function,  $V_{out}(j\omega)/V_{in}(j\omega)$  as a function of  $\log_{10}\omega$ .



Solution

$V_{o2}(s)$  can be written as  $V_{o2}(s) = -\frac{R_2}{Z_1}v_{out}(s)$ . Thus, the currents flowing toward the

inverting terminal of the 1st op amp are,  $\frac{V_{in}(s)}{R} + \frac{V_{o2}(s)}{R} = \frac{V_{in}(s)}{R} - \frac{R_2}{Z_1(s)} \frac{V_{out}(s)}{R} = 0$

$$\therefore \frac{V_{out}(s)}{V_{in}(s)} = \frac{Z_1(s)}{R_2} = \frac{1}{R_2} \frac{R_1(1/sC_1)}{R_1+(1/sC_1)} = \frac{R_1}{R_2} \frac{1}{sR_1C_1+1} \quad \boxed{\frac{V_{out}(s)}{V_{in}(s)} = \frac{R_1}{R_2} \frac{1}{sR_1C_1+1}}$$

By inspection,  $\boxed{Z_{in}(s) = R = 10k\Omega \text{ and } Z_{out}(s) = 0}$

For the Bode plot we want to plot the magnitude and phase of  $\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{10}{1+j\omega/10}$ .

