


Homework Assignment No. 2 - Solutions**Problem 10.20 (11.16)**

$$g_{11} = \left. \frac{\mathbf{i}_1}{\mathbf{v}_1} \right|_{\mathbf{i}_2=0} : \mathbf{v}_1 = 10^4 \mathbf{i}_1 + 101 \mathbf{i}_1 (240 \text{ k}\Omega) \rightarrow g_{11} = 4.124 \times 10^{-8} \text{ S} = 4.12 \times 10^{-8} \text{ S}$$

$$g_{12} = \left. \frac{\mathbf{i}_1}{\mathbf{i}_2} \right|_{\mathbf{v}_1=0} : \mathbf{i}_1 = -\frac{240 \text{ k}\Omega}{240 \text{ k}\Omega + 10 \text{ k}\Omega} (\mathbf{i}_2 + 100 \mathbf{i}_1) \rightarrow g_{12} = -9.90 \times 10^{-3}$$

$$g_{21} = \left. \frac{\mathbf{v}_2}{\mathbf{v}_1} \right|_{\mathbf{i}_2=0} : \mathbf{v}_2 = 101 \mathbf{i}_1 (240 \text{ k}\Omega) \mid \mathbf{i}_1 = g_{11} \mathbf{v}_1 \rightarrow g_{21} = 1.00$$

$$g_{22} = \left. \frac{\mathbf{v}_2}{\mathbf{i}_2} \right|_{\mathbf{v}_1=0} : \mathbf{i}_2 = \frac{\mathbf{v}_2}{240 \text{ k}\Omega} + \frac{\mathbf{v}_2}{10 \text{ k}\Omega} + 100 \frac{\mathbf{v}_2}{10 \text{ k}\Omega} \rightarrow g_{22} = 99.0 \text{ }\Omega$$

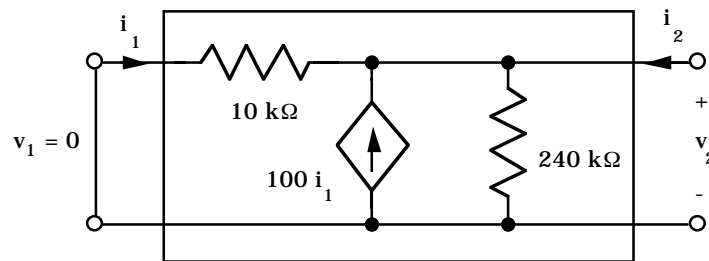**Problem 10.48 (11.34)**

$$V_O = V_S \frac{R_{IN}}{R_{IN} + R_S} A \frac{R_{IN}}{R_{IN} + R_{OUT}} A \frac{R_L}{R_L + R_{OUT}}$$

$$A_V = \frac{5000}{5000 + 1000} (-1000) \frac{5000}{5000 + 250} (-1000) \frac{100}{100 + 250} = +2.27 \times 10^5$$

$$A_I = \frac{I_O}{I_S} = \frac{2.27 \times 10^5 V_S}{100} \frac{1}{\frac{V_S}{6000}} = +1.36 \times 10^7$$

$$A_P = \frac{2.27 \times 10^5 V_S (+1.36 \times 10^7 I_S)}{V_S I_S} = +3.09 \times 10^{12}$$

Problem 10.57 (11.37)


$$A_V = \frac{2\pi \times 10^7 \text{ s}}{(s + 20\pi)(s + 2\pi \times 10^4)} = \frac{1000 \text{ s}}{(s + 20\pi) \left(1 + \frac{s}{2\pi \times 10^4}\right)} \mid A_{\text{mid}} = +1000 = 60 \text{ dB}$$

$$f_L = \frac{20\pi}{2\pi} = 10 \text{ Hz} \mid f_H = \frac{2\pi \times 10^4}{2\pi} = 10 \text{ kHz} \mid \text{BW} = 10 \text{ kHz} - 10 \text{ Hz} = 9.99 \text{ kHz}$$

Bandpass Amplifier

Problem 10.63 (11.43)

Using MATLAB: `n=[2e7*pi 0]; d=[1 (20*pi+2e4*pi) 40e4*pi^2]; bode(n,d)`

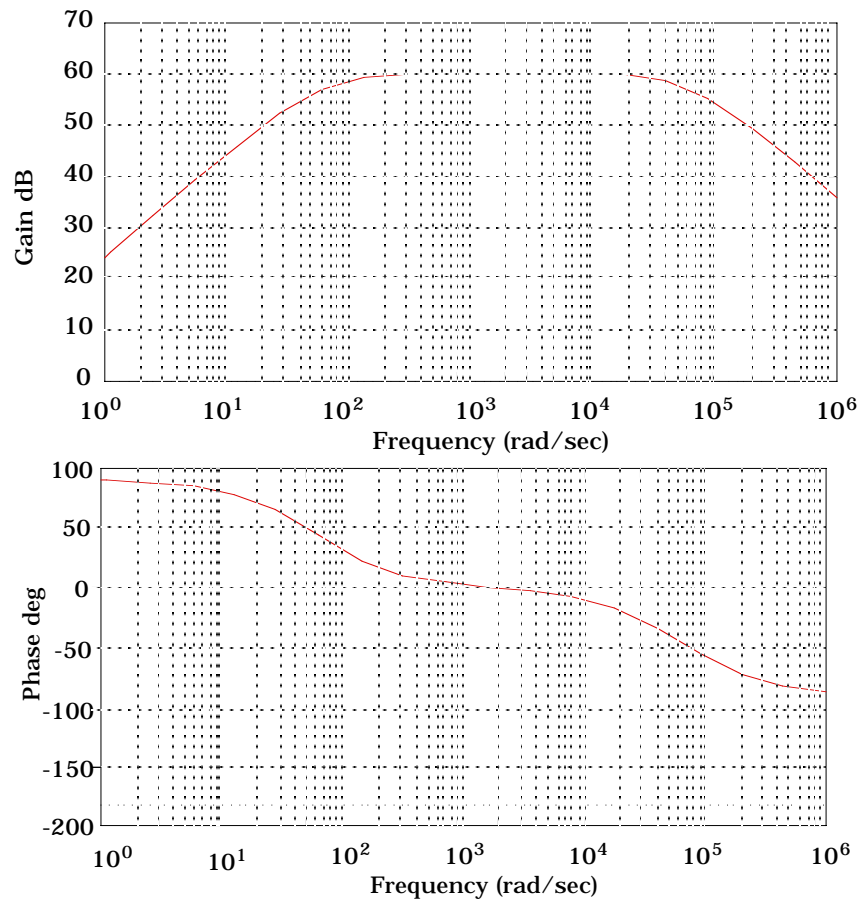
Problem 10.75 (11.55)

$$(a) A_{\text{mid}} = +10^{\frac{20}{20}} = +10 \quad | \quad A_V = \frac{10}{1 + \frac{s}{2\pi \times (5 \times 10^6)}} = \frac{10}{1 + \frac{s}{10^7 \pi}} = \frac{10^8 \pi}{s + 10^7 \pi}$$

$$(b) A_{\text{mid}} = -10^{\frac{20}{20}} = -10 \quad | \quad A_V = -\frac{10^8 \pi}{s + 10^7 \pi}$$

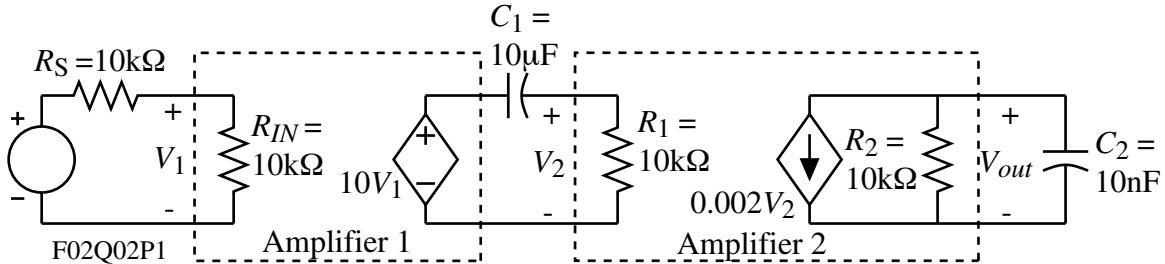Problem 6

a.) Find the transfer function, $V_{out}(s)/V_S(s)$, of the circuit shown and identify the location of the poles and zeros. What is the gain in the region where the transfer function is independent of frequency?



$$\frac{V_{out}(s)}{V_S(s)} = \left(\frac{V_{out}}{V_2}\right) \left(\frac{V_2}{V_1}\right) \left(\frac{V_1}{V_{in}}\right) = \left(\frac{-G(R_2/sC_2)}{R_2+1/sC_2}\right) \left(\frac{10R_1}{R_1+1/sC_1}\right) \left(\frac{R_{IN}}{R_S + R_{IN}}\right)$$

where $G = 0.002 \text{ A/V}$. Rearranging gives,

$$\frac{V_{out}(s)}{V_S(s)} = \left(\frac{R_{IN}}{R_S + R_{IN}}\right) \left(\frac{10sR_1C_1}{sR_1C_1+1}\right) \left(\frac{-GR_2}{sR_2C_2+1}\right) = \left(\frac{10(-20)}{2}\right) \left(\frac{\frac{s}{10}}{\frac{s}{10}+1}\right) \left(\frac{1}{\frac{s}{10^4}+1}\right)$$

Poles are at -10 rads/sec. and -10^4 rads/sec. and the zeros are at 0 and ∞ .

The gain in the frequency independent range (midband) is $\underline{100V/V.}$

b.) Sketch the asymptotic (straight-line) plot for the magnitude and phase of transfer function shown. Use the same plot for phase shift. Label the phase shift on the right side of the plot.

$$A(s) = \frac{-10s}{(s+1)(s+100)} \rightarrow A(j\omega) = \left(\frac{-10}{100}\right) \left(\frac{\frac{j\omega}{1}}{\left(1+\frac{j\omega}{1}\right)\left(1+\frac{j\omega}{100}\right)}\right)$$

The asymptotic plot of the magnitude and phase of the above transfer function is shown:

