

Topics -

- Small-signal model of the diode
- Diode example
- MOSFET - Physical
- MOSFET Large signal model
- MOSFET Example 1 and 2

More Office Hours:

Richard Tarbell



10-12 MW

1-2:30 TTh

Prof. Moad's help office
area (4th floor)
Rm. 448

Small-signal Model

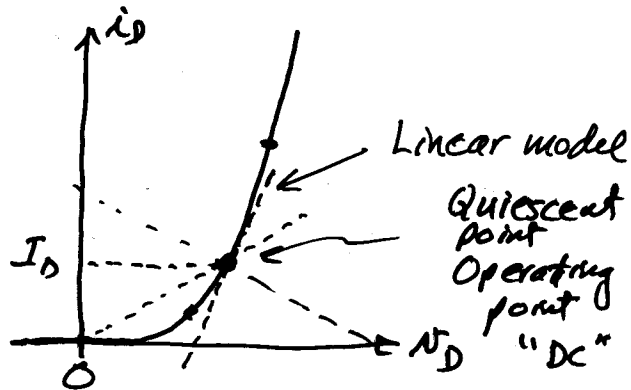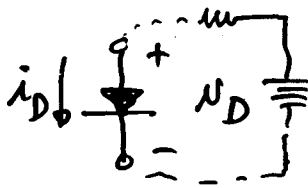The s.s. model is a LINEAR model of a nonlinear device



$$\frac{\partial i_D}{\partial v_D} = g_d = \frac{1}{r_d}$$

$$i_D \approx I_s \exp\left(\frac{v_D}{nV_T}\right)$$


$$\frac{\partial i_D}{\partial v_D} = \frac{I_s}{nV_T} \exp\left(\frac{v_D}{nV_T}\right) = \frac{I_D}{nV_T} = g_d = \frac{1}{r_d}$$



Diode Example


- a.) Find the dc operating point if $V_T = 0.025V$, $n=1$ and $I_s = 100fA$.

$V_1 = 20V$

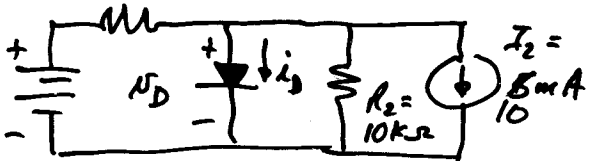



- b.) If the 20V voltage source has a peak-peak sinusoidal signal of 10mV placed in series with it, find the p-p value of v_D and i_D of the diode.

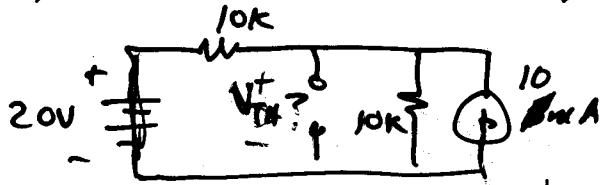a.) Find the Thevenin eq. seen from diode



$$V_{TH} = 10V - 9mA \cdot 5K = 5V$$

$$R_{TH} = 5K$$


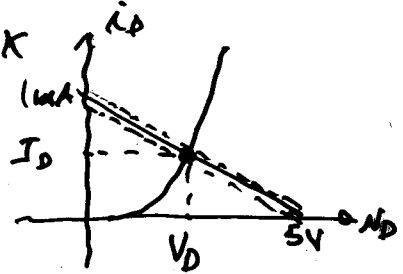
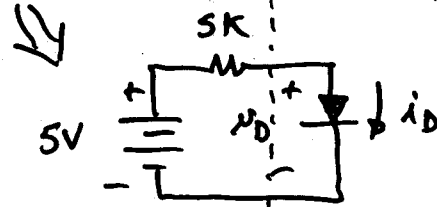


Guess at V_D	$i_D = \frac{5V - V_D}{5K}$	$i_D = I_S \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right]$
0.6	0.88mA	2.331mA
0.57	0.886mA	0.798mA
⋮	⋮	⋮
0.5726	0.88548mA	0.88528mA

∴ $V_D = 0.573V \rightarrow I_D = 0.885mA$


b.) S.S. model of diode.
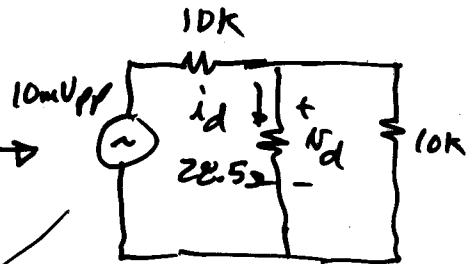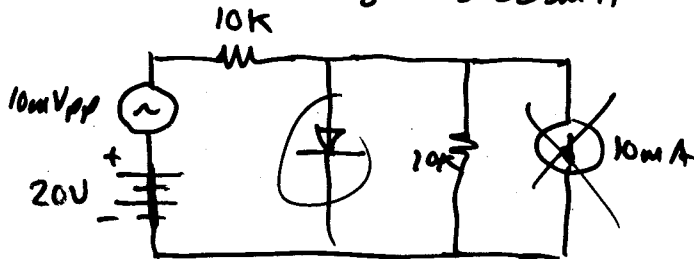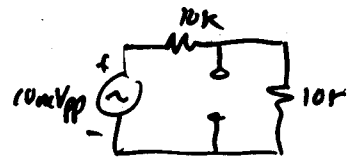
$$r_d = \frac{V_T}{I_D} = \frac{25mV}{0.885mA} = 28.5\Omega$$



Large-signal ckt.

Small-signal ckt.

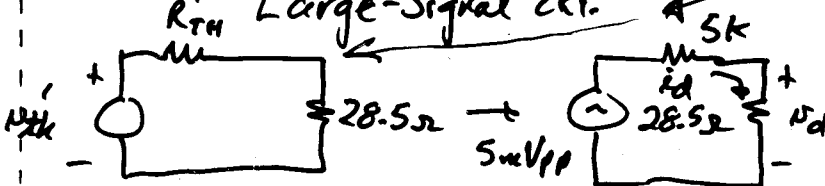


$$V_d = \frac{28.5}{5028.5} \times 5mV_{pp}$$

$$i_d = \frac{5mV_{pp}}{5028.5}$$

MOSFET

Physical -

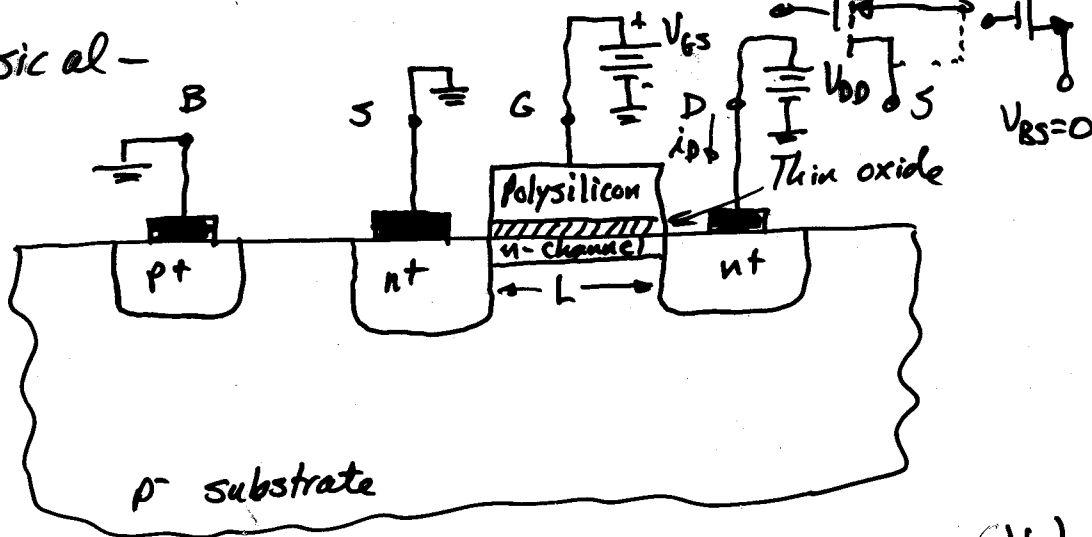


Enhancement - Threshold is > 0 for NMOS (V_t)
 Depletion - Threshold is < 0 for NMOS (V_t)

Model -


1.) Linear region - $i_D = k_n' \frac{W}{L} (V_{GS} - V_{TN} - \frac{V_{DS}}{2}) V_{DS} (1 + \lambda V_{DS})$
 $V_{GS} - V_{TN} < V_{DS}$

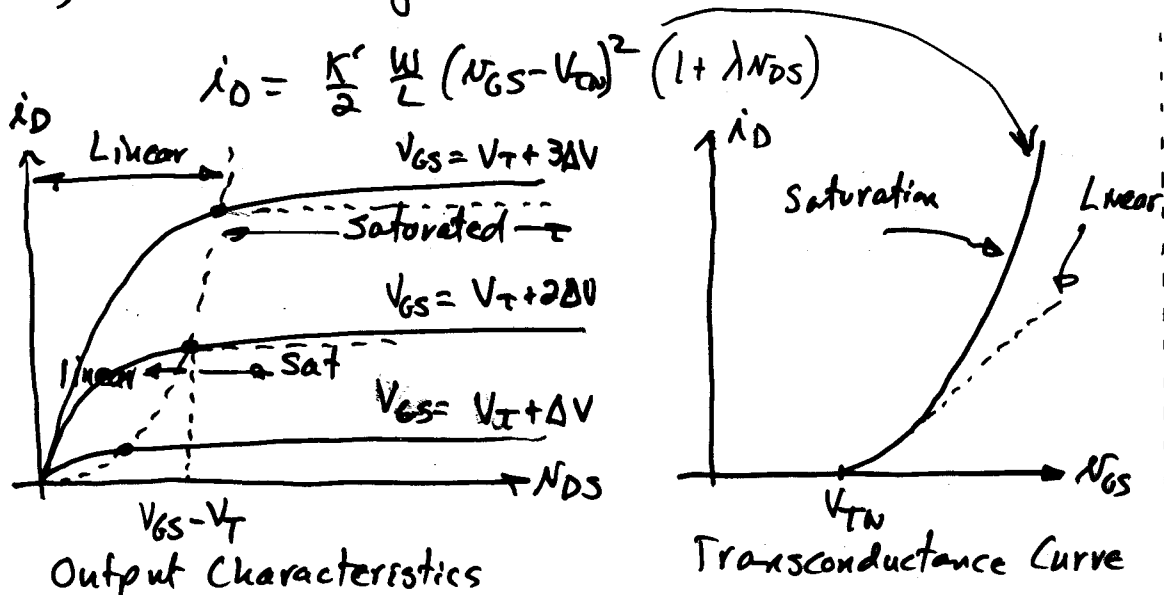2.) Saturated region ($V_{GS} - V_{TN} > V_{DS}$)




MOSFET Example

Find the dc operating point of the NMOS transistor shown assuming that $K_N' = 25 \mu\text{A/V}^2$, $\frac{W}{L} = 10$, $V_{TN} = 1\text{V}$ and $\lambda = 0$.

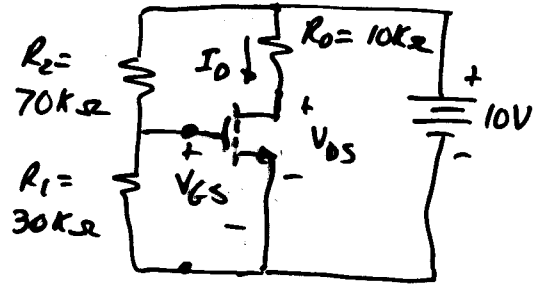Solution

Thev. eq. circuit from G-S.

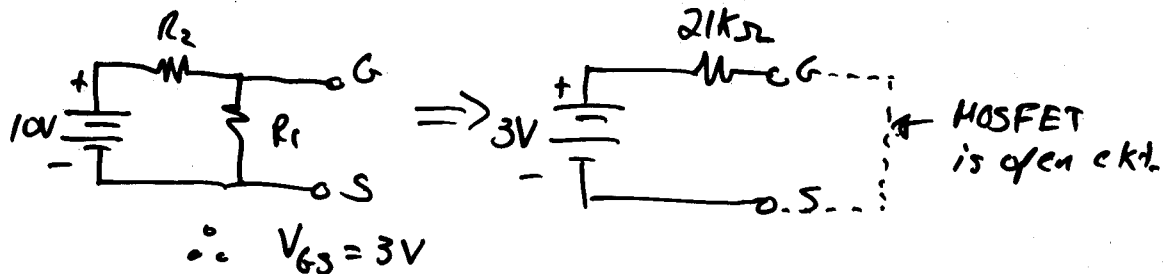

Assume the MOSFET is sat.

$$I_D = \frac{K_N'}{2} \frac{W}{L} (V_{GS} - V_{TN})^2 = 500 \mu\text{A} \Rightarrow V_{DS} = 5\text{V}$$

Check to make sure $V_{DS} > V_{GS} - V_T$ OKAY