

Topics

- Second MOSFET Example
- Bipolar Junction Transistors
- Approximate BJT Large Signal Models
- BJT Example 1
- BJT Example 2

TA Information:

Shakeel Qureshi

10-11am TTh

Room 292 Van Leer


(in front of my office)

Remember: Quiz #1 a week from now.


Second MOSFET Example

Find operating point if $R_2 = 100k$
 $K_N' = 25 \mu A/V^2$, $\frac{W}{L} = 10$, $V_{TN} = 1V$,
 and $\lambda = 0$.

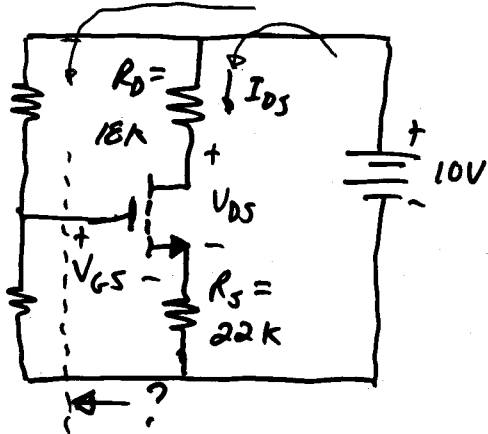
$I_D = \frac{1}{2} \frac{K_N'}{W} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$ $R_1 = 150k$



Solution

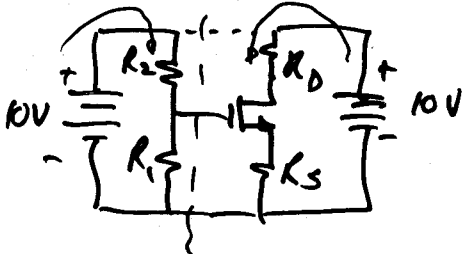

Thevenin eq. ckt:

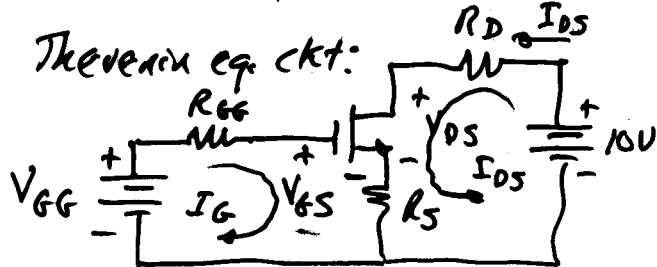

$V_{GG} = 10V \times \frac{150k}{250k} = 6V$

$R_{GG} = R_1 || R_2 = 60k$

$K_N = K_N' \frac{W}{L}$

G-S loop eq: $V_{GG} = V_{GS} + I_{DS} R_S$

Large Sig. Model for sat.: $I_{DS} = \frac{K_N}{2} (V_{GS} - V_T)^2$


Combine eqs. $V_{GG} = V_{GS} + \frac{K_N R_S}{2} (V_{GS} - V_T)^2$

$V_{GS}^2 - 1.636 V_{GS} - 1.182 = 0$



$\Rightarrow V_{GS} = 0.8182 \pm 1.361 = \underline{2.179V}$

$I_{DS} = 174 \mu A \rightarrow V_{DS} = 10 - (174 \mu A) 18k$

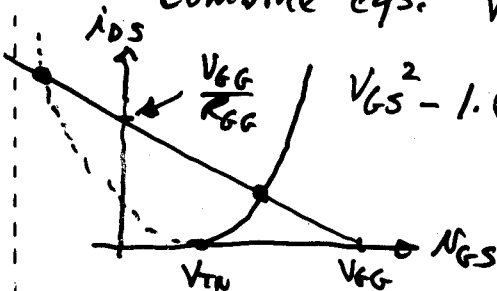$V_{DS} = 6.868V$ $V_{GS} - V_T = 1.179V$



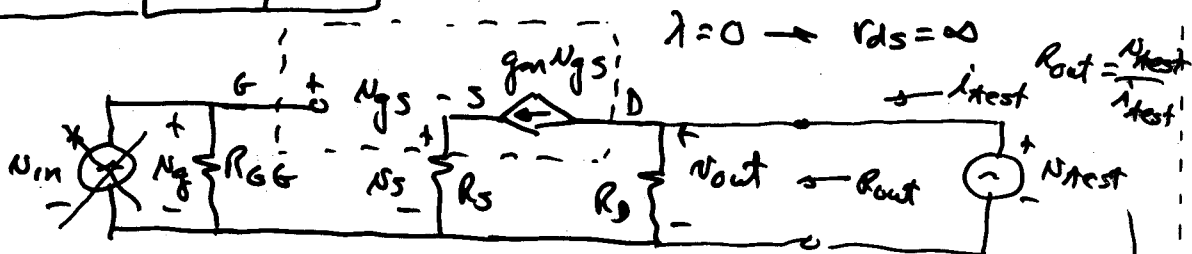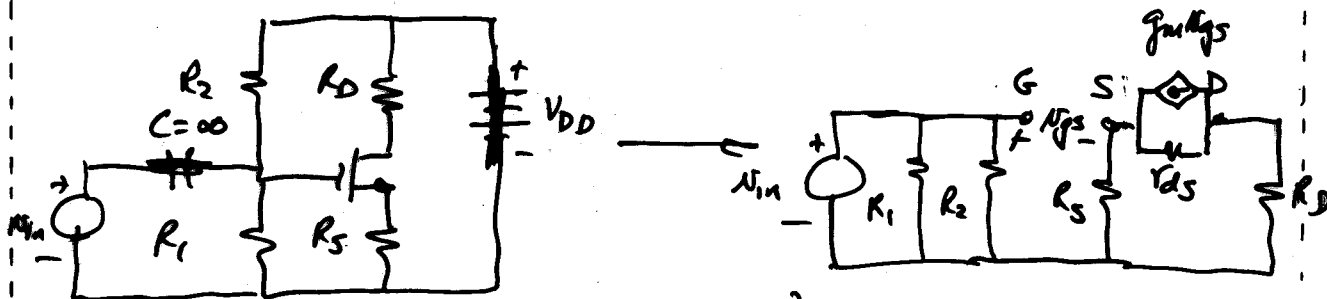Small-signal MOSFET Model of Previous Example




$$\frac{N_{out}}{N_{in}} = ? \quad \frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{N_{gs}} \right) \left(\frac{N_{gs}}{N_{in}} \right) = (-gmRD) \left(\frac{1}{1+gmRS} \right)$$

$$N_{gs} = N_g - N_s = N_{in} - gmRS N_{gs} \rightarrow N_{gs}(1+gmRS) = N_{in}$$

$$R_{out} = \frac{N_{test}}{i_{test}} \quad N_{in} = 0$$

MOSFET

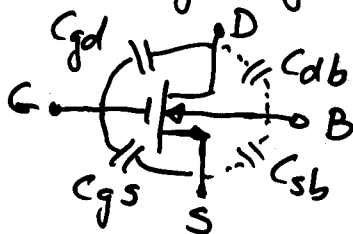Capacitances - $C_{gs}, C_{gd}, C_{db}, C_{sb}$ $\rightarrow 0$ if $V_{SB} = 0$



Linear :
 $N_{DS} < N_{GS} - V_T$

$$C_{gs} = C_{OL}W + 0.5C_{ox}WL, \quad C_{gd} = C_{OL}W + 0.5C_{ox}WL, \quad C_{db} = 0$$

Saturation:
 $N_{DS} > N_{GS} - V_T$

$$C_{gs} = C_{OL}W + \frac{2}{3}C_{ox}WL, \quad C_{gd} = C_{OL}W, \quad C_{db} = 0$$


Cutoff:
 $N_{GS} < V_T$

$$C_{gs} = C_{OL}W, \quad C_{gd} = C_{OL}W, \quad C_{gb} = C_{ox}WL$$

C_{OL} = overlap capacitance between gate & drain/source

BIPOLAR JUNCTION TRANSISTORS

Physical Picture:

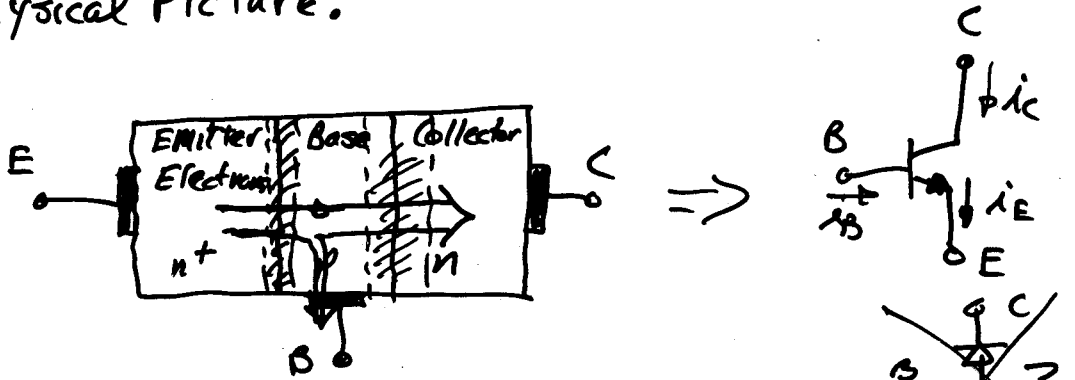


Active Forward Region of operation:

BE is forward-biased
BC is reverse-biased

$$i_c = \beta_F i_B$$

$$i_c = \alpha_F i_E$$

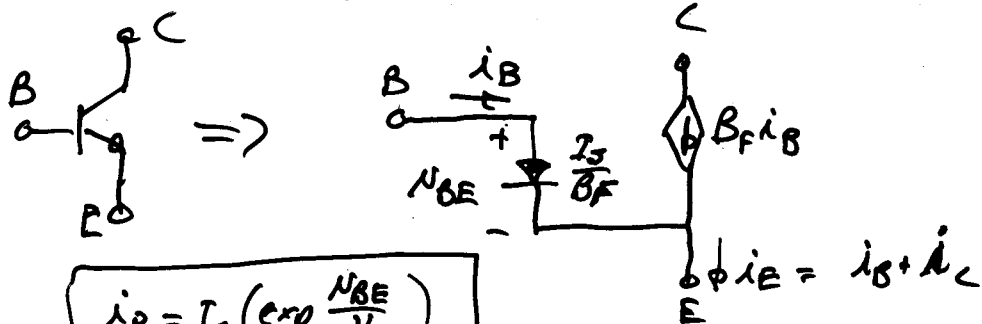Large Signal Model:
(Forward-active region)





$$i_B = \frac{I_S}{\beta_F} \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$i_c = \beta_F i_B = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \quad (m=1)$$

Simplification:

Current i_B is determined externally

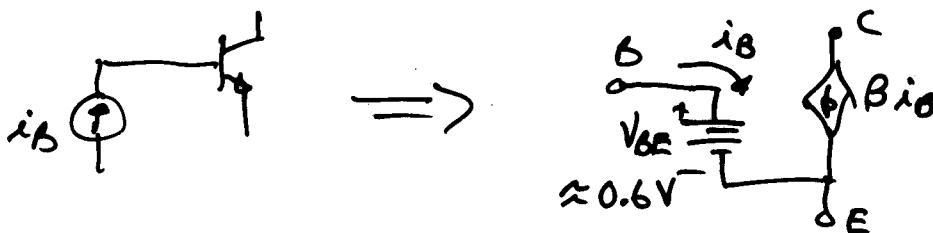

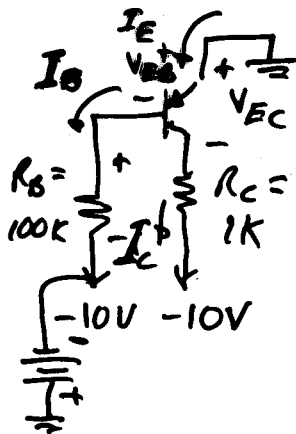Example 1

If $\beta_F = 50$, find I_C , V_{EC} , V_{EB} , I_E , & I_B

$$+10V = I_B R_B + V_{EB}$$

$$I_B = \frac{10 - V_{EB}}{R_B}$$

$$I_B = \frac{10 - 0.7}{100k} = \underline{\underline{93\mu A}}$$

$$I_B \approx \frac{10}{100k} = 100\mu A$$

$$I_C = 50 \cdot 93\mu A = \underline{\underline{4.65 mA}}$$

$$I_E = I_B + I_C = \underline{\underline{4.74 mA}}$$

$$V_{EB} \approx 0.7$$

$$V_C = -10 + I_C R_C = \underline{\underline{-5.35V}}$$

$$V_B = \underline{\underline{-0.7V}} \quad V_E = \underline{\underline{0}}$$

$$V_{EC} = 5.35V$$