


Topics:

- Linearity
- Linear Amplifier
- Decibels
- Amplifiers (power viewpoint)
- Example

CHAPTER 10 - ANALOG SYSTEMS

AMPLIFIER - System Viewpoint

1.) Linearity

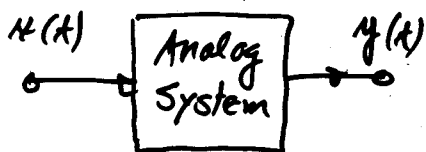

A system is linear iff

$$x_1(t) \rightarrow y_1(t)$$


$$x_2(t) \rightarrow y_2(t)$$

and

$$x_1(t) + x_2(t) \rightarrow y_1(t) + y_2(t)$$

for all $x(t)$.

2.) Linear Amplifier

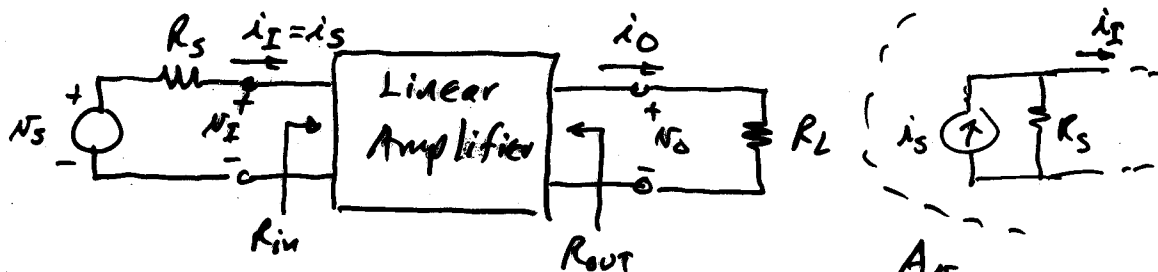

a.) Voltage gain

$$A_N = \frac{v_o}{v_I} (R_s=0) \rightarrow A_V = \frac{v_o}{v_s} = \frac{v_o}{v_I} \times \frac{v_I}{v_s}$$

$$\therefore A_V = A_N \frac{R_{in}}{R_s + R_{in}} \quad (\text{loaded amplifier})$$

\uparrow
 $\frac{R_{in}}{R_s + R_{in}}$

b.) Current gain

$$A_I = \frac{i_o}{i_I} = \frac{i_o}{i_s} = \frac{v_o/R_L}{v_s/R_{in}} = \left(\frac{R_{in} + R_s}{R_L} \right) A_V$$


Comment on R_{out} :

When calculating R_{out} , be sure to set $v_s = 0$

c.) Power gain -

$$A_p = A_v A_i$$

d.) $R_{in} = \frac{N_I}{i_I} = \frac{N_S}{i_S}$ and $R_{out} = - \left. \frac{N_O}{i_O} \right|_{N_S=0} = \left. \frac{N_O}{i_T} \right|_{N_S=0}$

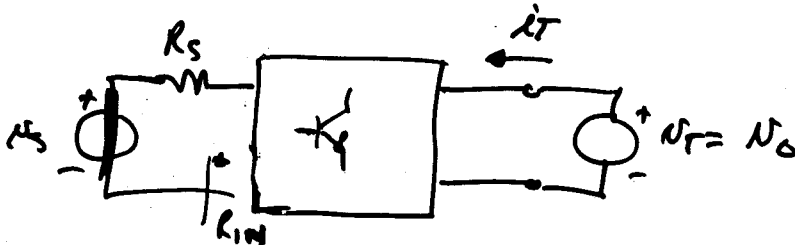

3.) Decibels

Definition: $A_p(\text{dB}) \equiv 10 \log_{10}(A_p)$

If $A_p = 10$, then $A_p(\text{dB}) = 10 \text{ dB}$

Suppose that $R_S = 0$, and $R_L = R_{in}$

$$A_i = \frac{R_S + R_{in}}{R_L} A_v \rightarrow A_i = A_v$$


$$A_v(\text{dB}) = 10 \log_{10}(A_i A_v) = 10 \log_{10}(A_v)^2 = 20 \log_{10} A_v$$

$$\underline{\underline{A_v(\text{dB}) = 20 \log_{10}(A_v)}}$$


$A_v(\text{V/V})$	10	100	1000	$\frac{1}{10}$	100	2	30	20	40
$A_v(\text{dB})$	20	40	60	-20	...	6	30	26	32

Doubling in ratio \rightarrow 6dB increase
 Halving " " \rightarrow -6dB decrease

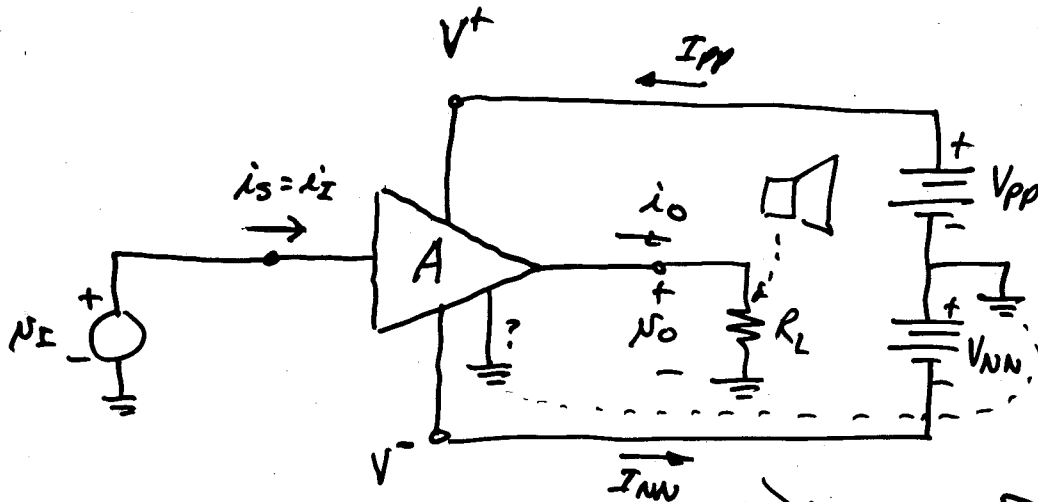4.) Amplifier from a power flow viewpoint



What types of power exist?

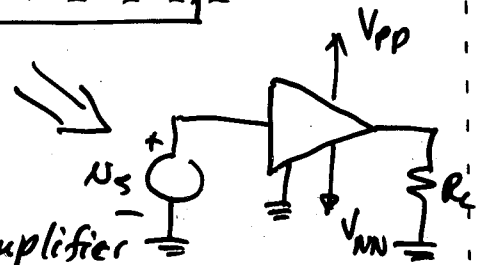

- 1.) DC power delivered to the amplifier from the batteries.

$$P_{DC} = V_{PP} I_{PP} + V_{NN} I_{NN}$$

- 2.) Input power from N_I or the source.

$$P_{IN} = N_I i_s = N_I i_I \quad (\text{typically small})$$

- 3.) Power out = the power in R_L .

$$P_{OUT} = i_o N_o = \frac{N_o^2}{R_L} = i_o^2 R_L$$

- 4.) Power loss - The losses in the amplifier.


Power conservation:

$$P_{DC} + P_{IN} = P_{OUT} + P_{DISS}$$

Efficiency: $\eta = \frac{P_{OUT}}{P_{DC} + P_{IN}} \approx \frac{P_{OUT}}{P_{DC}}$ where $P_{IN} \approx 0$

25%

5.) Example -

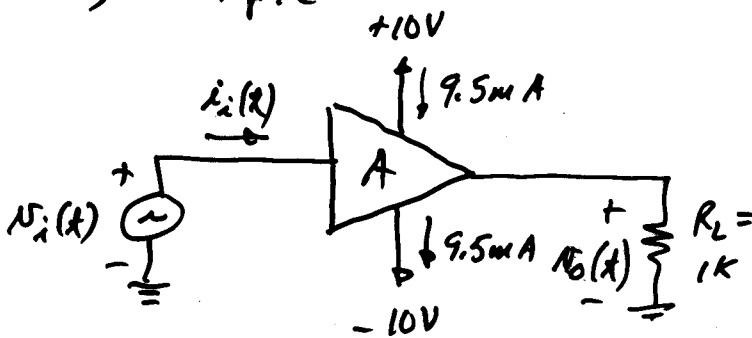

If $v_i(t) = 1 \sin \omega t$,
 then $v_o(t) = 9 \sin \omega t$
 and $i_i(t) = 0.1 \sin \omega t$ (mA).
 Find the efficiency of
 this amplifier.

Solution

$$\eta = \frac{P_L}{P_{DC} + P_{IN}}$$

$$A_V = 9 \text{ V/V} \rightarrow A_V(\text{dB}) = 20 \log_{10}(9)$$

$$= 19.1 \text{ dB}$$

$$i_o(\text{peak}) = \frac{v_o(\text{peak})}{R_L} = \frac{9 \text{ V}}{1 \text{ k}\Omega} = 9 \text{ mA (peak)}$$

$$\therefore i_o(t) = 9 \sin \omega t \text{ (mA)}$$

$$A_i = \frac{i_o(\text{peak})}{i_i(\text{peak})} = \frac{9 \text{ mA}}{0.1 \text{ mA}} = 90 \frac{\text{A}}{\text{A}} \rightarrow A_i(\text{dB}) = 39.1 \text{ dB}$$

$$P_L = \left(\frac{v_o(\text{peak})}{\sqrt{2}} \right)^2 \frac{1}{R_L} = \frac{81 \text{ V}^2}{2 \cdot \text{k}\Omega} = \underline{\underline{40.5 \text{ mW}}}$$

$$P_{IN} = P_I = \frac{v_i(\text{peak})}{\sqrt{2}} \frac{i_i(\text{peak})}{\sqrt{2}} = \left(\frac{1}{\sqrt{2}} \right) \left(\frac{0.1 \text{ mA}}{\sqrt{2}} \right) = \underline{\underline{0.05 \text{ mW}}}$$

$$A_p = \frac{40.5 \text{ mW}}{0.05 \text{ mW}} = 810 \rightarrow A_p(\text{dB}) = 29.1 \text{ dB}$$

$$P_{DC} = 10(9.5 \text{ mA}) + 10(9.5 \text{ mA}) = 190 \text{ mW}$$

$$\eta = \frac{P_L}{P_{DC}} = \frac{40.5 \text{ mW}}{190 \text{ mW}} = 0.21 \rightarrow \underline{\underline{21\%}}$$

$$P_{DISS} = P_{DC} + P_I - P_L = \underline{\underline{149.65 \text{ mW}}}$$

Next:

Review 2-port parameter
 Bode plots