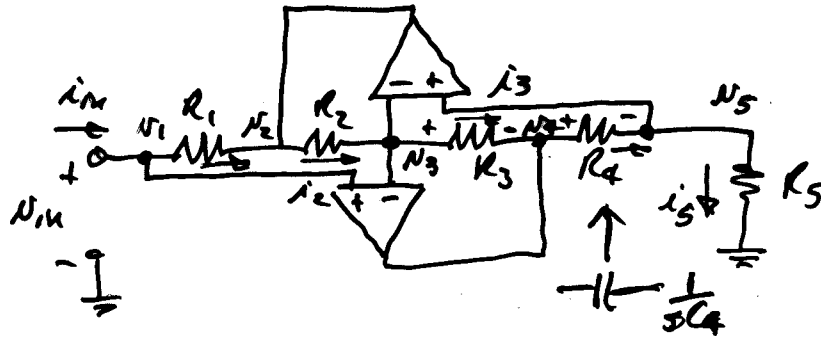


Find R_{in} of the op amp ckt. (Op amps are ideal)



Ideal opamp: $N_1 = N_3 = N_5$, $i_2 = i_3$, $i_{in} = i_1$, $i_4 = i_5$

$$\frac{N_{in}}{i_{in}} = \frac{N_1}{i_1} = ? = \frac{N_3}{i_3} = \frac{N_5}{i_5}$$

$$i_4 = i_5$$

$$i_3 R_3 + i_4 R_4 = 0 \Rightarrow i_3 = -\frac{R_4}{R_3} i_4 = -\frac{R_4}{R_3} i_5$$

$$i_2 = i_3 = -\frac{R_4}{R_3} i_5$$


$$i_1 R_1 + i_2 R_2 = 0 \Rightarrow i_1 = -\frac{R_2}{R_1} i_2 = \left(-\frac{R_2}{R_1}\right) \left(-\frac{R_4}{R_3}\right) i_5$$

$$\therefore \frac{N_{in}}{i_{in}} = \frac{N_5}{i_1} = \frac{N_5}{\frac{R_2 R_4}{R_1 R_3} i_5} = \frac{R_1 R_3}{R_2 R_4} \frac{N_5}{i_5} = \frac{R_1 R_3 R_5}{R_2 R_4}$$

$$Z_{in} = \frac{R_1 R_3 R_5}{R_2} sC_4 = sL_{eq}$$

Some Op Amp Ckts.


1.) Voltage buffer

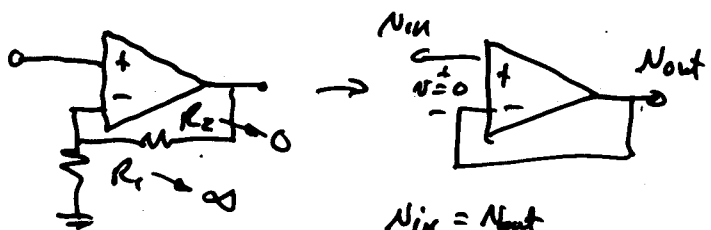


$$N_{in} = N_{out}$$

$$\frac{N_{out}}{N_{in}} = 1$$


2.) Summing Amplifier

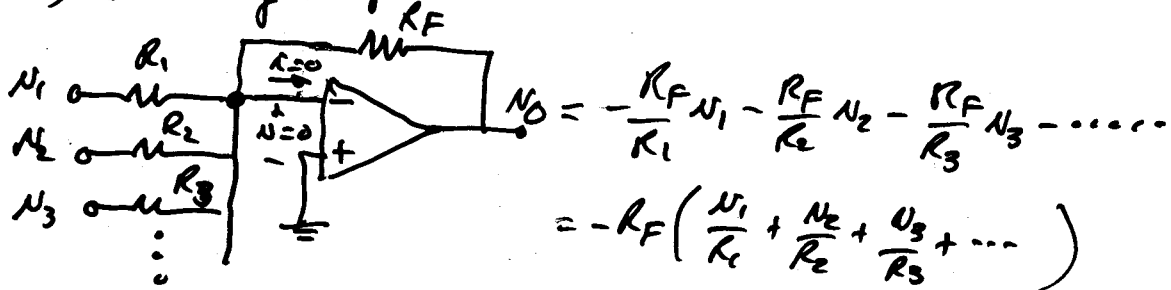


3.) Difference Amplifier

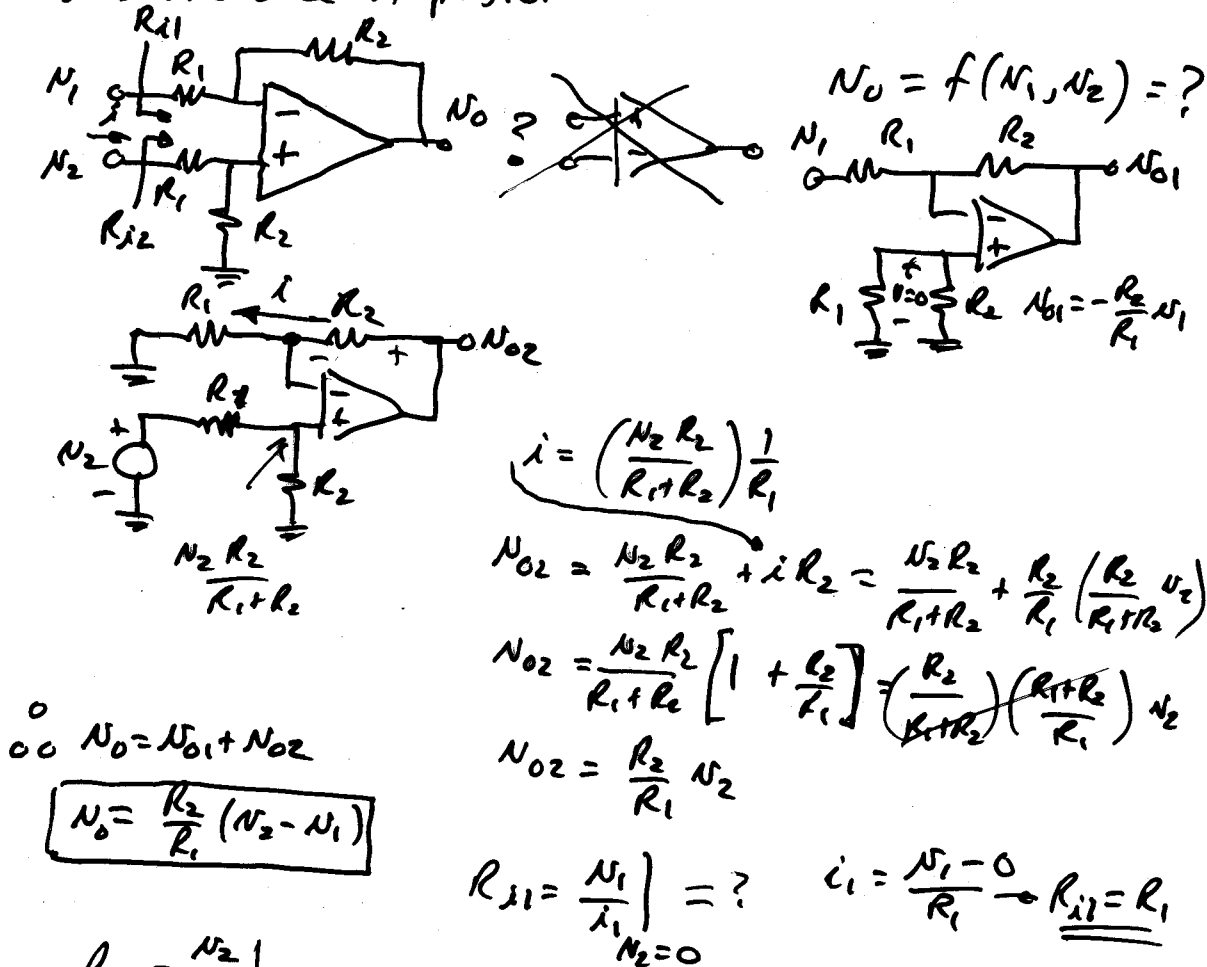

4.) Integrator

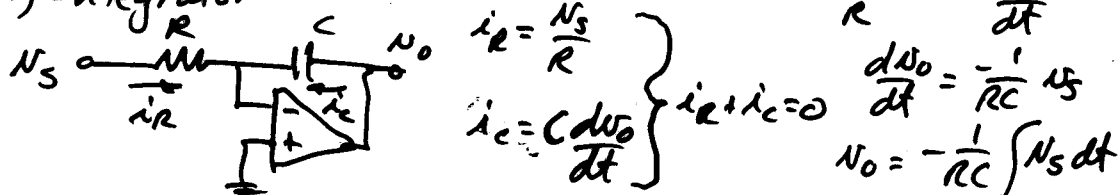

5.) First-order lowpass circuit

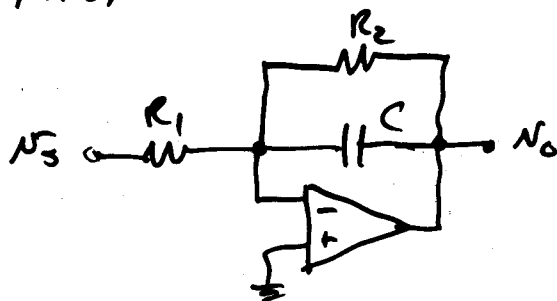


$$Z_2 = \frac{R_2 \frac{1}{sC}}{R_2 + \frac{1}{sC}} = \frac{R_2}{sR_2C + 1} \rightarrow \frac{V_o}{V_s} = -\frac{R_2}{R_1} \left(\frac{1}{sR_2C + 1} \right)$$

$$\text{Let } \omega_H = \frac{1}{R_2C} \quad \& \quad A_0 = \frac{R_2}{R_1}$$



$$\frac{V_o(s)}{V_s(s)} = A_v(s) = \frac{-A_0}{\left(\frac{s}{\omega_H} + 1 \right)}$$

Non-ideal op amp

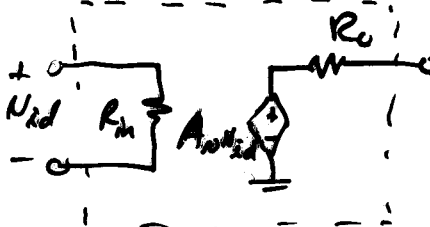- 1.) $A_v \neq \infty$
- 2.) $BW \neq \infty$
- 3.) $R_{in} \neq \infty$ and $R_o \neq 0$




Single-pole model of an op amp

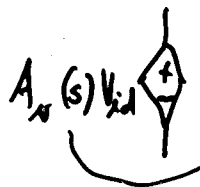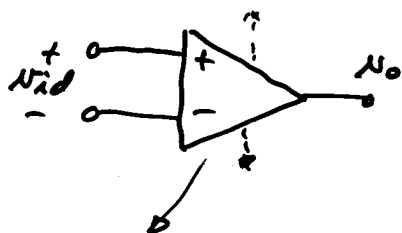


$$A_v(s) = \frac{A_0 \omega_B}{s + \omega_B}$$

$$= \frac{A_0}{\frac{s}{\omega_B} + 1} = \frac{\omega_T}{s + \omega_B} = \frac{GB}{s + \omega_B + 50^\circ}$$

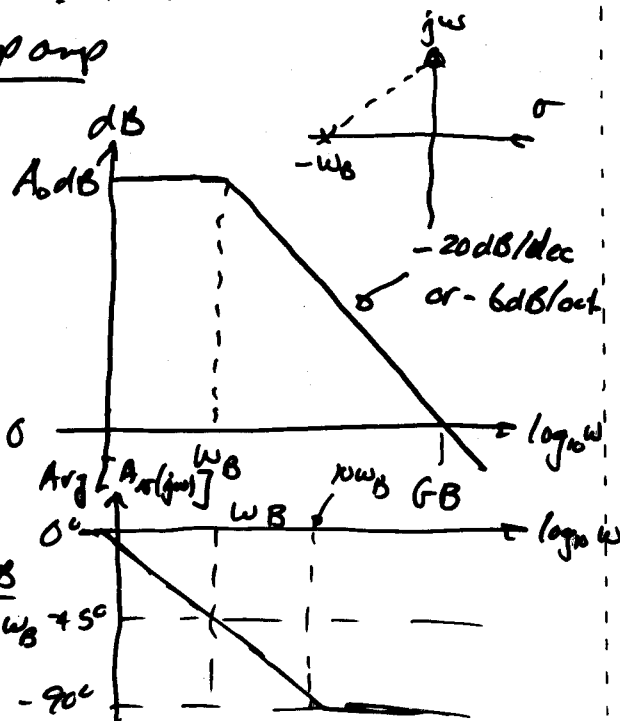$\omega_T = GB = \text{unity-gain frequency}$



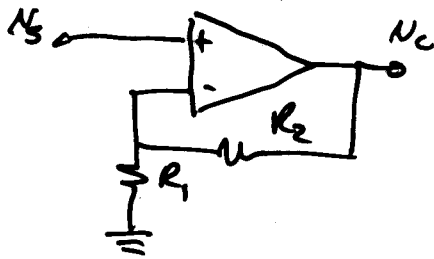Frequency Response of the Noninverting Amplifier

If $A_v(s) = \frac{GB}{s + \omega_B}$, what
is $\frac{V_o(j\omega)}{V_s(j\omega)}$?