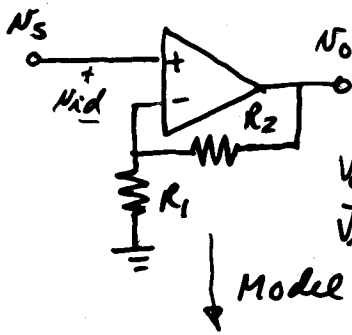


Frequency Response of the Noninverting Amplifier




If the differential voltage gain of the op amp is

$$\frac{V_o(s)}{V_{id}(s)} = A_v(s) = \frac{GB}{s + \omega_B}$$

what is  $\frac{V_o(j\omega)}{V_s(j\omega)}$ ?

$$GB = A_o \omega_B$$

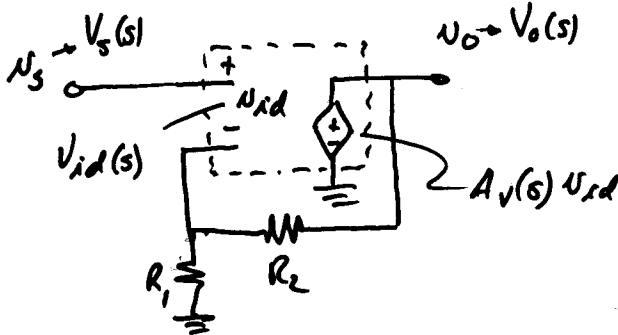

$$V_o(s) = A_v(s) V_{id}(s)$$


$$V_{id}(s) = V_s - \frac{R_1}{R_1 + R_2} V_o(s)$$

$$V_o(s) = A_v(s) \left[ V_s(s) - \frac{R_1}{R_1 + R_2} V_o(s) \right]$$

$$\frac{V_o(s)}{V_s(s)} = \frac{A_v(s)}{1 + A_v(s) \frac{R_1}{R_1 + R_2}} = \frac{A}{1 + AB}$$

$A = A_v(s)$   
 $B = \frac{R_1}{R_1 + R_2}$

What is the op amp frequency response?

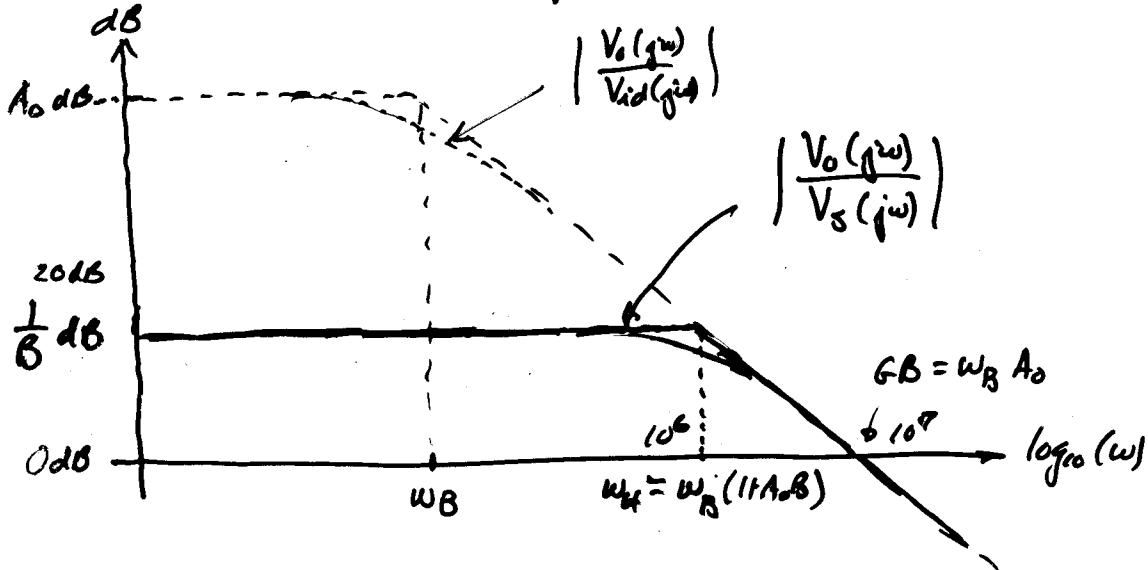

$$\frac{V_o(s)}{V_s(s)} = \frac{A_v(s)}{1 + \frac{R_1}{R_1 + R_2} A_v(s)} = \frac{1}{\frac{1}{A_v(s)} + \frac{R_1}{R_1 + R_2}} = \frac{1}{\frac{s + \omega_B}{GB} + \frac{R_1}{R_1 + R_2}} = \frac{GB}{s + \omega_B + \frac{R_1}{R_1 + R_2} GB}$$

Using  $\beta \equiv \frac{R_1}{R_1 + R_2} \rightarrow \frac{V_o(s)}{V_s(s)} = \frac{A_o \omega_B}{s + \omega_B + \beta \omega_B A_o} = \frac{A_o \omega_B}{s + \omega_B (1 + A_o \beta)} \times \frac{(1 + A_o \beta)}{1 + A_o \beta}$


$$\frac{V_o(s)}{V_s(s)} = \left( \frac{A_o}{1 + A_o \beta} \right) \left( \frac{\omega_B (1 + A_o \beta)}{s + \omega_B (1 + A_o \beta)} \right) = \frac{A_o}{1 + A_o \beta} \frac{1}{\frac{s}{\omega_B (1 + A_o \beta)} + 1}$$

$$\frac{V_o(j\omega)}{V_s(j\omega)} = \left( \frac{A_o}{1 + A_o \beta} \right) \frac{1}{1 + j \frac{\omega}{\omega_H}}, \quad \omega_H = \omega_B (1 + A_o \beta)$$

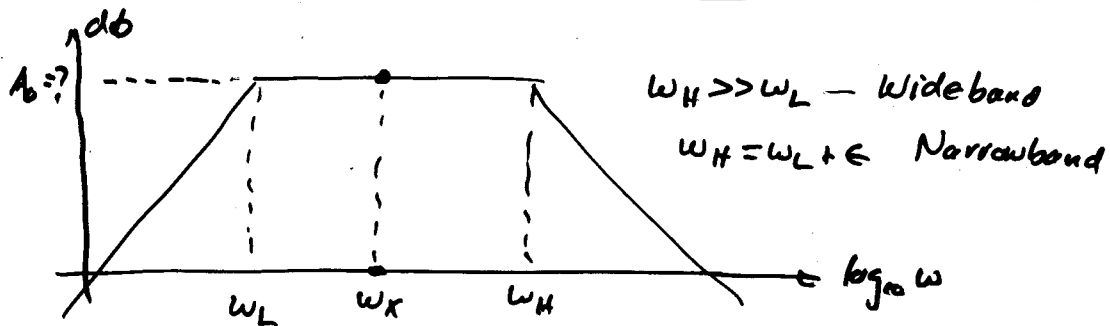Example:  $A_o = 10,000, \omega_B = 1000 \text{ rad/s} \left\{ R_2 = 9R_1 \right.$


$$\beta = \frac{R_1}{R_1 + R_2} = \frac{1}{1 + \frac{R_2}{R_1}} = \frac{1}{10}, \quad \frac{10^4}{1 + 10^4 \cdot \frac{1}{10}} = \frac{10^4}{1 + 10^3} \approx 10$$

$$\omega_H = 1000 (1 + 10^3) \approx 10^6 \text{ rad/sec}$$




$$A_v(s) = 100 \left( \frac{10^4}{s + 10^4} \right) \left( \frac{s}{s + 10} \right) = \frac{10^6 s}{(s + 10)(s + 10^4)}$$

Inverting Amplifier Frequency Response

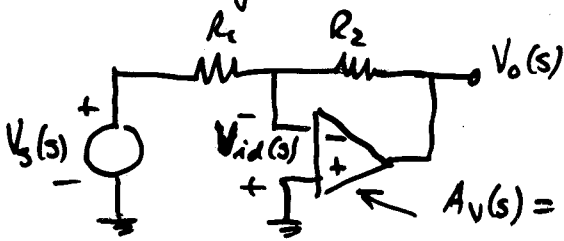

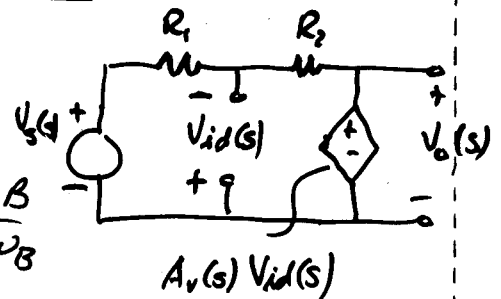
$$A_v(s) = \frac{A_o \omega_B}{s + \omega_B} = \frac{GB}{s + \omega_B}$$



Results:

$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{\omega_B A_o B}{s + \omega_B (1 + A_o B)} = \left(-\frac{R_2}{R_1}\right) \left(\frac{A_o B}{1 + A_o B}\right) \left[\frac{\omega_B (1 + A_o B)}{s + \omega_B (1 + A_o B)}\right]$$


$$B = \frac{R_1}{R_1 + R_2}$$

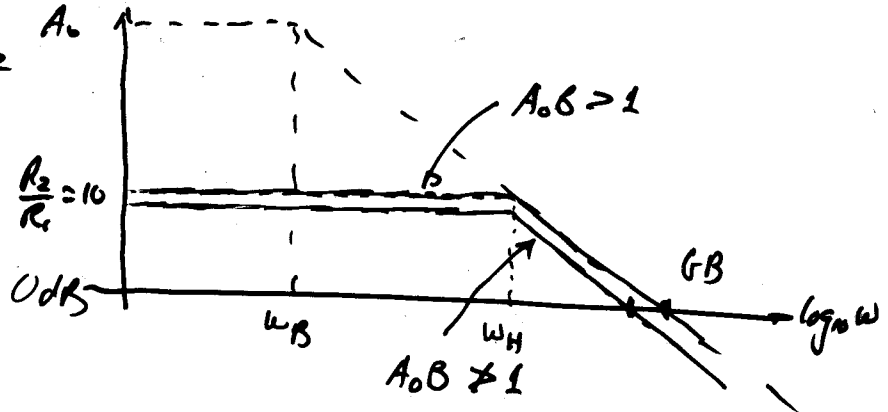

Examples

a) An op amp with  $A_o = 100 \text{ dB}$  and  $GB = 10 \text{ MHz}$  is used to build a voltage amplifier with a gain of  $+1$  and then a gain of  $-1$ . Find  $\omega_H$  of the amplifiers.

$+1$ :

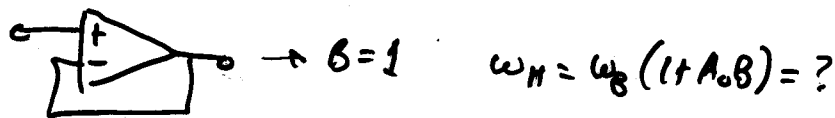


$\rightarrow B = 1 \quad \omega_H = \omega_B (1 + A_o B) = ?$

$$\omega_B = \frac{GB}{A_o} = \frac{10^7 \times 2\pi}{10^5} = 200\pi \rightarrow 100 \text{ kHz}$$

$$f_H = 100 (1 + 10^5 \cdot 1) \approx 100 \text{ MHz}$$

$-1$ :

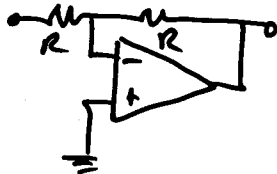

$\Rightarrow B = \frac{1}{2} \rightarrow f_H = 100 (1 + 10^5 \cdot \frac{1}{2}) = 50 \text{ MHz}$

$+100$ :

$$B = \frac{1}{100} = \frac{R_1}{R_1 + R_2} \rightarrow f_H = 50 \text{ kHz}$$

$-100$ :

$$B = \frac{1}{101} = \frac{R_1}{R_1 + R_2} \quad f_H = 49.5 \text{ kHz}$$



Chapter 13