

What homework will Quiz #2 be on? (Allen asked this question.)


Op amps (ideal) and frequency. (Q2 & Q3 of Fall 2002)

Question:

$$\frac{-10(s+1)}{(s+10)(s+100)} \rightarrow \frac{-10\left(\frac{s}{1}+1\right)}{10(100)\left(\frac{s}{10}+1\right)\left(\frac{s}{100}+1\right)}$$


$$20 \log_{10} \frac{1}{100} + 20 \log_{10} \sqrt{1+\left(\frac{\omega}{1}\right)^2} - 20 \log_{10} \sqrt{1+\left(\frac{\omega}{10}\right)^2} - 20 \log_{10} \sqrt{1+\left(\frac{\omega}{100}\right)^2}$$
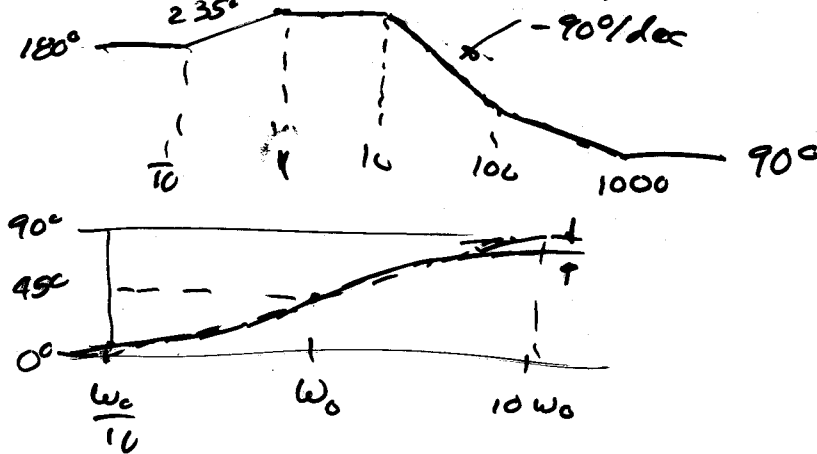
$$\pm 180^\circ + \tan^{-1}\left(\frac{\omega}{1}\right) - \tan^{-1}\left(\frac{\omega}{10}\right) - \tan^{-1}\left(\frac{\omega}{100}\right)$$



TRANSISTOR AMPLIFIERS

1.) BJT

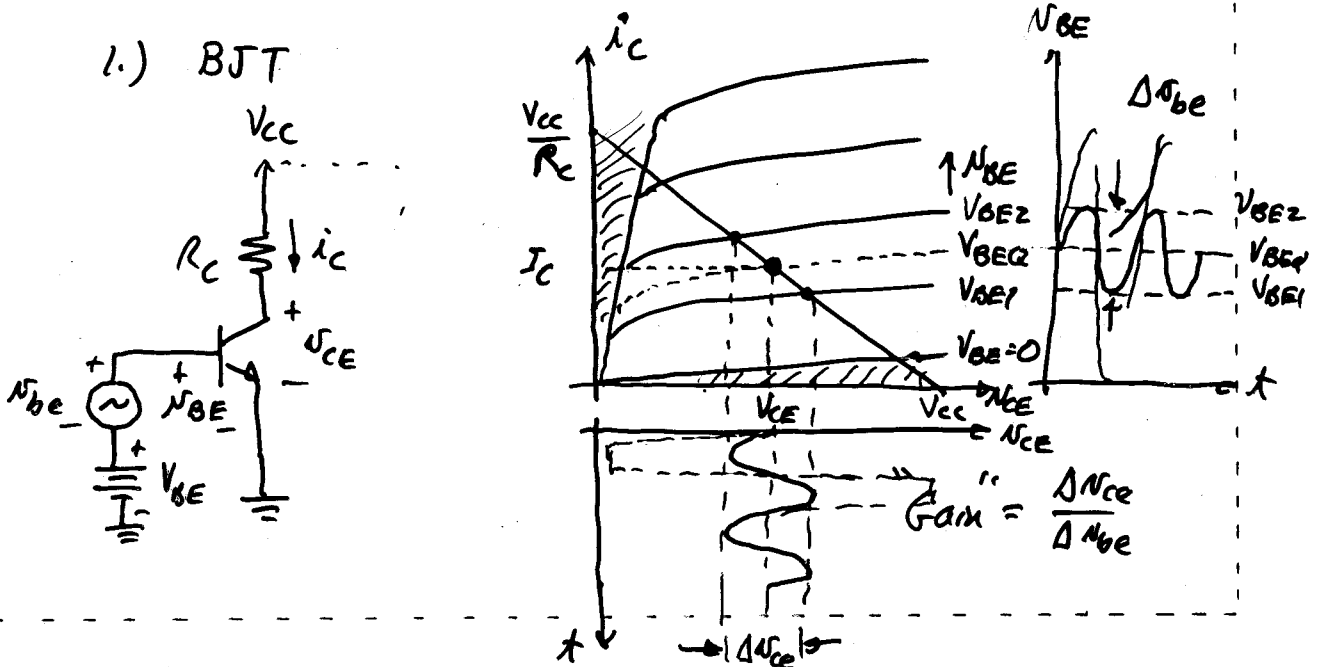



Mathematically,

$$V_{CE} = V_{CC} - I_C R_C = V_{CC} - R_C I_S \exp\left(\frac{V_{BE}}{V_T}\right) - I_C R_C \quad I_{CQ}$$

$$\left. \frac{\partial V_{CE}}{\partial V_{BE}} \right|_{V_{BE} = V_{BEQ}} = - \frac{R_C I_S}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) \bigg|_{V_{BEQ}} = - \frac{R_C I_S}{V_T} \exp\left(\frac{V_{BEQ}}{V_T}\right)$$

$$\text{"Gain"} = \left. \frac{\partial V_{CE}}{\partial V_{BE}} \right|_Q = - \frac{R_C I_{CQ}}{V_T} \rightarrow - \frac{10k\Omega (1mA)}{25mV} = \underline{\underline{-400 V/V}}$$

2.) MOSFET

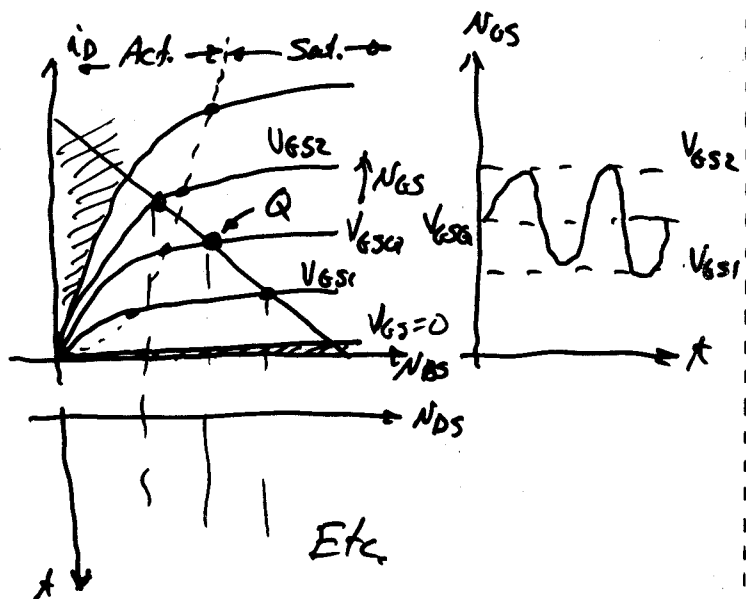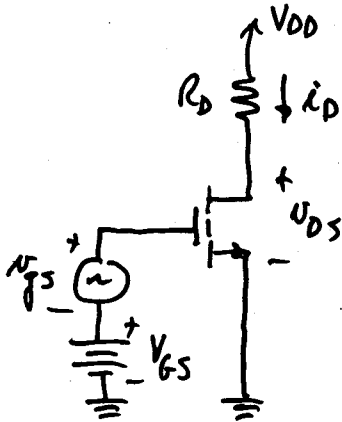


$$V_{DS} = V_{DD} - i_D R_D = V_{DD} - R_D \frac{K_n}{2} (V_{GS} - V_{TN})^2$$

$$\left. \frac{\partial V_{DS}}{\partial V_{GS}} \right|_Q = - R_D K_n (V_{GSQ} - V_{TN}) = - R_D K_n \sqrt{\frac{2 I_{DQ}}{K_n}} = - R_D \sqrt{2 K_n I_{DQ}}$$


$$= - 10k \sqrt{2 \left(\frac{250 \mu A}{V^2}\right) 1mA} = \underline{\underline{-7.07 V/V}}$$

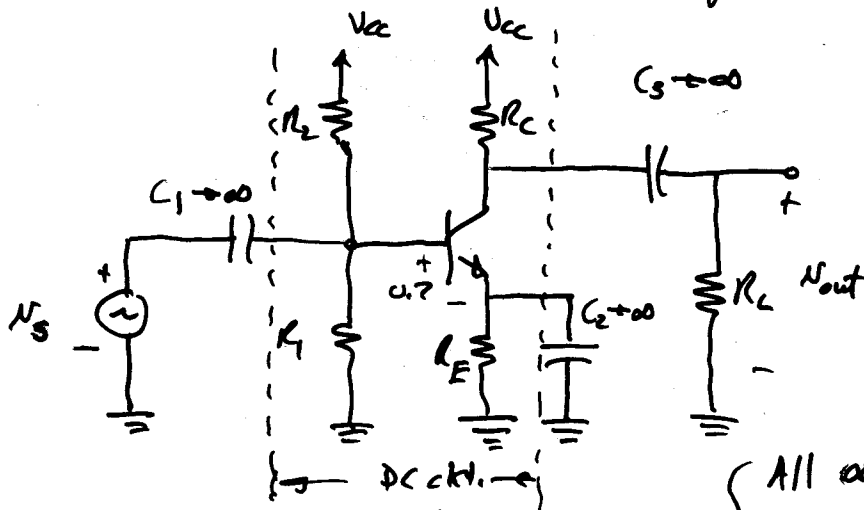3.) Coupling and By pass Capacitors

How do you separate the ac and dc signals?



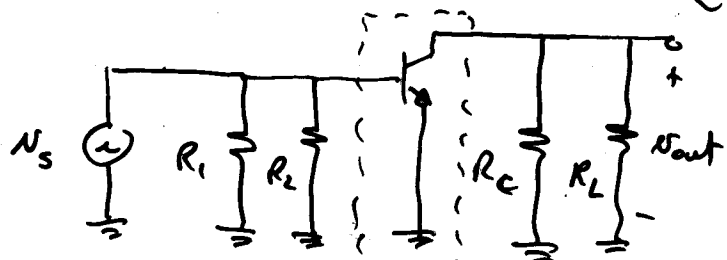DC ckt.
 AC circuit
 { All infinity caps are shorted
 All dc voltages are "
 All dc current sources are opened



4.) Diode Small-Signal Model - ac model, s.s. model

Large signal: $i_D = I_S \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right]$

$i_D = i_d + I_D = I_S \left[\exp\left(\frac{V_d + V_D}{V_T}\right) - 1 \right]$

$i_d + I_D = I_S \exp\left(\frac{V_D}{V_T}\right) \exp\left(\frac{V_d}{V_T}\right) - 1$

Expand $\exp\left(\frac{V_d}{V_T}\right)$ with a Maclaurin's series

$i_d + I_D = I_S \left\{ \exp\left(\frac{V_D}{V_T}\right) \left[1 + \frac{V_d}{V_T} + \frac{1}{2} \left(\frac{V_d}{V_T}\right)^2 + \dots \right] - 1 \right\}$

$i_d + I_D \approx I_S \left[\exp\left(\frac{V_D}{V_T}\right) \right] \left[1 + \frac{V_d}{V_T} \right] - I_S = I_S \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right] + \left[I_S \exp\left(\frac{V_D}{V_T}\right) \right] \left(\frac{V_d}{V_T} \right)$

$\therefore i_d + I_D = I_D + \left[I_S \exp\left(\frac{V_D}{V_T}\right) \right] \left(\frac{V_d}{V_T} \right) \rightarrow i_d = \left(\frac{I_D + I_S}{V_T} \right) V_d = g_m V_d$