

Diode Small-Signal Model - Cont'd

$$i_D = i_d + I_D = I_S \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right] = I_S \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right]$$

$$i_d + I_D = I_S \left[\exp\left(\frac{V_D}{V_T}\right) \exp\left(\frac{V_D}{V_T}\right) - 1 \right]$$


$$\text{If } V_D \ll V_T, \text{ then } \exp\left(\frac{V_D}{V_T}\right) \approx 1 + \frac{V_D}{V_T} + \frac{1}{2} \left(\frac{V_D}{V_T}\right)^2 + \dots$$

$$\therefore i_d + I_D \approx I_S \left[\exp\left(\frac{V_D}{V_T}\right) \right] \left[1 + \frac{V_D}{V_T} \right] - I_S$$


$$\approx \underbrace{I_S \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right]}_{I_D} + \underbrace{\left[I_S \exp\left(\frac{V_D}{V_T}\right) \right]}_{I_D + I_S} \left(\frac{V_D}{V_T} \right)$$

$$\therefore i_d \approx \left(\frac{I_D + I_S}{V_T} \right) V_D \approx \left(\frac{I_D}{V_T} \right) V_D \text{ if } V_D > 0$$

Graphically -

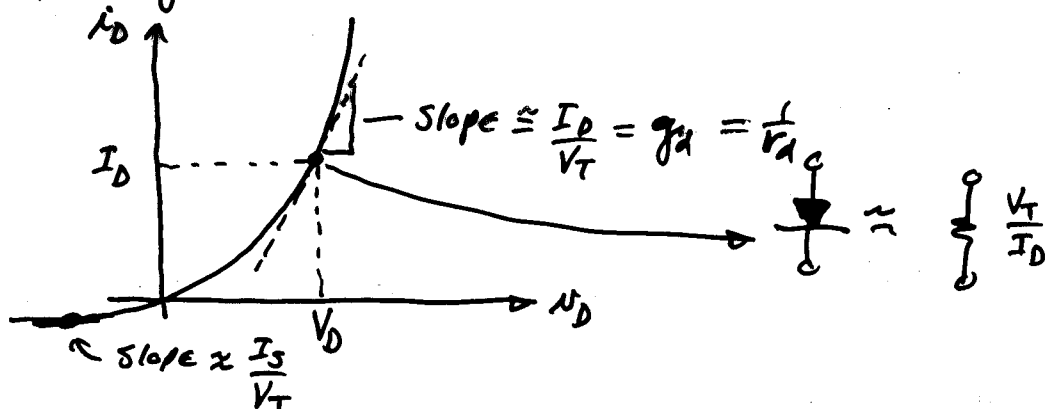

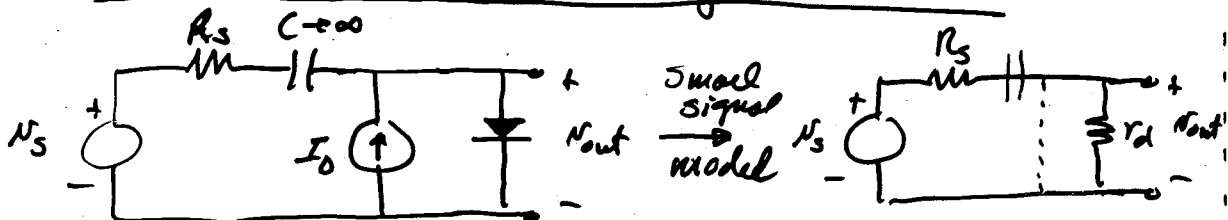Current-Controlled Small-Signal Attenuator




$$\frac{V_{out}}{V_S} = \frac{r_d}{r_d + R_S} = \frac{1}{1 + \frac{R_S}{r_d}} = \frac{1}{1 + \frac{R_S I_D}{V_T}}$$

SMALL-SIGNAL TRANSISTOR MODELS

Approach:

1.) $i_A = i_a + I_A \rightarrow i_a = i_A - I_A = \Delta i_A = \Delta i_A$

2.) CE BJT

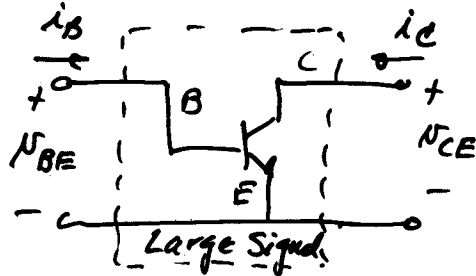


Forward active (BE is fwd. biased and CE is reverse biased.)


$$i_C = I_S \left[\exp\left(\frac{V_{BE}}{V_T}\right) \right] \left[1 + \frac{V_{CE}}{V_A} \right]$$

$$i_B = \frac{I_S}{\beta_F} \exp\left(\frac{V_{BE}}{V_T}\right)$$
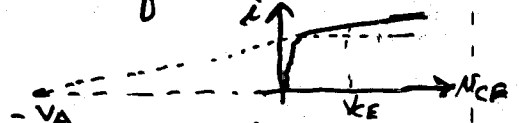
$$V_T = \frac{kT}{q} \approx 26 \text{ mV}$$



"Linearize"

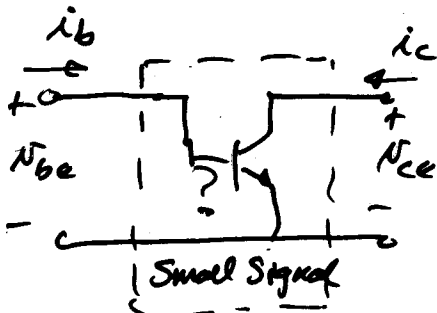

$$i_C = k_1 V_{BE} + k_2 V_{CE}$$

$$i_B = k_3 V_{BE}$$

What are k_1, k_2, k_3 ?

Define:


$$k_1 = \left. \frac{i_C}{V_{BE}} \right|_{V_{CE}=0} = \left. \frac{\partial i_C}{\partial V_{BE}} \right|_Q = \frac{I_C}{V_T} = g_m$$

$$k_2 = \left. \frac{i_C}{V_{CE}} \right|_{V_{BE}=0} = \left. \frac{\partial i_C}{\partial V_{CE}} \right|_Q = \frac{I_C}{V_A + V_{CE}} \approx \frac{I_C}{V_A} = g_o$$

$$k_3 = \left. \frac{i_B}{V_{BE}} \right|_Q = \left. \frac{\partial i_B}{\partial V_{BE}} \right|_Q = \frac{I_C}{\beta_F V_T} = g_{\pi} = \frac{1}{r_{\pi}}$$

$i_c = g_m N_{be} + g_o N_{ce}$

$i_b = g_{\pi} N_{be}$

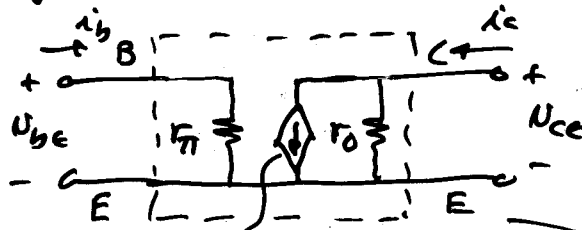

$g_m N_{be}$

