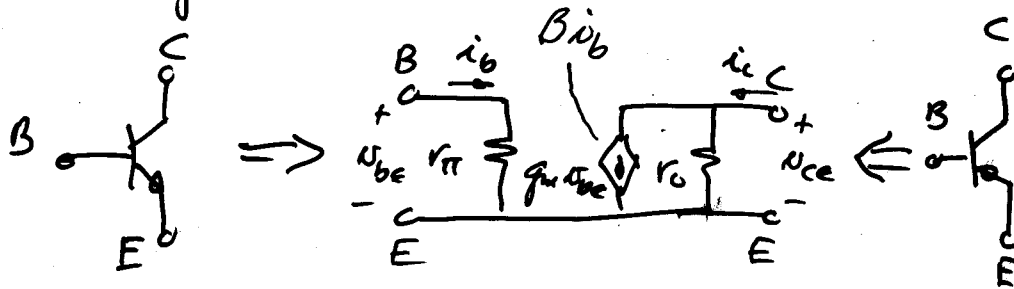


Small-signal analysis of transistor amplifiers


Small-signal-



Small-signal model parameter - (r_{π}, g_m, β, r_o)


$(\beta_F = g_m r_{\pi})$ $\beta_0 = g_m r_{\pi}$

• $\beta_F = f(I_C)$?

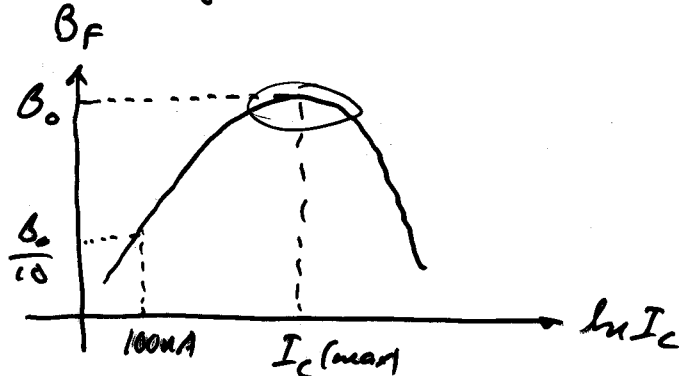


• $g_m = \frac{I_C}{V_T} = \frac{I_C}{kT/q}$, $r_{\pi} = \frac{I_C}{\beta_0 V_T} = \frac{g_m}{\beta_0} \rightarrow r_{\pi} = \frac{\beta_0}{g_m}$

$\frac{1}{r_o} = g_o = \frac{I_C}{V_A + V_{CE}} \approx \frac{I_C}{|V_A|}$

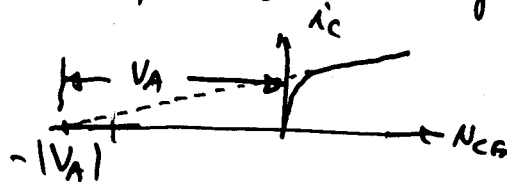


• A s.s. model is linear $\Rightarrow v_{be} \ll V_T \approx 26\text{mV}$

Example

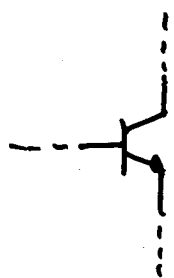


$I_C = 1\text{mA}$
 $\beta_0 = 100$
 $V_A = 100\text{V}$

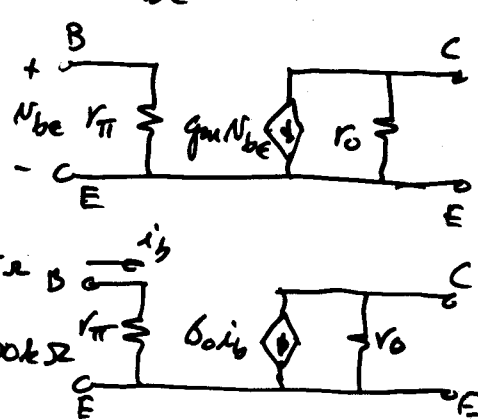$g_m = \frac{I_C}{V_T} = \frac{1\text{mA}}{26\text{mV}} = \frac{1}{26}\text{S}$
 $r_{\pi} = \frac{\beta_0}{g_m} = 2.6\text{k}\Omega$
 $r_o = \frac{100\text{V}}{1\text{mA}} = 100\text{k}\Omega$



MOSFET Small-Signal Models

1.) Large signal model

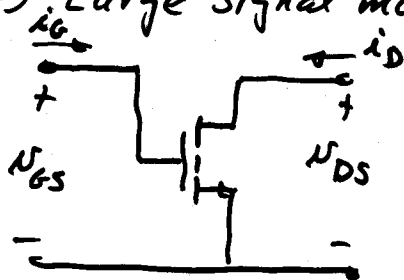


Mathematical Model

Assumes saturation

$$I_D = \frac{K_n'}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

$$I_G = 0$$

2.) Small-signal model

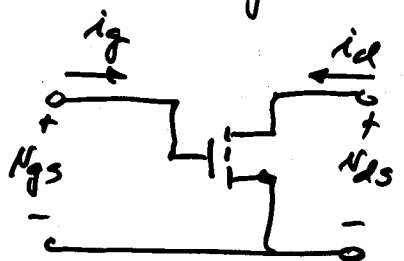

Mathematical Model

$$i_d = k_1 v_{gs} + k_2 v_{ds}$$

$$i_g = 0$$

$$k_1 = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS}=0} = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS}} \approx K_n' (V_{GS} - V_{TN}) (1 + \lambda V_{DS})$$

$$k_1 = g_m = K_n' (V_{GS} - V_{TN})$$

$$g_m \approx K_n' (V_{GS} - V_{TN})$$

where $\lambda V_{DS} \ll 1$

$$I_D = \frac{K_n'}{2} (V_{GS} - V_{TN})^2 \rightarrow V_{GS} - V_{TN} = \sqrt{\frac{2I_D}{K_n'}}$$


$$g_m = K_n' \sqrt{\frac{2I_D}{K_n'}} = \sqrt{2K_n' I_D}$$

$$k_2 = \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{V_{GS}=0} = \left. \frac{\partial I_D}{\partial V_{DS}} \right|_Q = \frac{K_n'}{2} (V_{GS} - V_{TN})^2 \lambda \approx I_D \lambda$$

$$g_{ds} = g_o = k_2 = \frac{I_D \lambda}{1 + \lambda V_{DS}} \approx I_D \lambda$$


Amplification factor

$$\mu \equiv g_m r_o$$

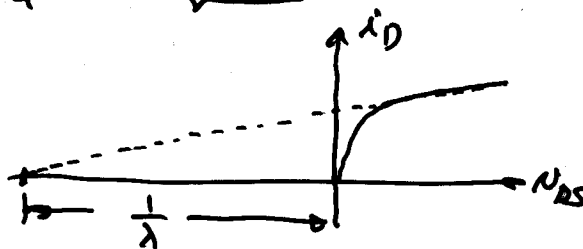

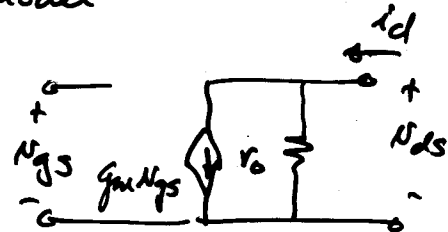3.) Schematic small-signal model


$$\left. \begin{aligned} i_d &= g_m N_{gs} + g_o N_{ds} \\ i_g &= 0 \end{aligned} \right\}$$



Good for both NMOS and PMOS

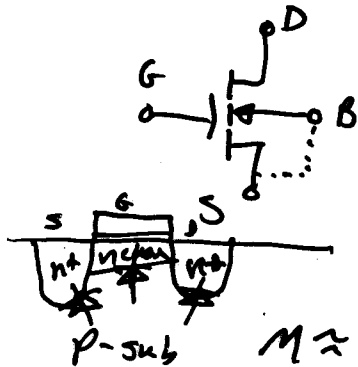4.) Body effect


$$V_{TN} = V_{T0} + \gamma \sqrt{N_{SB} + 2\phi_F} - \gamma \sqrt{2\phi_F} = f(N_{SB})$$



$$i_d = g_m N_{gs} + g_o N_{ds} + k_3 N_{sb} \rightarrow g_m$$


$$\frac{\partial i_d}{\partial N_{sb}} = g_{mb} = \frac{\gamma k_n (V_{GS} - V_{T0})}{2 \sqrt{N_{SB} + 2\phi_F}} = M g_m$$

$$M \approx \frac{1}{10}$$

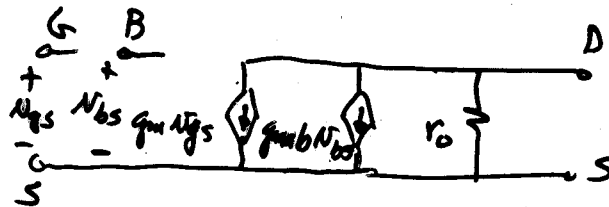


$g_m N_{sb} \Rightarrow$ the arrow ALWAYS points to the 2nd subscript.

BJT Example

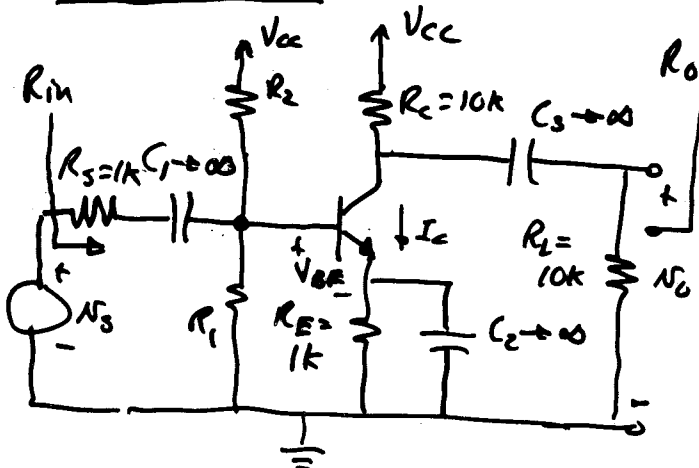

Find the small-signal input resistance, R_{in} , the output resistance, R_{out} , and $\frac{N_o}{N_s}$ where $I_C = 1mA$, $\beta_0 = 100$ and $V_A = 100V$.
 $R_1 || R_2 = R_B = 20k\Omega$

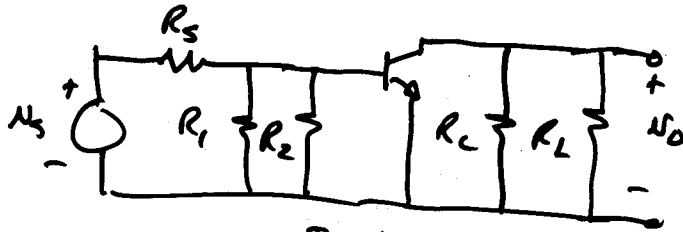SS eq. ckt. ($C \rightarrow \infty \rightarrow$ short $V_{CC} = 0$)



To be continued