

My Wednesday Office Hour has changed from 2-3pm to 3-4pm


NMOS Example

If $k_n = 0.5 \text{ mA/V}^2$,


$V_{TN} = 1\text{V}$ and

$\lambda = 0.001 \text{ V}^{-1}$, find

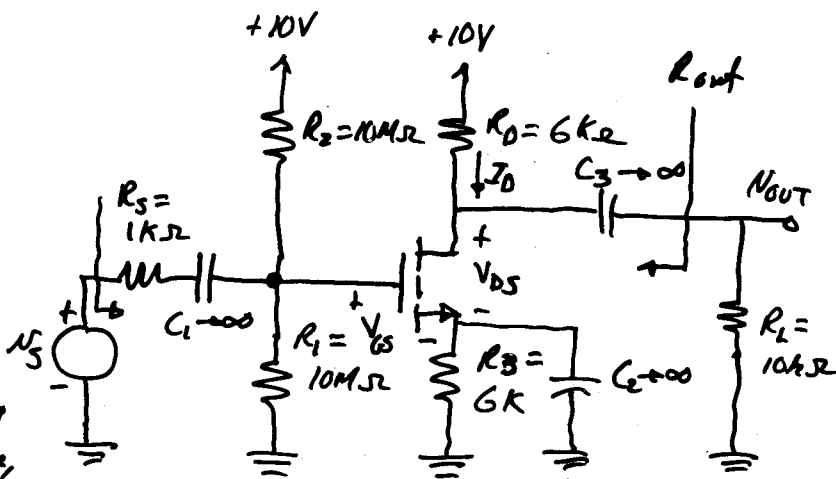The small signal voltage gain, $\frac{v_{out}}{v_s}$,
input resistance, R_{in} ,
and output resistance, R_{out} .




1.) Q point

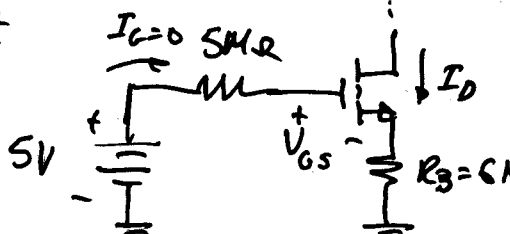

$5 = V_{GS} + I_D R_3$
Assume saturation
 $I_D = k_n (V_{GS} - V_{TN})^2 \dots$

Resulting quadratic is:

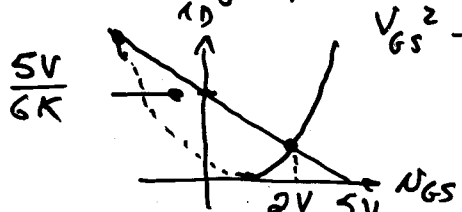

$V_{GS}^2 - \frac{5}{3} V_{GS} - \frac{2}{3} = 0 \rightarrow \frac{5}{6} \pm 1.1667 = 2\text{V}$

$I_D = 0.5 \frac{\text{mA}}{\text{V}^2} (2-1)^2 = \underline{\underline{0.5 \text{ mA}}}$

$V_{DS} = 10 - I_D R_D - I_D R_S = 10 - \frac{1}{2}(12) = 4\text{V}$


$I_S 4\text{V} \geq 2-1 \text{ Yes}$

2.) SS model parameters

$f_m = \sqrt{2 k_n I_D (1 + \lambda V_{DS})} = \underline{\underline{0.721 \text{ MS}}}$

$r_{ds} = \frac{V_{DS} + \frac{1}{\lambda}}{I_D} = \frac{4\text{V} + 1000\text{V}}{0.5 \text{ mA}} = \frac{104}{0.5} \text{ K} = \underline{\underline{208 \text{ k}\Omega}}$

3.) Small-signal circuit

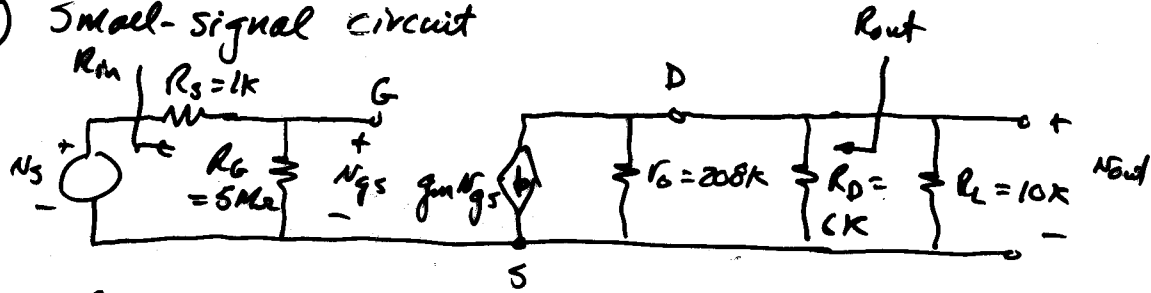


$$R_{in} = R_s + R_g = \underline{5.001M\Omega} \quad R_{out} = 208k \parallel 6k \approx \underline{6k} \quad (5.83k\Omega)$$

$$\frac{N_{out}}{N_s} = \left(\frac{N_{out}}{N_{GS}} \right) \left(\frac{N_{GS}}{N_s} \right) = \left[-g_m (r_o \parallel R_D \parallel R_L) \right] \left[\frac{R_g}{R_s + R_g} \right]$$

$$= -(0.721) \left[208k \parallel 6k \parallel 10k \right] \left[\frac{5M}{5.001M} \right] = \underline{-2.13V}$$

PNP Example

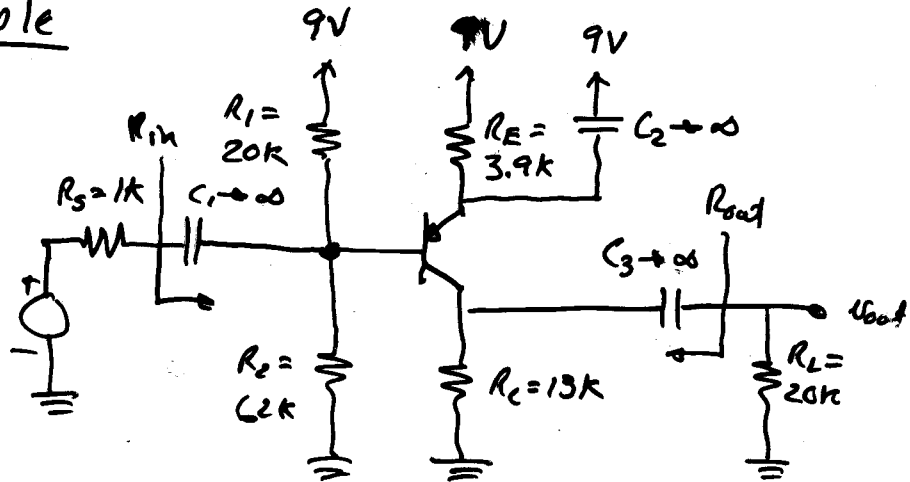If $\beta_0 = 135$
and $V_A = 100V$,
find $\frac{N_{out}}{N_s}$,
 R_{in} & R_{out} .



1.) Q point