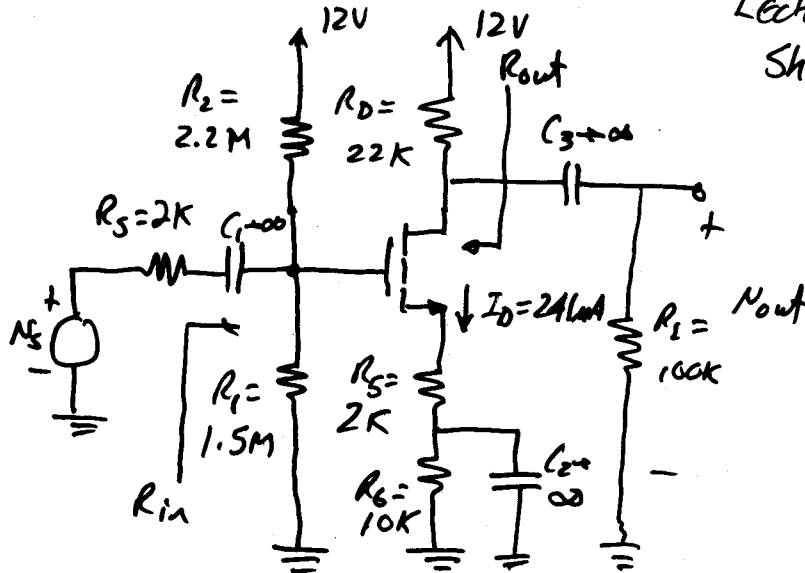


Common Source Example


2/16 → 2/20

Lecturer will be Shaked.



$V_{DS} = 3.81V$
 $V_{GS} = 1.982V$
 $k_n = 500\mu A/V^2$
 $V_{TN} = 1V$
 $\lambda = 0$

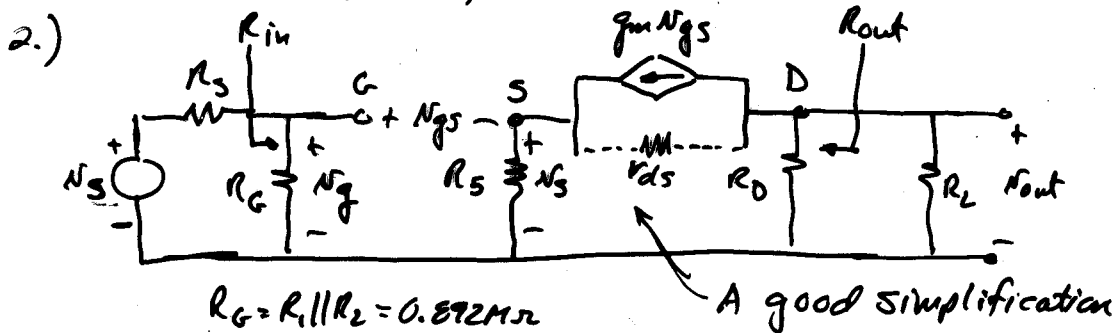1.) $g_m = \sqrt{2k_n I_{D5}} = \sqrt{2 \cdot 500 \cdot 241} \approx 500\mu S$ (509µS)
 $r_{DS} = \infty$ (223kΩ)



$R_G = R_1 || R_2 = 0.892M\Omega$

$R_{out} = R_D = 22k\Omega$

$R_{out}(r_{ds} \neq \infty) = 20.98k\Omega$

$\frac{N_{out}}{N_s} = \left(\frac{N_{out}}{N_{gs}}\right) \left(\frac{N_{gs}}{N_s}\right)$

"Nab trick" → $N_{ab} = N_a - N_b$

$\frac{N_{out}}{N_{gs}} = -g_m (R_D || R_L)$

$\frac{N_{gs}}{N_s} = ?$

$N_{gs} = N_g - N_s$
 Note that $N_s = g_m R_s N_{gs}$

If we let

$\frac{N_{gs}}{N_s} = \left(\frac{N_{gs}}{N_g}\right) \left(\frac{N_g}{N_s}\right)$

$N_{gs} = N_g - g_m R_s N_{gs}$
 $N_{gs}(1 + g_m R_s) = N_g$


Cont'd-

$$\frac{N_{GS}}{N_o} = \left(\frac{1}{1 + g_m R_S} \right) \left(\frac{R_G}{R_S + R_G} \right)$$

$$\therefore \frac{N_{out}}{N_S} = \left(\frac{N_{out}}{N_{GS}} \right) \left(\frac{N_{GS}}{N_G} \right) \left(\frac{N_G}{N_S} \right) = \frac{-g_m (R_o \parallel R_L) R_G}{(1 + g_m R_S) (R_G + R_S)}$$

$$\frac{N_{out}}{N_S} = \frac{509 (-500 \mu S) (22K \parallel 100K) \left(\frac{892}{894} \right)}{1 + (500 \mu S) (2K)} = -4.54 \frac{V}{V}$$

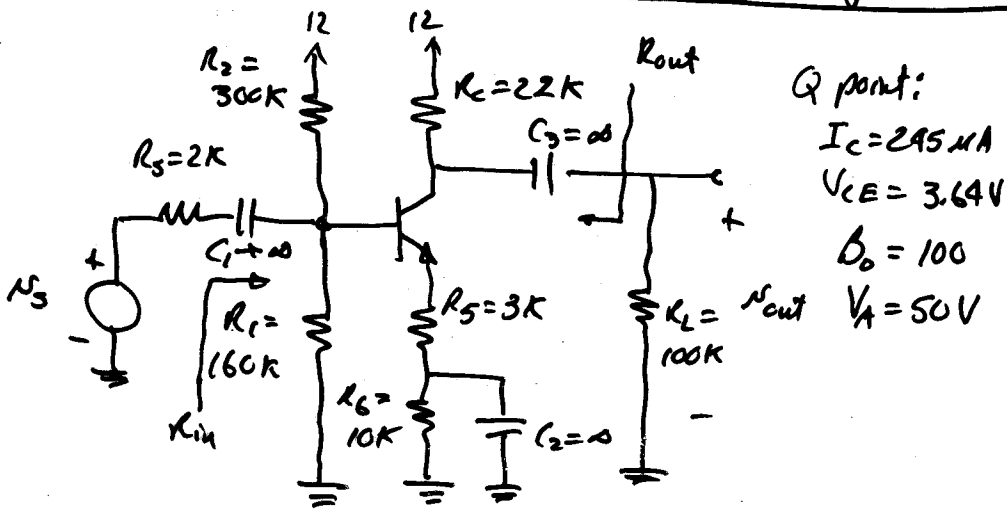Common Emitter Amplifier with Emitter Degeneration




1.) SS model parameters

$$r_{\pi} = \frac{\beta_o}{g_m} = \frac{\beta_o V_T}{I_C} = \frac{100 \cdot 25mV}{0.245mA} = 10.2k\Omega$$

$$r_o = \frac{V_A + V_{CE}}{I_C} \rightarrow \infty \quad \frac{53V}{0.245mA} \approx 100k\Omega$$



2.) Small

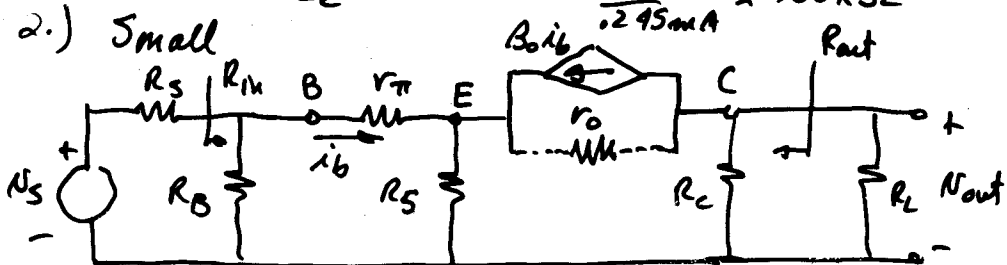

$$R_B = R_1 \parallel R_2 = 104.35k\Omega$$

BJT Example - cont'd

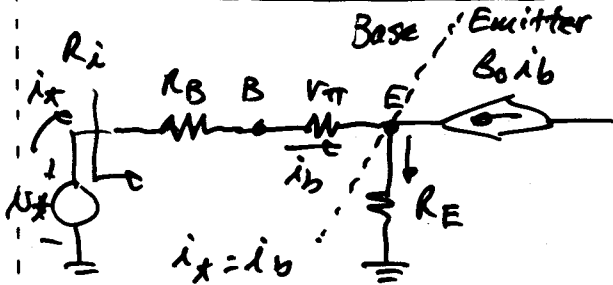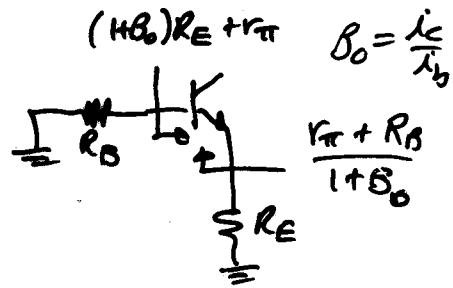
$$R_{in} = R_B \parallel [r_{\pi} + (1 + \beta_0) R_E]$$



Impedance transformation

$$N_x = i_b [R_B + r_{\pi} + R_E (1 + \beta_0)]$$
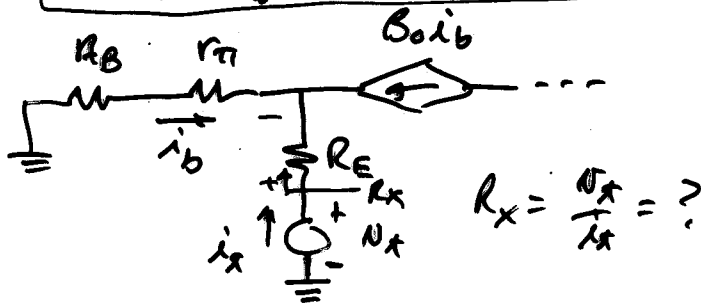
$$\therefore R_i = \frac{N_x}{i_x} = \frac{N_x}{i_b} = R_B + r_{\pi} + R_E (1 + \beta_0)$$



$$N_x = - (1 + \beta_0) i_b R_E - i_b (r_{\pi} + R_B)$$

$$N_x = - i_b [r_{\pi} + R_B + (1 + \beta_0) R_E]$$

$$= - i_b \frac{(1 + \beta_0)}{(1 + \beta_0)} [r_{\pi} + R_B + (1 + \beta_0) R_E] = i_x \left[R_E + \frac{r_{\pi} + R_B}{1 + \beta_0} \right]$$

$$\therefore \frac{N_x}{i_x} = R_x = R_E + \frac{r_{\pi} + R_B}{1 + \beta_0}$$

Base-Emitter Impedance Reflection Principle:

1. Resistance looking into the base is r_{π} plus $(1 + \beta_0)$ times the resistance from the emitter to ground.
2. Resistance looking into the emitter is r_{π} plus the resistance from the base to ground, both divided by $(1 + \beta_0)$