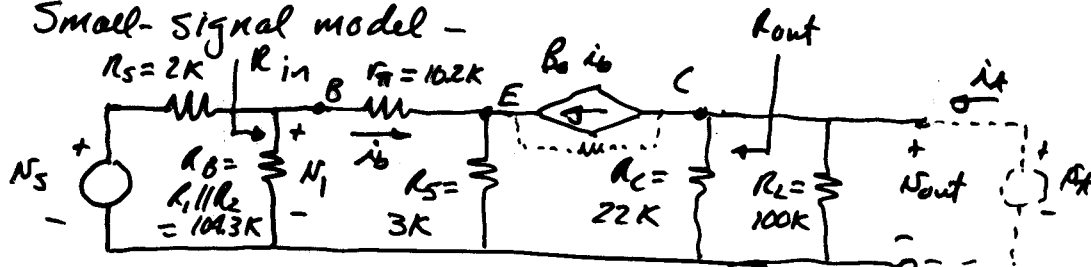


Common Emitter Amplifier with Emitter Degeneration - Cont'd

Small-signal model -



$$R_{in} = R_B \parallel [r_{\pi} + (1 + \beta_0) R_E] = 104.3K \parallel [10.2K + (101) 3K] = 104.3K \parallel 313.2K$$

$$R_{out} = R_C \parallel R_L = 22K \parallel 100K = 78.3K$$

$$\frac{N_{out}}{N_S} = \left(\frac{N_{out}}{i_b} \right) \left(\frac{i_b}{N_S} \right) = [-\beta_0 \times (R_C \parallel R_L)] \left(\frac{i_b}{N_S} \right) \left(\frac{N_1}{N_S} \right)$$


$$\therefore \frac{i_b}{N_1} = \frac{1}{r_{\pi} + (1 + \beta_0) R_E} = \frac{1}{313.2K}, \quad \frac{N_1}{N_S} = \frac{R_{in}}{R_S + R_{in}}$$

$$\frac{N_1}{N_S} = \frac{R_B \parallel [r_{\pi} + (1 + \beta_0) R_E]}{R_S + R_B \parallel [r_{\pi} + (1 + \beta_0) R_E]}$$



$$\frac{N_{out}}{N_S} = [-100 (18.03K)] \left(\frac{1}{313.2K} \right) \left(\frac{78.3K}{2 + 78.3K} \right) = -5.61 V/V$$

$$\frac{i_b}{N_S} = ? \quad i_b = \frac{N_S}{R_S + R_{in}} \times \frac{R_B}{R_B + r_{\pi} + (1 + \beta_0) R_E}$$

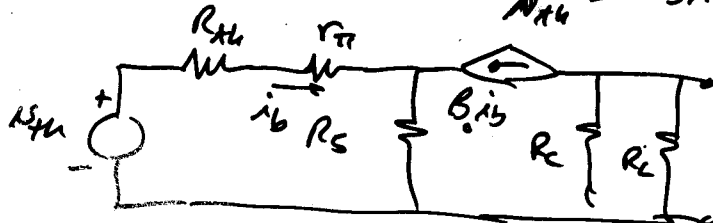Text calculates $\frac{N_{out}}{N_{TH}} = -5.72 V/V$ 

$$N_{TH} = \frac{R_B}{R_B + R_S} N_S$$

$$\frac{N_{out}}{N_{TH}} \approx -\frac{R_C}{R_E}$$

Q5 -





Next Example - Common Drain Amplifier

~~CE & CS~~

CC & CD

CB & CG

Common nothing & Last example
 (Source degeneration or emitter degeneration)

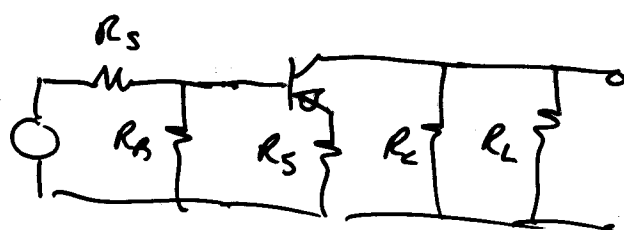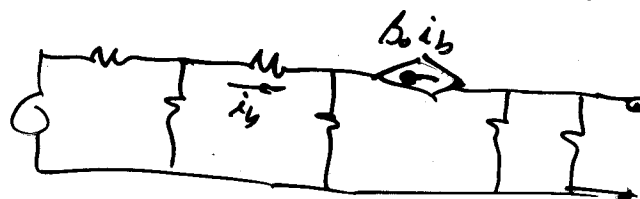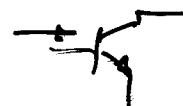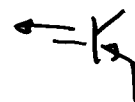 $1\mu A \rightarrow 1.1\mu A$  $1.1\mu A - 1\mu A$ 

TH