

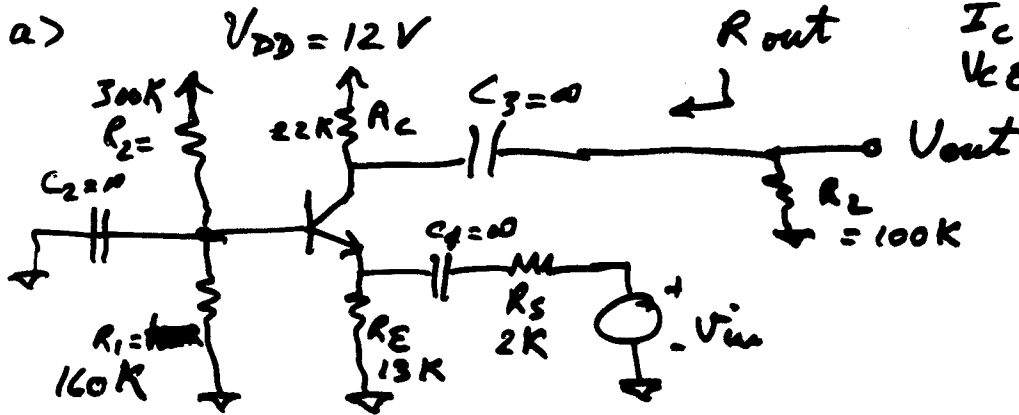


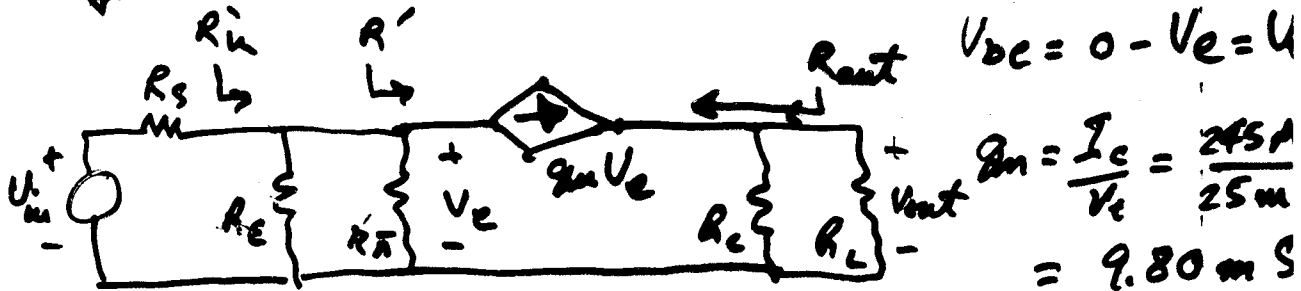1) COMMON BASE AMPLIFIER

$\beta_F = 100$
 $V_A = 50V$
 $I_C = 245\mu A$
 $V_{CE} = 3.4V$



b) SMALL SIGNAL MODEL :

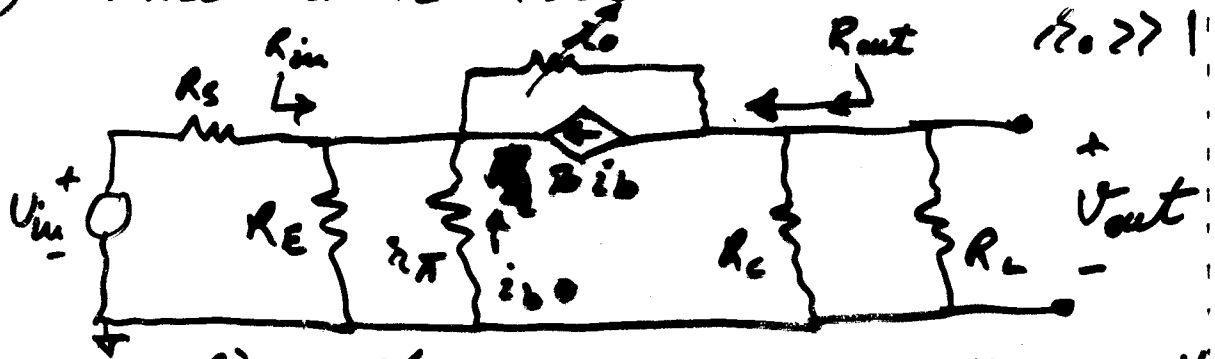


$$\beta_m = \frac{I_C}{V_{CE}} = \frac{245\mu A}{25mV} = 9.80mS$$

$$r_o = \frac{V_A}{I} = 204K$$

$$R_{in} = R_E \parallel R'$$

$$R' = \frac{V_{CE}}{i_c}$$

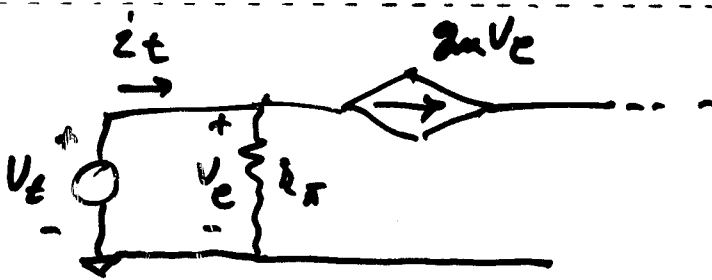

$$i_t = \frac{V_t}{r_g} + g_m V_t = V_t \left(\frac{1}{r_g} + g_m \right)$$


$$\therefore R' = \frac{1}{\frac{1}{r_g} + g_m} = \frac{r_g}{1 + g_m r_g} \approx \frac{1}{g_m} = 102 \Omega$$

$$R_{in} = 13K // 102 \Omega = 101 \Omega$$

$$\frac{V_{out}}{V_{in}} = \left(\frac{V_{out}}{V_{gs}} \right) \left(\frac{V_{gs}}{V_{in}} \right) = (g_m R_c // R_L) \cdot \left(\frac{R_{in}}{R_{in} + R_s} \right)$$

$$\frac{V_{out}}{V_{in}} = 8.48 \left\{ V/V \right\}$$

d) OUTPUT RESISTANCE

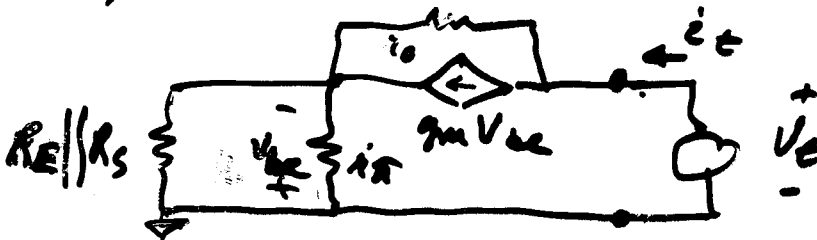

$$V_t = (i_t - g_m V_{gs}) r_o - V_{gs} = r_o i_t - V_{gs} (1 + g_m r_o)$$

$$-V_{gs} = i_t (r_g // R_E // R_S)$$


$$\therefore V_t = \left\{ r_o + (r_g // R_E // R_S) (1 + g_m r_o) \right\} i_t$$

$$R_{out} = \frac{V_t}{i_t} = r_o + (r_g // R_E // R_S) (1 + g_m r_o) \approx g_m r_o (r_g // R_E // R_S) + r_o$$

$$R_{out} = 3.166 M\Omega$$

2) COMMON GATE AMPLIFIER

$C_{1,2,3} = \infty$

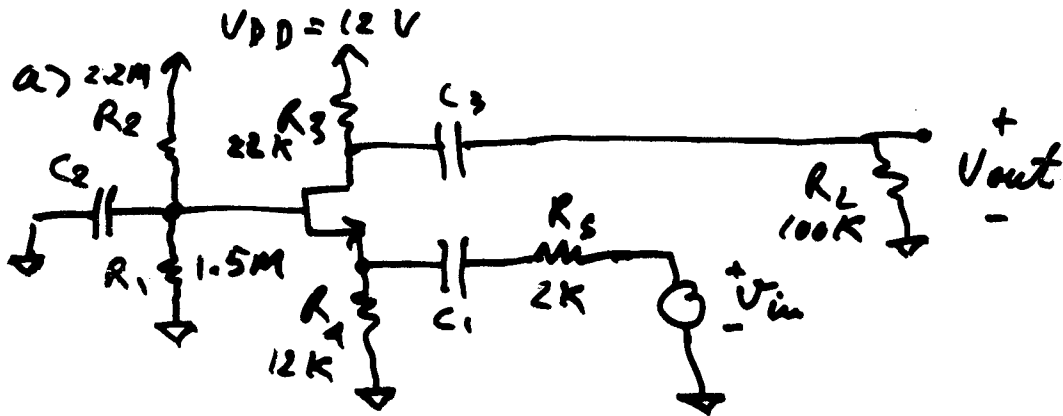

$K_n = 500 \mu A/V^2$, $V_{TN} = 1V$, $\lambda = 0.02 V^{-1}$
 $I_{DS} = 241 \mu A$, $V_{DS} = 3.8V$


b) $g_m = \sqrt{2 K_n I_{DS} (1 + \lambda V_{DS})} = 509 \mu S$

$r_o = \frac{1}{\lambda} + \frac{V_{DS}}{I_{DS}} = 223 K\Omega$

c) SMALL SIGNAL (NEGLECT r_o)



$R_{in} = \frac{V_t}{i_t}$

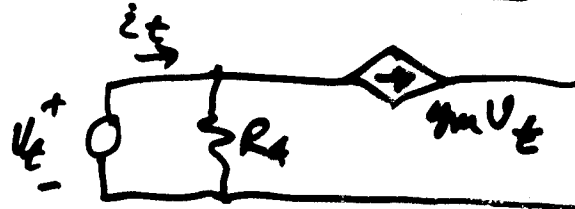


$i_t = \frac{V_t}{R_4} + g_m V_t \rightarrow R_{in} = \frac{1}{\frac{1}{R_4} + g_m} \approx \frac{1}{g_m}$

$$R_{in} = \frac{1}{50 \mu S} = \underline{1.96 \text{ k}\Omega}$$

~~$$R_{out} = R_3 = 22 \text{ k}\Omega$$~~
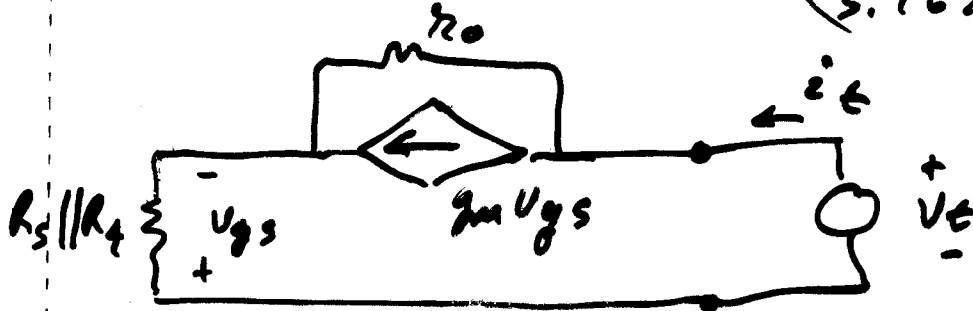
$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \left(\frac{V_{out}}{V_{gs}} \right) \left(\frac{V_{gs}}{V_{in}} \right) = -(g_m R_3 \parallel R_2) \left(-\frac{R_{in}}{R_{in} + R_s} \right) \\ &= (0.509) (18) \left(\frac{1.96}{3.96} \right) = 4.54 \text{ [V/V]} \end{aligned}$$



$$V_t = (i_t - g_m V_{gs}) r_o - V_{gs}$$

$$V_t = i_t r_o - V_{gs} (1 + g_m r_o)$$

$$V_t = i_t \left\{ r_o + R_s \parallel R_4 (1 + g_m r_o) \right\}$$

$$R_{out} = r_o + R_s \parallel R_4 (1 + g_m r_o)$$

$$= 416 \text{ k}\Omega$$