

Homework #7 is nominally due today (will accept on 2/25)

Topics Ahead -

Amplifiers - small-signal

Differential amplifiers


Frequency response ($C \neq \infty$)

Feedback

Design Example

Design a single-transistor amplifier to meet the following specs:

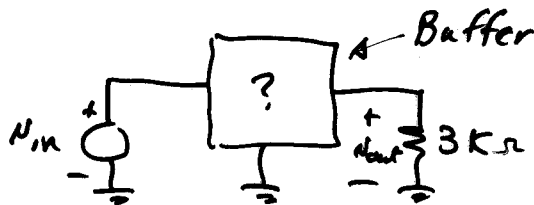$R_{in} \geq 20M\Omega$, $A_v \geq 0.85$ with an external load of $3K\Omega$




1.) Obviously the correct configuration is CC or CD. Which one?

R_{in} is no problem for the MOSFET

$R_{in}(BJT) = (1+\beta)R_L = (1+\beta)3K = 20M\Omega$

$\beta \approx \frac{20M}{3K} = 6667$ (beta too large)

∴ Choose the CD configuration

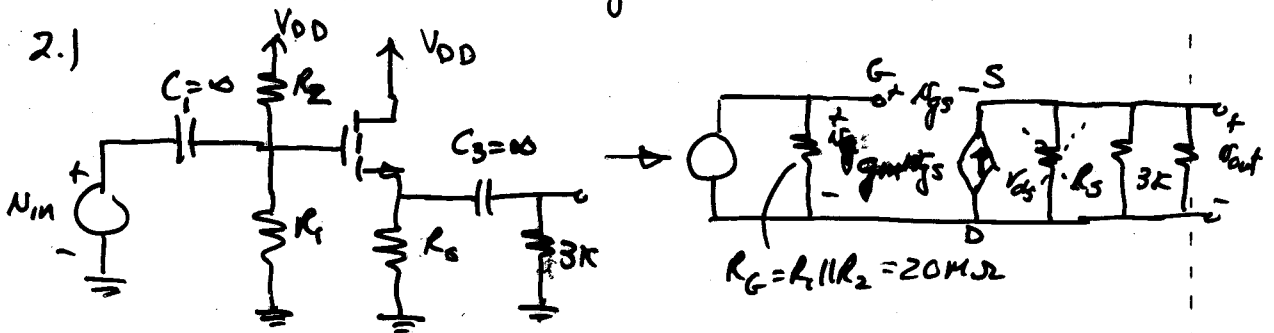

Voltage gain -

$$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{N_{gs}} \right) \left(\frac{N_{gs}}{N_{in}} \right), \quad \frac{N_{out}}{N_{gs}} = g_m (R_S \parallel 3K)$$

$$N_{gs} = N_g - N_s = N_{in} - N_{out} = N_{in} - g_m (R_S \parallel 3K) N_{gs}$$

$$N_{gs} [1 + g_m (R_S \parallel 3K)] = N_{in}$$

$$\frac{N_{out}}{N_{in}} = \frac{g_m (R_S \parallel 3K)}{1 + g_m (R_S \parallel 3K)} \geq 0.85 \rightarrow g_m (R_S \parallel 3K) \geq 5.67$$

Choosing $R_S = 3k\Omega \rightarrow g_m \geq 3.78 \text{ mS}$

3.) Examine the MOSFET

Range of I_{DS} -

$$g_m = \sqrt{2K_n I_{DS}}$$

Data sheet gives,

K_n is from 0.1 to $20 \frac{\text{mA}}{\text{V}^2}$


Choosing $K_n = 10 \text{ mS}$ & knowing that $V_{TN} = 1\text{V}$

Then, $I_{DS} = \frac{K_n}{2} (V_{GS} - V_{TN})^2 \rightarrow V_{GS} = \sqrt{\frac{2I_{DS}}{K_n}} + V_{TN}$

Also if $K_n = 10 \text{ mS}$ and $g_m \geq 3.78 \text{ mS}$


$$\therefore I_{DS} = \frac{g_m^2}{2K_n} = 0.714 \text{ mA} \rightarrow 1 \text{ mA}$$
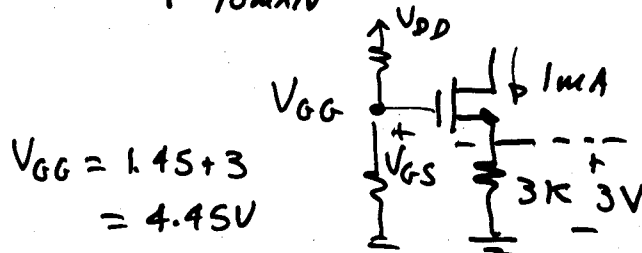
$$\therefore V_{GS} = \sqrt{\frac{2 \cdot 1 \text{ mA}}{10 \text{ mA/V}^2}} + 1 = 1.45 \text{ V}$$



Choosing $R_1 \parallel R_2 = 20 \text{ M}\Omega \Rightarrow R_1 = R_2 = 40 \text{ M}\Omega$
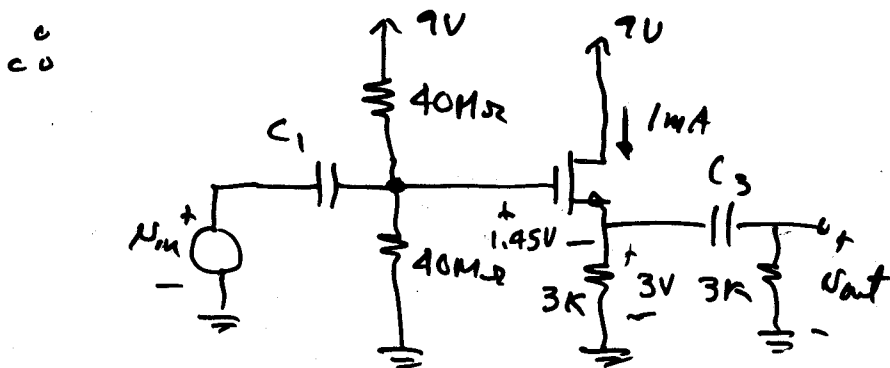
$$V_{DD} = 2 \times 4.45 \text{ V} = 8.9 \text{ V} \rightarrow \underline{9 \text{ V}}$$



$$\frac{N_{out}}{N_{in}} = \frac{g_m(1.5k)}{1 + g_m(1.5k)} = \frac{15}{1 + 15} = \frac{15}{16} \approx 0.85 \checkmark$$


CHAPTER 15 - MULTISTAGE AMPLIFIERS

Multi-stage Example

Darlington

Diff. amps.

Multi-stage Amplifier Example

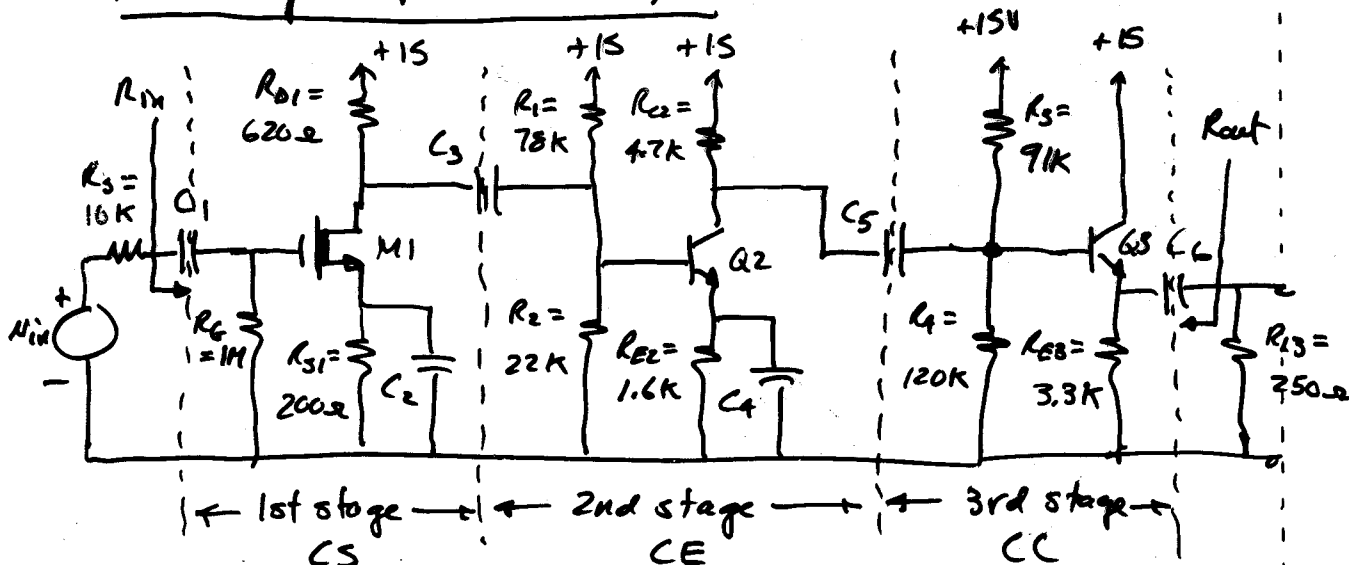

Transistor Parameters:

\$M_1\$: \$K_n = 10 \text{ mA/V}^2\$, \$V_{TN} = -2 \text{ V}\$, \$\lambda = 0.02 \text{ V}^{-1}\$

\$Q_2\$: \$\beta_o = \beta_f = 150\$, \$V_A = 80 \text{ V}\$, \$V_{BE} = 0.6 \text{ V}\$

\$Q_3\$: \$\beta_f = 80\$, \$V_A = 60 \text{ V}\$, \$V_{BE} = 0.6 \text{ V}\$

Q-point & SS model parameters

$$M1: I_{D1} = 5 \text{ mA}, V_{D1} = 10.9 \text{ V} \rightarrow g_{m1} = 10 \text{ mS} \quad \& \quad r_{\pi} = 12.2 \text{ k}\Omega$$

$$Q2: I_{C2} = 1.57 \text{ mA}, V_{CE2} = 5.09 \text{ V} \rightarrow g_{m2} = 62.5 \text{ mS}, r_{\pi 2} = 2.39 \text{ k}\Omega$$

$$r_{o2} = 54.2 \text{ k}\Omega$$

$$Q3: I_{C3} = 1.99 \text{ mA}, V_{CE3} = 8.36 \text{ V} \rightarrow g_{m3} = 79.6 \text{ mS}$$

$$r_{\pi 3} = 1 \text{ k}\Omega$$

$$r_{o3} = 34.4 \text{ k}\Omega$$