
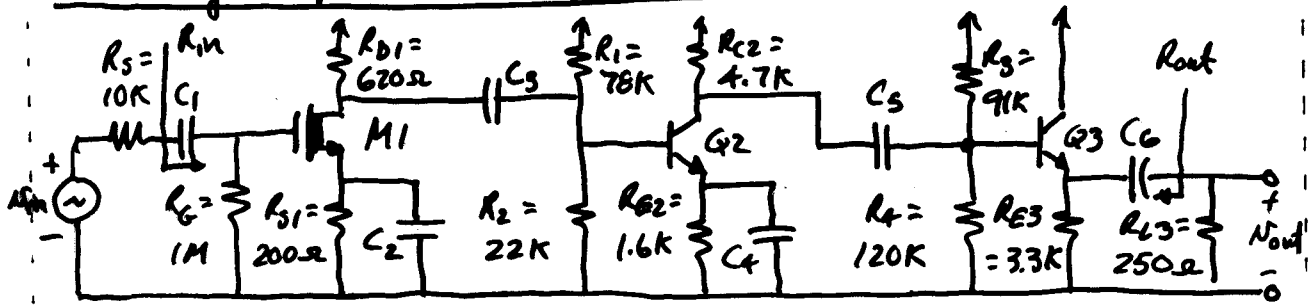



Multistage Amplifier Example - Cont'd

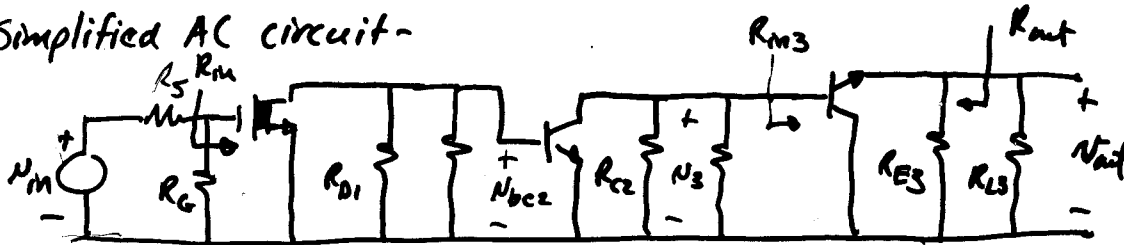

Simplified AC circuit -



Small-signal circuit -

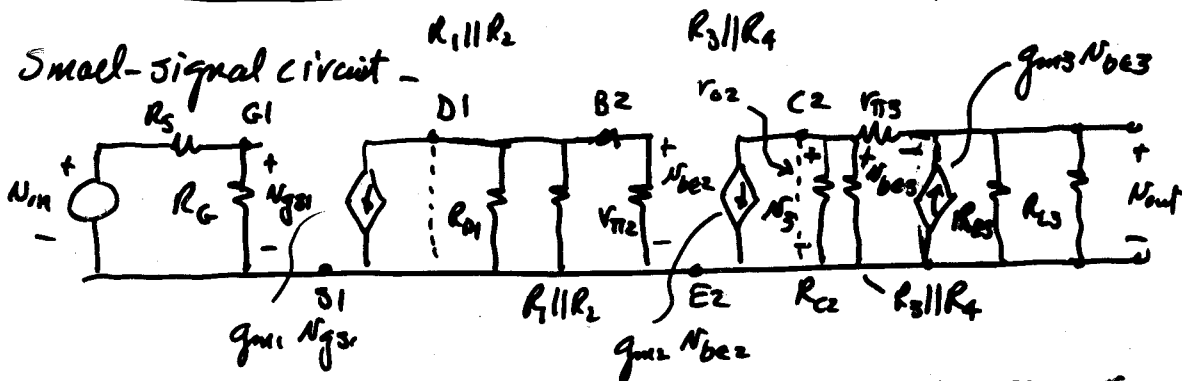

$$R_{in} = R_g = 1M\Omega$$

$$R_{out} = R_{E3} \parallel \left[\frac{r_{\pi 3} + R_{C2} \parallel R_3 \parallel R_4}{1 + \beta_3} \right]$$


$$= 3.3K \parallel \left[\frac{1K + 4.7K \parallel 51.75K \parallel 54.2K}{\beta_3} \right]$$

$$= 60.4\Omega$$

$$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{N_{be3}} \right) \left(\frac{N_{be3}}{N_3} \right) \left(\frac{N_3}{N_{be2}} \right) \left(\frac{N_{be2}}{N_{gs1}} \right) \left(\frac{N_{gs1}}{N_{in}} \right)$$

$$\frac{N_{out}}{N_{be3}} = \frac{(1 + \beta_3)(R_{E3} \parallel R_{L3})}{r_{\pi 3}}$$
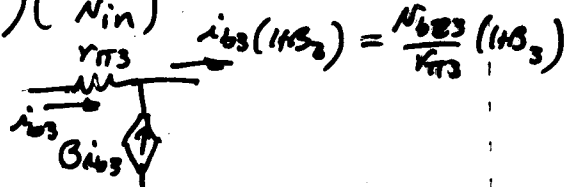
$$= \left(\frac{1}{r_{\pi 3}} + g_{m3} \right) (R_{E3} \parallel R_{L3}) = 18.82 V/V$$



$$R_{in3} = r_{\pi 3} + (1 + \beta_3) [R_{E3} \parallel R_{L3}] = 19.82 K\Omega$$

$$\frac{r_{\pi 3}}{R_{in3}} = \frac{1}{19.82}$$

Cont'd -

$$\frac{N_3}{N_{be2}} = -g_{m2} [r_{o2} \parallel R_{c2} \parallel R_3 \parallel R_4 \parallel R_{in3}] = -62.8 (3.322) = -208.6 \text{ V/V}$$

$$\frac{N_{be2}}{N_{gs1}} = -g_{m1} [r_{o1} \parallel R_{o1} \parallel R_1 \parallel R_2 \parallel r_{\pi2}] = -10 \text{ mS} (0.4781 \text{ k}\Omega) = -4.786 \text{ V/V}$$

$$\frac{N_{gs1}}{N_{in}} = \frac{R_G}{R_S + R_G} = \frac{1}{1.01}$$

$$\therefore \frac{N_{out}}{N_{in}} = (12.82) \left(\frac{1}{19.82}\right) (-208.6) (-4.786) \left(\frac{1}{1.01}\right) = 938.6 \text{ V/V}$$

Input signal -

Find the max. input to keep the amplifier in "small signal"

~~Step 1:~~

FET

BJT

For "s.s.", $N_{gs1} \leq 0.2 (V_{GS} - V_T)$ or $N_{be} \leq 5 \text{ mV}$

Stage 1:

$$N_{gs1} \leq 0.2 (V_{GS1} - V_T) = 0.2 [-5 \text{ mA} \times 200 \Omega - (-2)] = 0.2 [-1 + 2] = 0.2 \text{ V}$$

$$N_{in} = 1.01 (0.2) = 0.202 \text{ V} \leftarrow \text{max input to keep M1 "small signal"}$$

Stage 2:

$$N_{be2} \leq 5 \text{ mV}$$

$$\frac{N_{be2}}{N_{in}} = 4.786 \rightarrow N_{in}(\text{max}) = \frac{5 \text{ mV}}{4.786}$$


$$N_{in}(\text{max}) = 1.06 \text{ mV}$$

Stage 3:

$$N_{be3} \leq 5 \text{ mV}$$


$$N_{in}(\text{max}) = \frac{5 \text{ mV}}{\left(\frac{N_{be3}}{N_3}\right) \left(\frac{N_3}{N_{be2}}\right) \left(\frac{N_{be2}}{N_{gs1}}\right) \left(\frac{N_{gs1}}{N_{in}}\right)} \approx 0.1 \text{ mV}$$

$$\therefore |N_{in}| < 0.1 \text{ mV} \Rightarrow \text{max } V_{out} = 938.6 (0.1 \text{ mV})$$

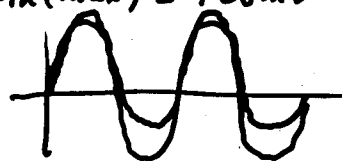


Direct Coupled Amplifiers

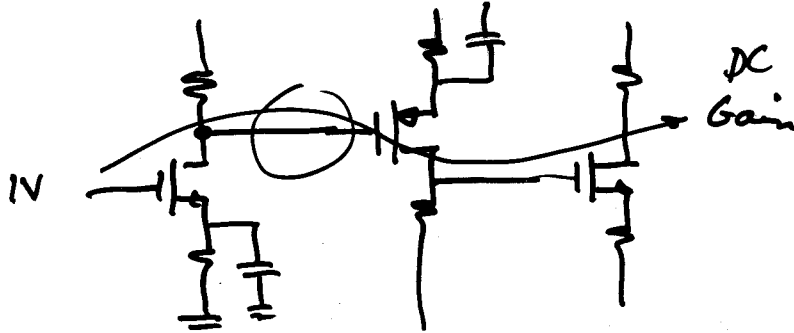Amplifiers that don't use coupling capacitors.



Darlington Circuit

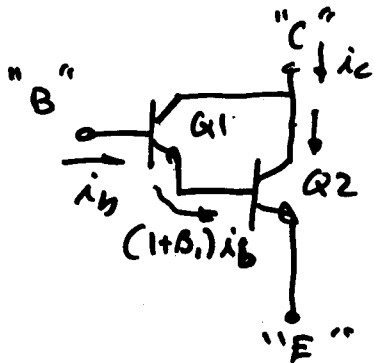A BJT circuit to increase the CE current gain





$$i_c = i_{c1} + i_{c2} = \beta_1 i_b + (1 + \beta_1) i_b \beta_2$$

$$i_c \approx \underline{\underline{(1 + \beta_1) \beta_2 i_b}}$$

Diff. Amps

This page includes material that is important but skipped in lecture 2/25/04

Darlington Amplifier

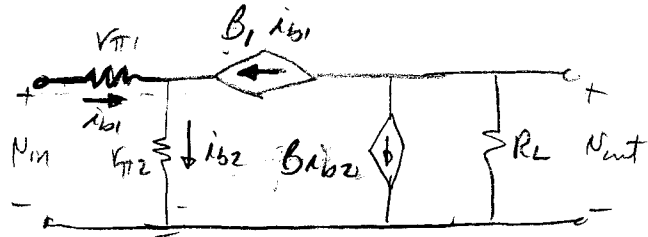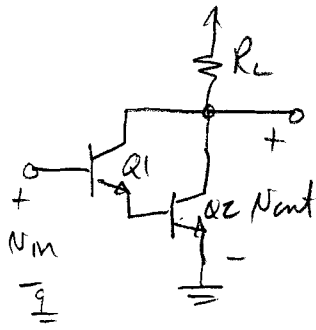

$$N_{out} = -\beta_1 i_{b1} R_L = \beta_2 i_{b2} R_L$$

$$N_{in} = i_{b1} r_{\pi 1} + (1 + \beta_1) i_{b1} r_{\pi 2} \rightarrow i_{b1} = \frac{N_{in}}{r_{\pi 1} + (1 + \beta_1) r_{\pi 2}}$$

$$i_{b2} = i_{b1} (1 + \beta_1)$$

$$\therefore N_{out} = -\beta_1 R_L i_{b1} - \beta_2 (1 + \beta_1) R_L i_{b1}$$

$$\therefore N_{out} = \left[-\beta_1 R_L - \beta_2 (1 + \beta_1) R_L \right] \frac{N_{in}}{r_{\pi 1} + (1 + \beta_1) r_{\pi 2}}$$

$$R_L = 10K$$

$$\beta = 100$$

$$r_{\pi} = 1K$$

$$\frac{N_{out}}{N_{in}} = \frac{-[\beta_1 + \beta_2 (1 + \beta_1)] R_L}{r_{\pi 1} + (1 + \beta_1) r_{\pi 2}}$$

$$r_{\pi 1} = \frac{\beta_1 V_T}{I_{C1}} \quad \& \quad r_{\pi 2} = \frac{\beta_2 V_T}{I_{C2}}$$

$$\therefore \frac{N_{out}}{N_{in}} \approx \frac{-\beta_2 \beta_1 R_L}{2 r_{\pi}} = \frac{10^4 \cdot 10^4}{2(1K)} = 5 \times 10^4$$

$$r_{\pi 2} = \frac{\beta_2 V_T}{(1 + \beta_1) I_{C1}} = \frac{r_{\pi 1}}{1 + \beta_1}$$


$$R_{in} = r_{\pi 1} + (1 + \beta_1) r_{\pi 2}$$

$$R_{out} = R_L$$

$$= 102K$$

Cascode Amplifier

Increases "r_o"

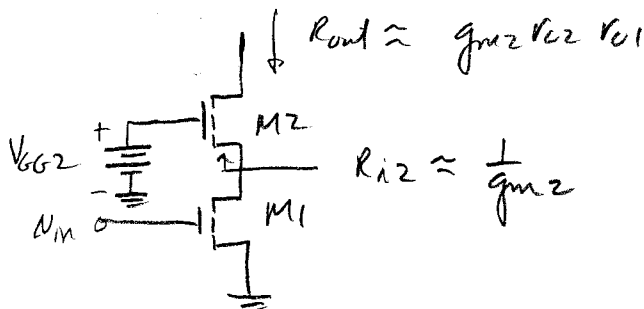

$$R_{out} \approx g_{m2} r_{o2} r_{o1}$$

$$r_{i2} \approx \frac{1}{g_{m2}}$$

(depends on where drain is connected)