
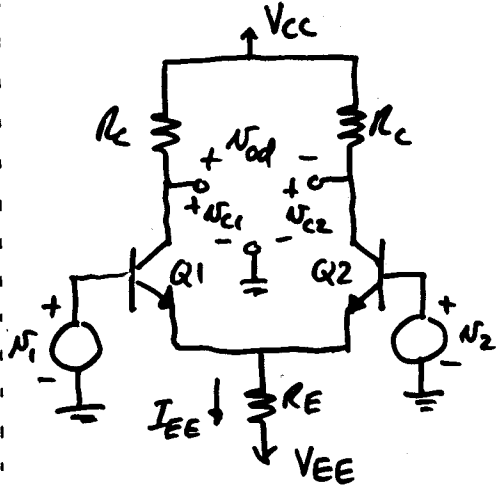


Differential Amplifiers

BJT Circuit:

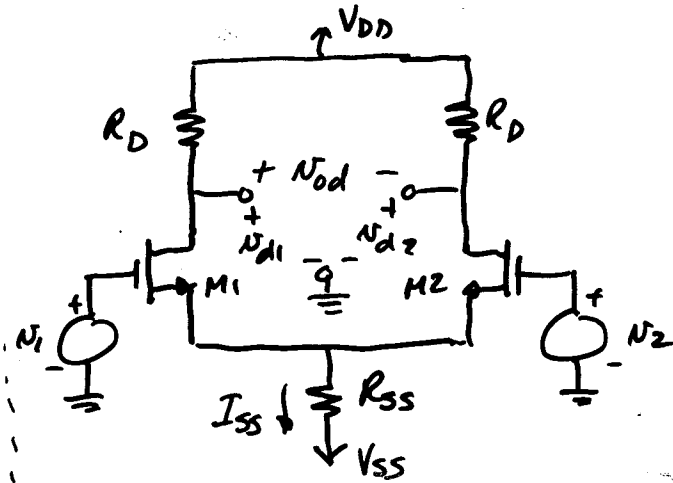

MOS Circuit:



DC Analysis:

Assume that $N_1 = N_2 = 0$

$$I_{EE} = \frac{|V_{EE}| - V_{BE}}{R_E}$$

$$I_{E1} = I_{E2} = \frac{I_{EE}}{2}$$


$$I_{C1} = I_{C2} = \alpha I_E$$

$$I_{SS} = \frac{|V_{SS}| - V_{GS}}{R_{SS}}$$

$$I_{D1} = I_{D2} = \frac{I_{SS}}{2}$$

MOS Diff. Amp Example

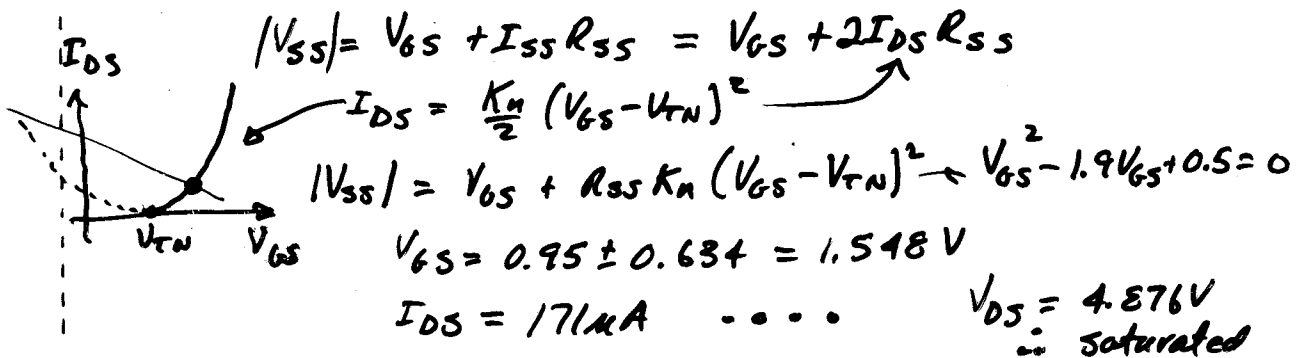
$V_{DD} = 5V, V_{SS} = -5V, R_S = 10K, R_D = 10K, K_n = 1mA/V^2, V_{TN} = 1V$
 ($N_1 = N_2 = 0$)



AC Analysis of Diff. Amps

Two modes of operation:

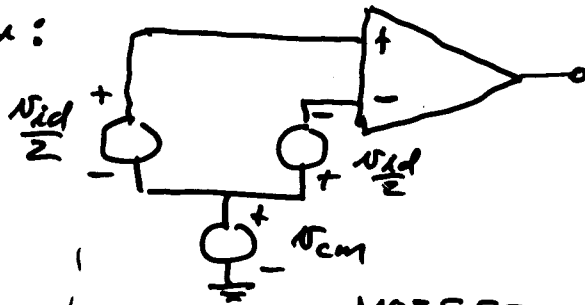- 1.) Differential (N_{id})
- 2.) Common (N_{cm})





BJT



MOSFET

Differential Mode Analysis:

AC equivalent ckt:

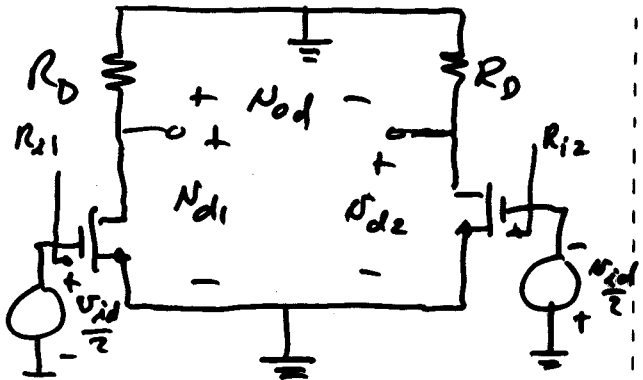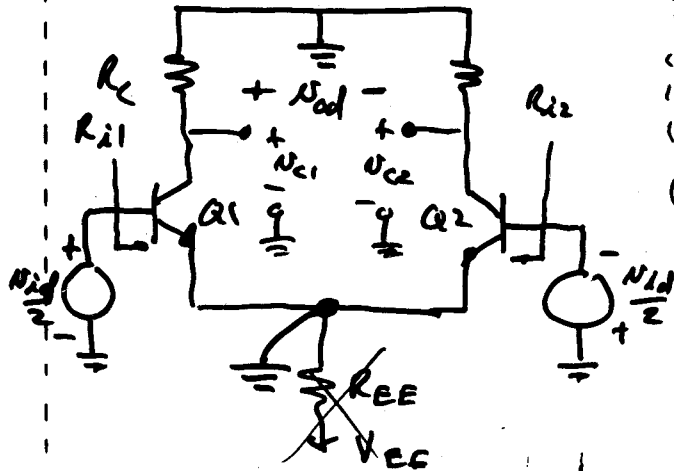

M2:

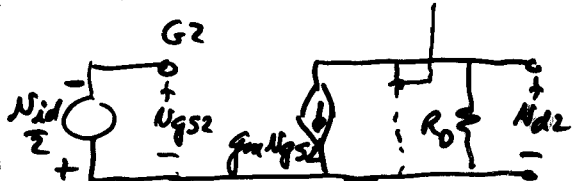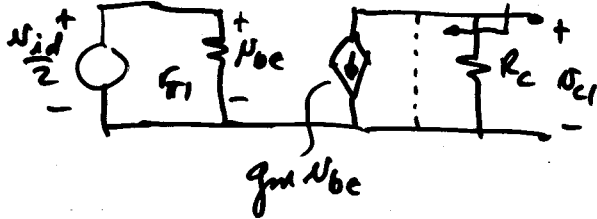

$$N_{c1} = -g_m R_c \frac{N_{id}}{2}$$

$$\frac{N_{c1}}{N_{id}} = -\frac{g_m R_c}{2}$$

$$\frac{N_{c2}}{N_{id}} = +\frac{g_m R_c}{2}$$

$$\frac{N_{od}}{N_{id}} = \frac{N_{c1}}{N_{id}} - \frac{N_{c2}}{N_{id}} = -g_m R_c$$


$$N_{d2} = +g_m R_D \frac{N_{id}}{2}$$

$$\frac{N_{d2}}{N_{id}} = +\frac{g_m R_D}{2}$$

$$\frac{N_{d1}}{N_{id}} = -\frac{g_m R_D}{2} \left(\frac{r_{o1}}{r_{o1} + R_D} \right)$$

$$\frac{N_{od}}{N_{id}} = -g_m R_D$$

What is R_{id} ?

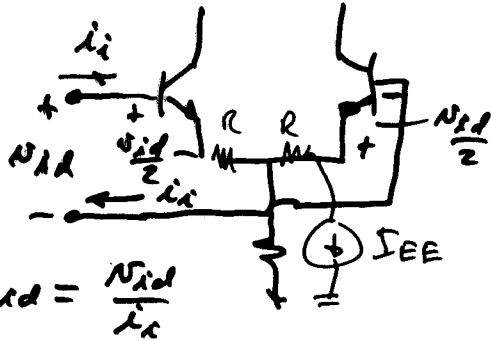


$$R_{id} = \frac{N_{id}}{i_i}$$

$$R_{id} = R_{e1} + R_{e2} = 2R$$

$$R_{o1} \approx R_c \quad R_{o2} \approx R_c$$


$$R_{od} = 2R_c$$

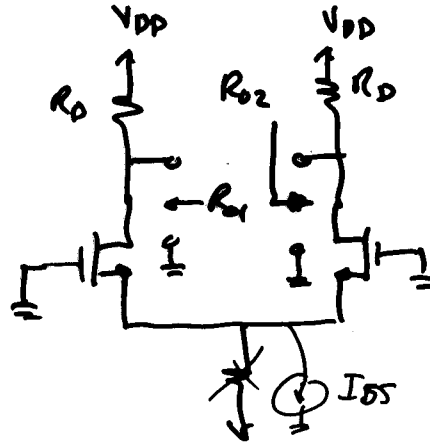

$$R_{o1} = R_{D1} || r_{o1} \approx R_{D1}$$

$$R_{o2} = R_{D2} || r_{o2} \approx R_{D2}$$



$$R_{od} = ? = \frac{N_A}{i_A}$$

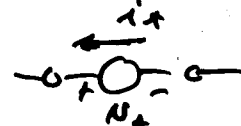



$$R_{od} = R_{o1} + R_{o2}$$

Common Mode Analysis of Diff. Amps

Common half circuit is:

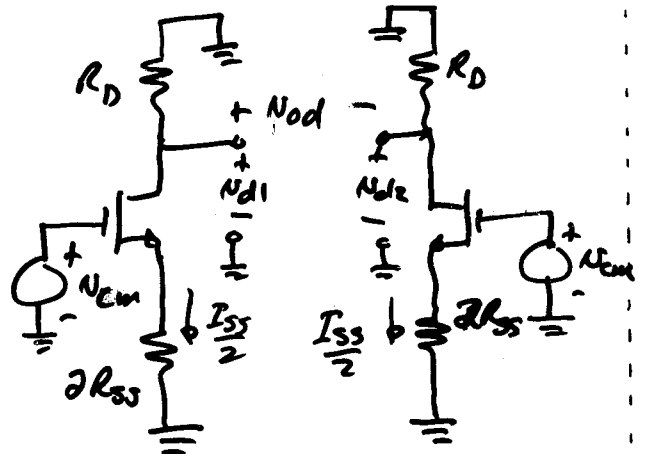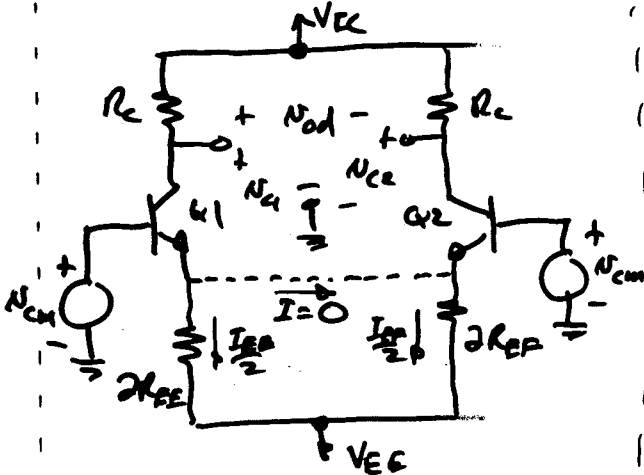

Small signal analysis -

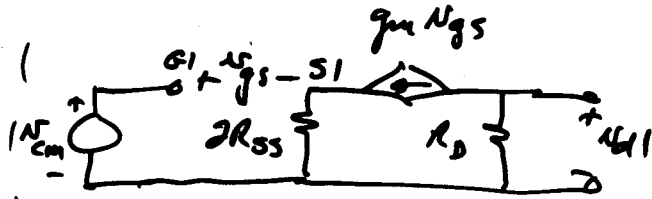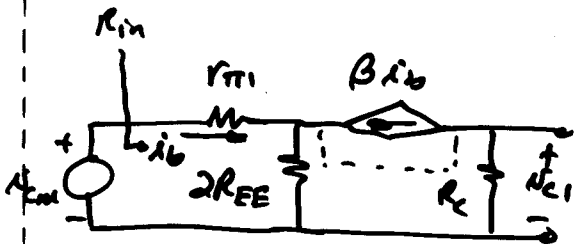

$$\frac{N_{c1}}{N_{cm}} = \left(\frac{N_{c1}}{i_b}\right) \left(\frac{i_b}{N_{cm}}\right)$$

$$= (-\beta R_c) \left(\frac{1}{r_{\pi} + (1+\beta)2R_{EE}}\right)$$

$$= \frac{-\beta R_c}{r_{\pi} + (1+\beta)2R_{EE}}$$

$$\frac{N_{c2}}{N_{cm}} = \frac{N_{c1}}{N_{cm}} \Rightarrow \frac{N_{od}}{N_{cm}} = 0$$

(Assume everything matches)

$$\frac{N_{d1}}{N_{cm}} = \left(\frac{N_{d1}}{v_{gs}}\right) \left(\frac{v_{gs}}{N_{cm}}\right)$$

$$= (-g_m R_D) \left(\frac{1}{1 + 2R_{SS}g_m}\right)$$

$$N_{gs} = N_g \cdot N_s = N_{cm} - 2R_{SS}g_m N_{gs}$$

$$N_{gs} [1 + 2R_{SS}g_m] = N_{cm}$$

$$\frac{N_{d1}}{N_{cm}} = \frac{-g_m R_D}{1 + 2R_{SS}g_m} = \frac{N_{d2}}{N_{cm}}$$

CMRR (common mode rejection ratio)

$$CMRR = \frac{\left|\frac{N_{c1}}{N_{id}}\right|}{\left|\frac{N_{c1}}{N_{cm}}\right|} = \frac{\left|\frac{N_{d1}}{N_{id}}\right|}{\left|\frac{N_{d1}}{N_{cm}}\right|}$$

$$\beta = g_m r_{\pi}$$

BJT:

$$CMRR = \frac{g_m R_c / 2}{\frac{\beta R_c}{r_{\pi} + (1+\beta)2R_{EE}}} = \frac{r_{\pi} + (1+\beta)2R_{EE}}{2r_{\pi}} \approx \frac{(1+\beta)2R_{EE}}{2r_{\pi}}$$

$$\boxed{CMRR \approx g_m R_{EE}}$$


Use current sinks to improve CMRR because R_{EE} & R_{SS} become large

MOSFET:

$$CMRR = \frac{g_m R_D / 2}{\frac{g_m R_D}{1 + 2g_m R_{SS}}} = \frac{1 + 2g_m R_{SS}}{2} = \boxed{g_m R_{SS} = CMRR}$$

MOSFET LOW Frequency Example - Cont'd

Small-signal model -

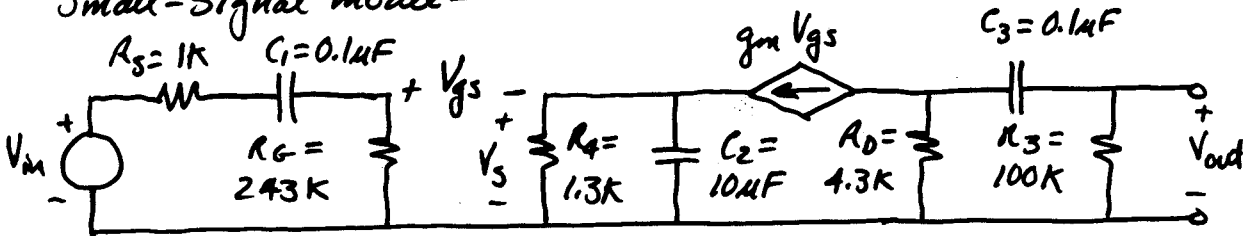


1.) Direct analysis

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{-g_m R_D R_L R_G}{(R_D + R_L)(R_G + R_S)} \left[\frac{s^2 (s + z_2)}{(s + p_1)(s + p_2)(s + p_3)} \right]$$

$$p_1 = \frac{-1}{C_1(R_G + R_S)} = -4 \frac{\text{rads}}{\text{sec}}, \quad z_2 = \frac{-1}{R_4 C_2} = -76.9 \frac{\text{rads}}{\text{sec}}, \quad p_2 = (1 + g_m R_4) z_2$$
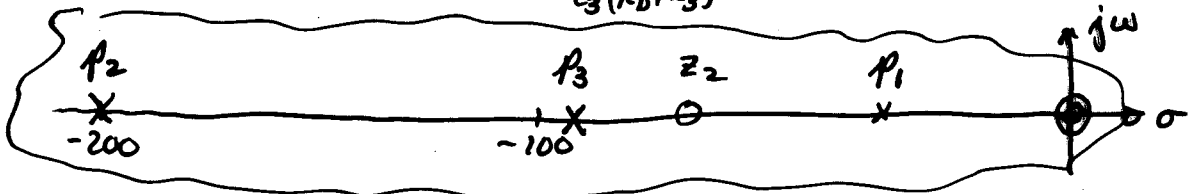
$$p_2 = -200 \frac{\text{rads}}{\text{sec}} \quad \text{and} \quad p_3 = \frac{-1}{C_3(R_D + R_L)} = -95.9 \frac{\text{rads}}{\text{sec}}$$




$\omega_L = ? = \omega_{-3dB}$ (lower) LF Roots


$$a.) \quad f_L = \frac{1}{2\pi} \sqrt{\sum \text{poles}^2 - 2 \sum \text{zeros}^2} = \frac{1}{2\pi} \sqrt{(200)^2 + (95.9)^2 + (4)^2 - 2(76.9)^2}$$

$$= 31.5 \text{ Hz}$$

b.) Bode Plot (Midband Gain = 14dB)

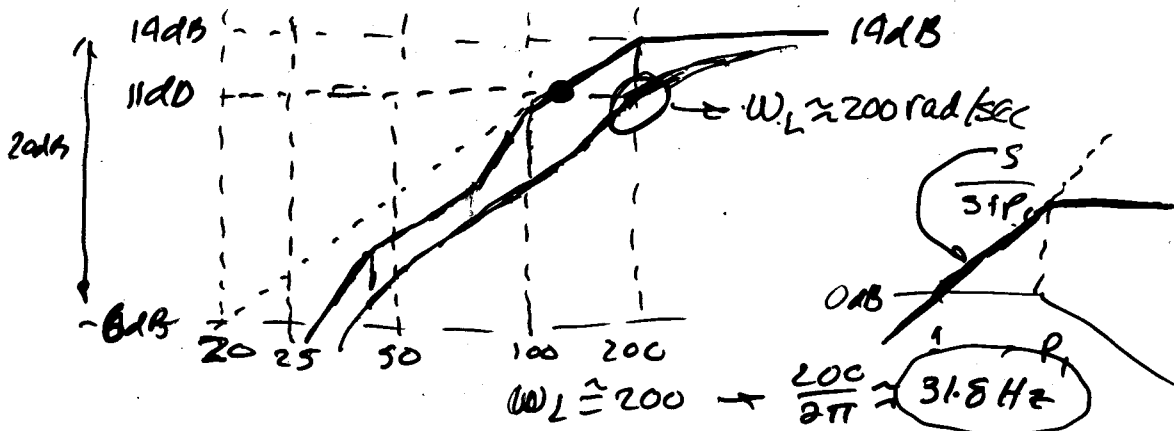

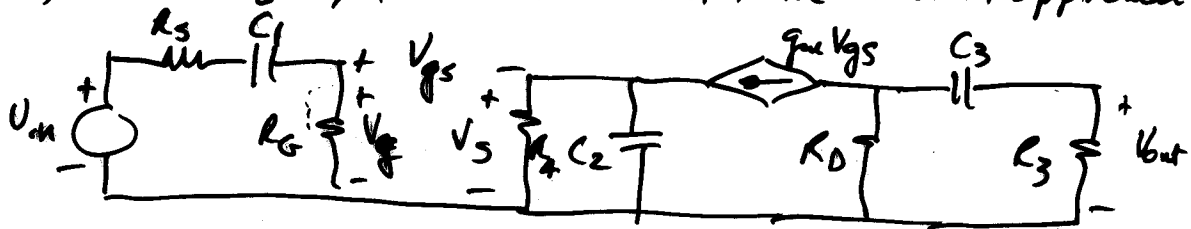
2.) Find ω_L by the short-circuit time constant approach



$$C_1: R_{sc1} = R_s + R_G = 244 \text{ k}\Omega$$

$$\frac{1}{C_1 R_{sc1}} = \frac{1}{(0.1 \mu\text{F})(244 \text{ k}\Omega)} = -41 \text{ rad/sec} = p_1$$
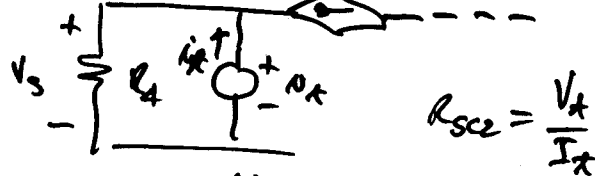
$$C_2: R_{sc2} \quad g_m V_{gs} \quad (V_g = 0) \rightarrow g_m V_{gs} = -g_m V_s$$



$$I_x = \frac{V_x}{R_4} + g_m V_x = V_x \left(\frac{1}{R_4} + g_m \right)$$

$$\therefore R_{sc2} = \frac{1}{g_m + \frac{1}{R_4}} = \frac{1}{g_m} \parallel R_4 = \frac{R_4}{1 + g_m R_4}$$

$$\frac{1}{C_2 R_{sc2}} = \frac{1 + g_m R_4}{R_4 C_2} = |p_2| = 200 \text{ rad/sec}$$

$$C_3: R_{sc3} = R_D + R_L \rightarrow \frac{1}{C_3 R_{sc3}} = |p_3| = +75.9$$

$$\omega_L \approx \frac{1}{R_{sc1} C_1} + \frac{1}{R_{sc2} C_2} + \frac{1}{R_{sc3} C_3} = 337 \text{ rad/sec.}$$

$$f_L = 53.6 \text{ Hz} \quad ???$$

Note: You would have been better off to use this method to find the poles and zeros (I need to show you how to do this) and use the methods used on the last page for finding ω_L .