

CHAPTER 17 - FREQUENCY RESPONSE

Quiz 7 - Diff. Amps

LOW FREQUENCY ANALYSIS

General amplifier response -



$$A_v(s) = \frac{a_0 + a_1s + a_2s^2 + \dots + a_ms^m}{b_0 + b_1s + b_2s^2 + \dots + b_ns^n} \quad m \leq n$$

$$= A_{mb} F_L(s) F_H(s)$$

Good only when there is a region of constant amplitude (wideband)

$$s = \sigma + j\omega$$

Frequency Response

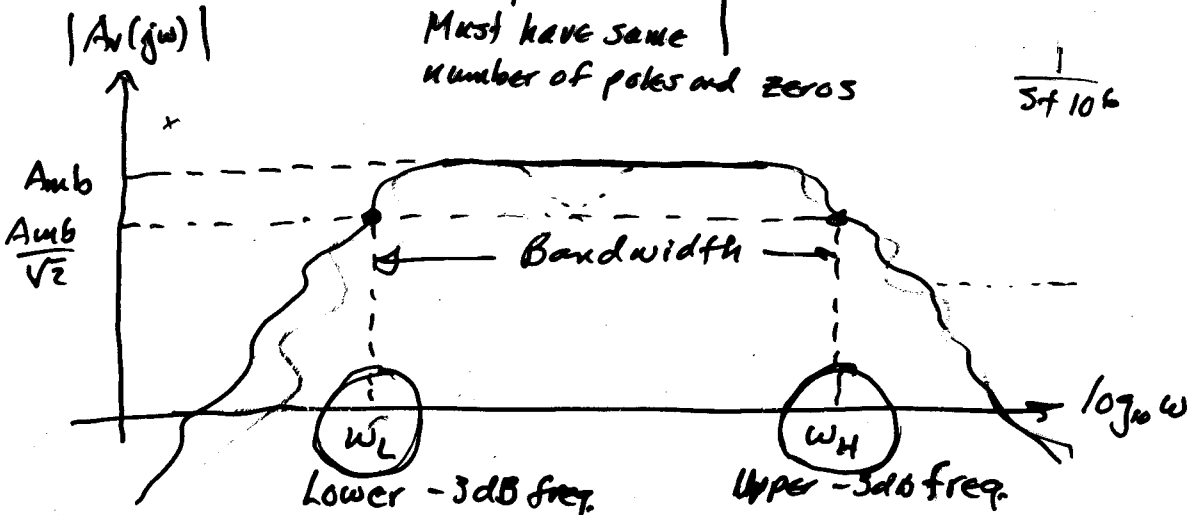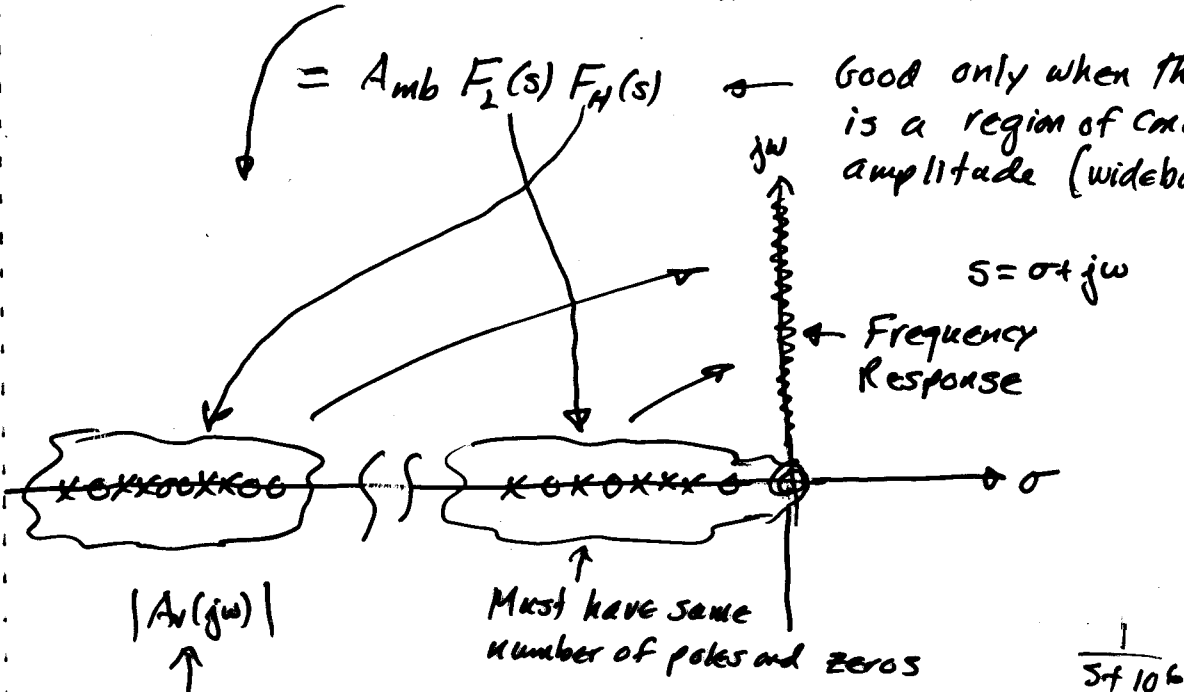


How do we find w_L ?

- 1.) Direct analysis
- 2.) Approximation methods



a.) Dominant pole

$$\omega_L \approx \omega_p(\text{dominant}) \text{ if } |\omega_p(\text{dominant})| \geq 4 (\text{next smallest pole})$$

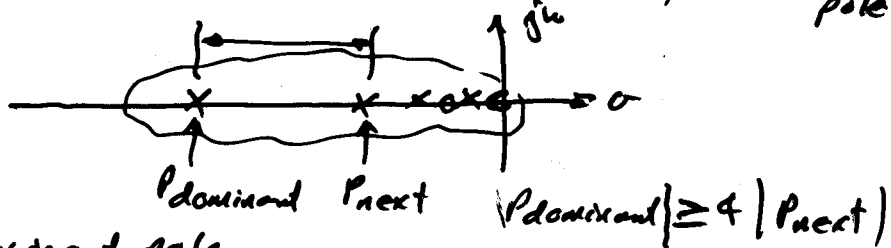

b.) No dominant pole -
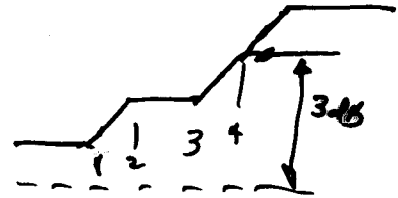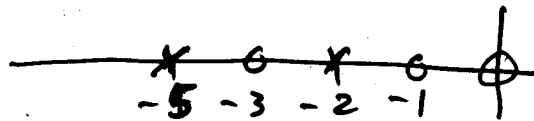
$$\omega_L \approx \sqrt{\sum_n \gamma_n^2 - 2 \sum_j z_j^2}$$



$$\omega_L \approx \sqrt{25 + 4 - 2[9 + 1]} \approx \sqrt{11} \approx 3$$


c.) Bode plot

3.) Short-circuit time constant

$$\omega_L \approx \sum_{i=1}^n \frac{1}{R_{iS} C_i}$$


R_{iS} is the Ther. eq. R seen by C_i with all other capacitors shorted.

MOSFET Low Frequency Example

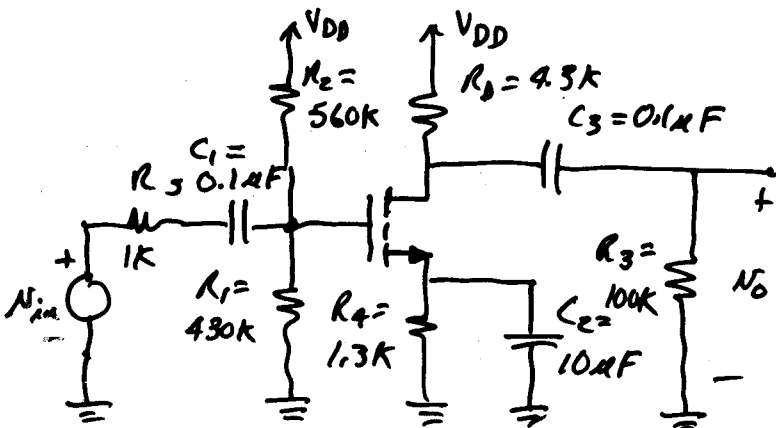

Find ω_L if $g_m = 1.23 \text{ mS}$ & $r_o = 0$

Small-signal model -

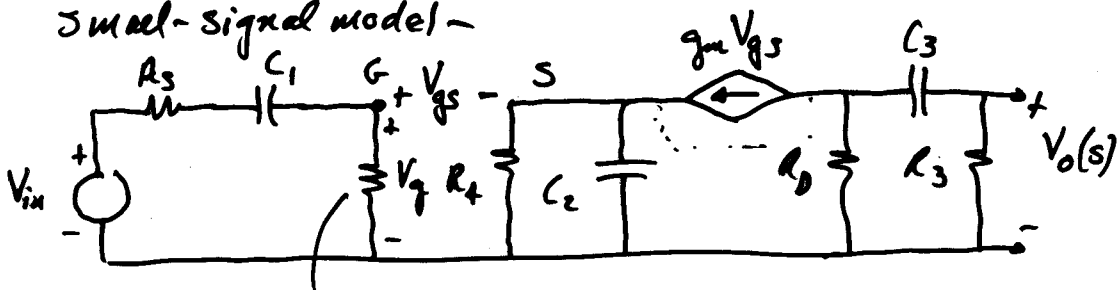

$$R_G = R_1 \parallel R_2 = 243k$$

1.) Direct analysis - no approximations except $r_o = \infty$.

$$\frac{V_o}{V_{in}} = \left(\frac{V_o}{V_{gs}} \right) \left(\frac{V_{gs}}{V_g} \right) \left(\frac{V_g}{V_{in}} \right) \quad Z_c(s) = \frac{1}{sC}$$

$$V_o = -g_m \left(\frac{R_D V_{gs}}{R_D + R_S + \frac{1}{sC_3}} \right) R_3 = \frac{-g_m R_D R_3}{R_D + R_S + \frac{1}{sC_3}} V_{gs} \quad z_3 = 0$$

$$\frac{V_o}{V_{gs}} = \left(\frac{-g_m R_D R_3}{R_D + R_S} \right) \left(\frac{s}{s + \frac{1}{C_3(R_D + R_S)}} \right) \quad p_3 = \frac{-1}{C_3(R_D + R_S)}$$

\uparrow
 $C_3 = \infty$

$$V_{gs} = V_g - V_S = V_g - g_m V_{gs} \left(\frac{R_4 \frac{1}{sC_2}}{R_4 + \frac{1}{sC_2}} \right)$$

$$V_{gs} \left[1 + \frac{g_m R_4}{sR_4 C_2 + 1} \right] = V_g \rightarrow \frac{V_{gs}}{V_g} = \frac{sC_2 R_4 + 1}{sC_2 R_4 + 1 + g_m R_4}$$

$$\frac{V_{gs}}{V_g} = \frac{s + \frac{1}{R_4 C_2}}{s + \frac{1 + g_m R_4}{R_4 C_2}} \quad z_2 = \frac{-1}{R_4 C_2}$$

$$p_2 = -\frac{1 + g_m R_4}{R_4 C_2}$$

$$\frac{V_g}{V_{in}} = \frac{R_G}{R_G + R_S + \frac{1}{sC_1}} = \left(\frac{R_G}{R_G + R_S} \right) \left(\frac{s}{s + \frac{1}{C_1(R_G + R_S)}} \right) \quad z_1 = 0$$

\uparrow
 $C_1 = \infty$

$$\frac{V_o(s)}{V_{in}(s)} = \left(\frac{-g_m R_D R_3}{R_D + R_S} \right) \left(\frac{R_G}{R_G + R_S} \right) \left[\frac{s}{s + p_1} \cdot \frac{s + z_2}{s + p_2} \cdot \frac{s}{s + p_3} \right]$$

$p_1 = -\frac{1}{C_1(R_G + R_S)}$

$$z_1 = 0, z_2 = -76.9 \text{ rad/s}, z_3 = 0, p_1 = -4 \text{ rad/s}, p_2 = -200 \text{ rad/s}$$

$$p_3 = -95.9 \text{ rad/s}$$