
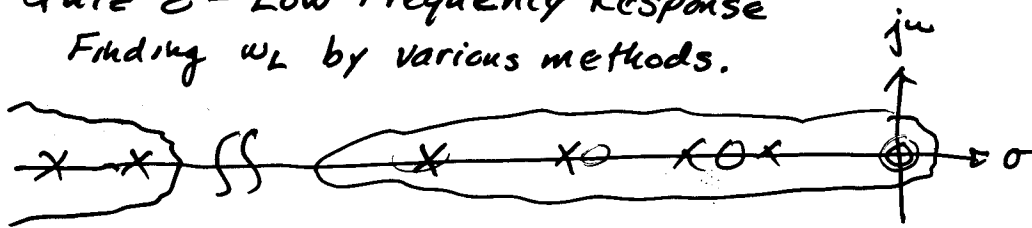


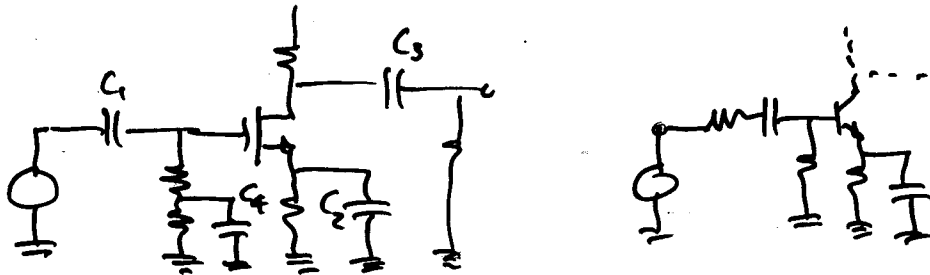Quiz #8 - Low Frequency Response
Finding ω_L by various methods.




Example of a MOSFET with dependent caps.



High frequency Response

$$\frac{V_{out}(s)}{V_{in}(s)} = A_{mid} F_L(s) F_H(s)$$

$$\text{Bandwidth} = f_H - f_L$$

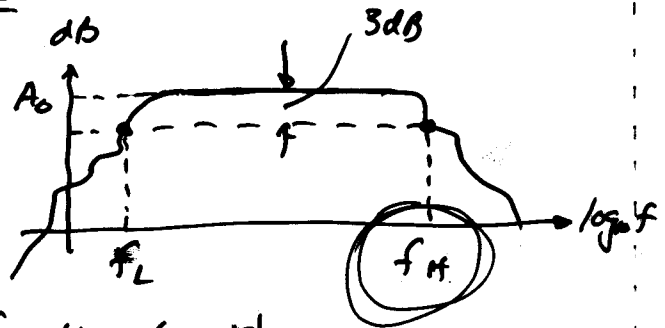

Methods of Finding ω_H , f_H , ω_{3dB} (upper)

1.) Given roots $\left(\frac{1}{s+p_i} \right)$

a.) Bode plot

b.) Dominant pole


$$\omega_H \approx \omega_p(\text{dominant}) \text{ if } \omega_p(\text{dominant}) \leq \frac{\omega_p(\text{next})}{4}$$

$$c.) \omega_H \approx \frac{1}{\sqrt{\sum_n \frac{1}{\omega_{pn}^2} - 2 \sum_n \frac{1}{\omega_{zn}^2}}} \approx \frac{1}{\sqrt{\frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2} + \dots}}$$


d.) Exact solution (quadratic)

2.) Roots are unknown

a.) Miller effect

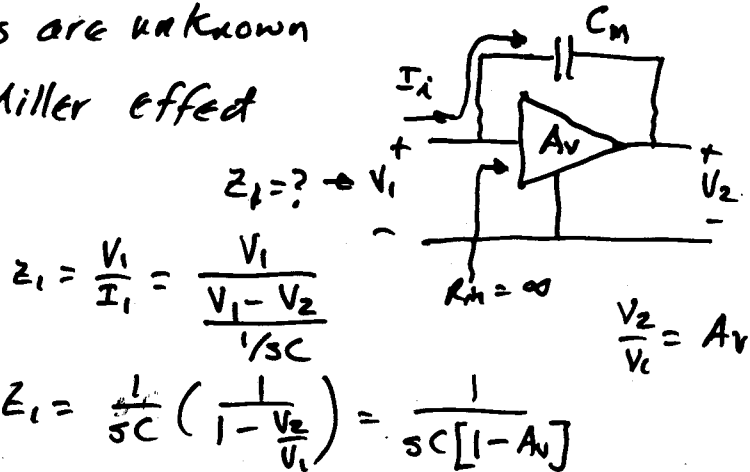

∴

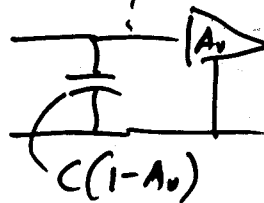


$A_v = -K$

$C_{eq} = sC(1+K)$

b.) Approximate algebraic approach (p.1311)

$s^2 + as + b = (s+p_1)(s+p_2) = s^2 + s(p_1+p_2) + p_1p_2$

Key is to assume that $p_1 \ll p_2$

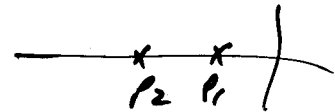


$s^2 + as + b \approx s^2 + sp_2 + p_1p_2$

$p_2 = a$ and $p_1p_2 = b \rightarrow p_1 = \frac{b}{a}$

c.) Open-circuit Time Constant


$\omega_{Hf} \approx \frac{1}{\sum_{i=1}^n R_{ioc} C_i}$

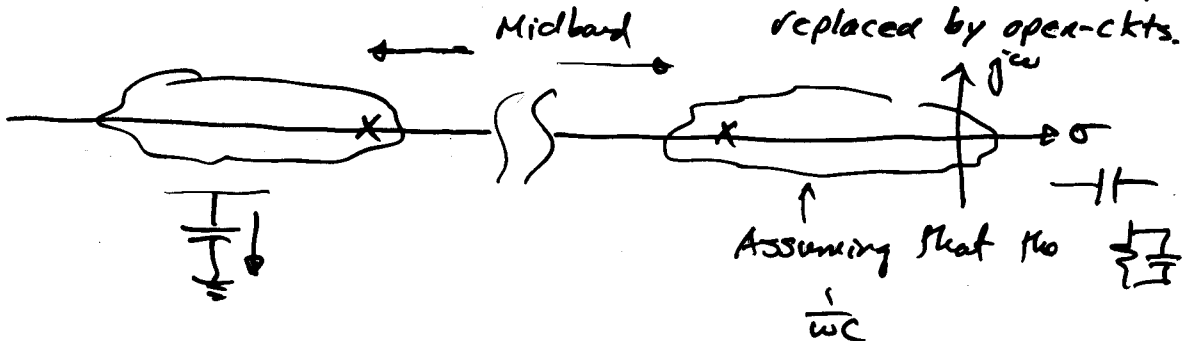where R_{ioc} is the resistance seen from C_i with all other caps replaced by open-ccts.




High Frequency, Small-Signal Models

BJT

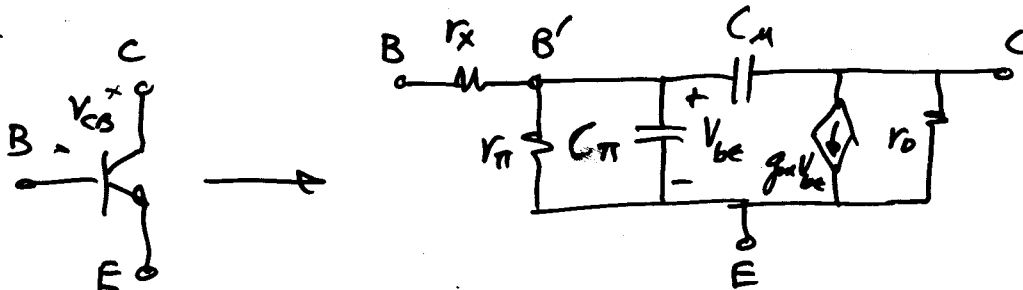


C_{μ} = the reverse-bias capacitance of the BC junction
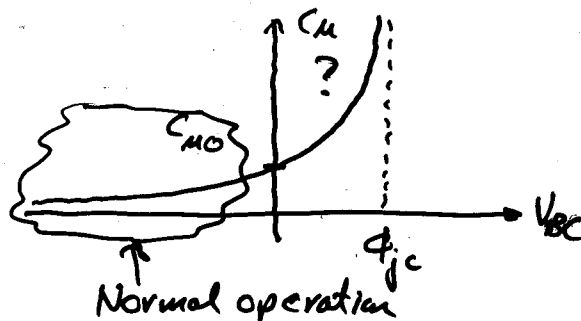
$$C_{\mu} = \frac{C_{\mu 0}}{\sqrt{1 + \frac{V_{CB}}{\phi_{jc}}}}$$





$$C_{\pi} = g_m \tau_F$$


τ_F = forward time constant

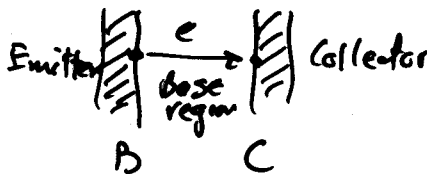

ω_T (unity gain bandwidth)

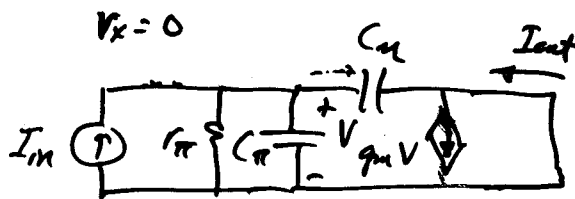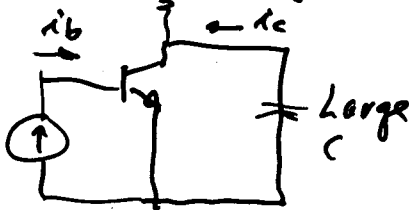

$$I_{out} \approx g_m V$$

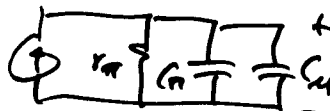

$$V = I_{in} \frac{1}{g_{\pi} + sC_{\pi} + sC_{\mu}} \rightarrow \frac{I_{out}}{I_{in}} = \frac{g_m}{g_{\pi} + s(C_{\pi} + C_{\mu})} = \frac{g_m \tau_{\pi}}{1 + s(C_{\pi} + C_{\mu}) \tau_{\pi}}$$

∴ $\frac{I_{out}(s)}{I_{in}(s)} = \frac{\beta}{s r_{\pi}(C_{\pi} + C_{\mu}) + 1}$ At high frequencies, $\frac{I_{out}}{I_{in}} \approx \frac{\beta}{s r_{\pi}(C_{\pi} + C_{\mu})}$

ω_T is the frequency where $\left| \frac{I_{out}(j\omega)}{I_{in}(j\omega)} \right| = 1$

∴ $\omega_T \approx ? \quad \left| \frac{\beta}{\omega_T r_{\pi}(C_{\pi} + C_{\mu})} \right| = 1 \rightarrow \omega_T = \frac{\beta / r_{\pi}}{C_{\pi} + C_{\mu}}$

$$\boxed{\omega_T = \frac{g_m}{C_{\pi} + C_{\mu}}}$$

How do you find C_{π} ?

1.) Given $f_F \rightarrow C_{\pi} = g_m f_F$

2.) Given ω_T and $C_{\mu} \rightarrow C_{\pi} = \frac{g_m}{\omega_T} - C_{\mu}$

r_x : r_x is a small resistance in series with the base of about 100Ω to 500Ω . It varies with I_C and is called "the base spreading resistance".

MOSFET