
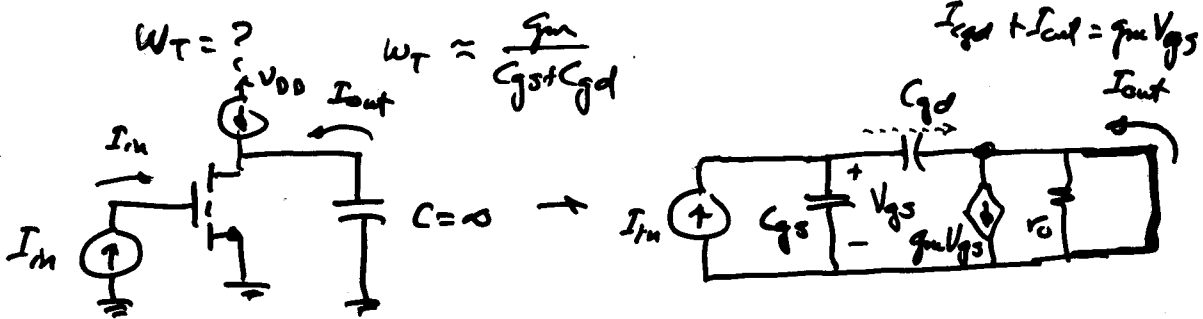
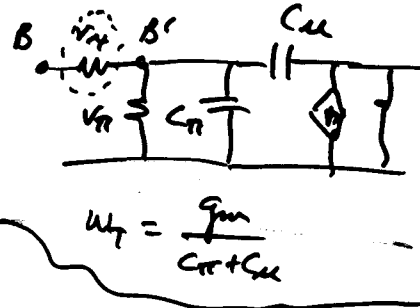


High-Frequency MOSFET Model

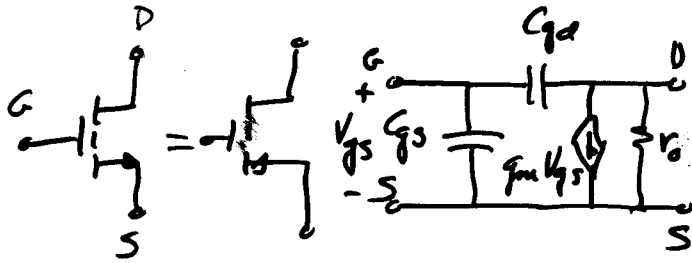


$$I_{out} \approx g_m V_{gs} \quad \text{and} \quad V_{gs} = I_{in} \left[\frac{1}{s(C_{gs} + C_{gd})} \right]$$

$$\frac{I_{out}}{I_{in}} = \frac{g_m}{s(C_{gs} + C_{gd})} \rightarrow \frac{I_{out}(j\omega)}{I_{in}(j\omega)} = \frac{g_m}{j\omega(C_{gs} + C_{gd})}$$

$$\left| \frac{I_{out}(j\omega)}{I_{in}(j\omega)} \right| = 1 \quad \text{where} \quad \omega = \omega_T \rightarrow \boxed{\omega_T = \frac{g_m}{C_{gs} + C_{gd}}}$$

MOSFET Example - Cont'd

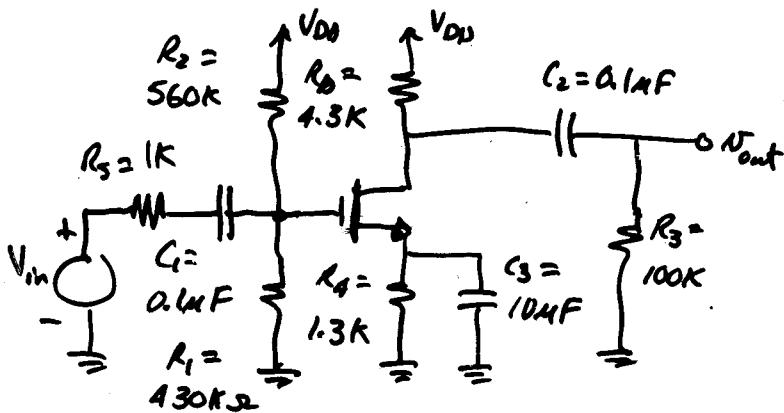


Find f_H .

$$X_C = \frac{1}{\omega C}$$

$$g_m = 1.23 \text{ mS} \quad C_{gs} = 10 \text{ pF} \quad C_{gd} = 2 \text{ pF}$$

5.5. Model -

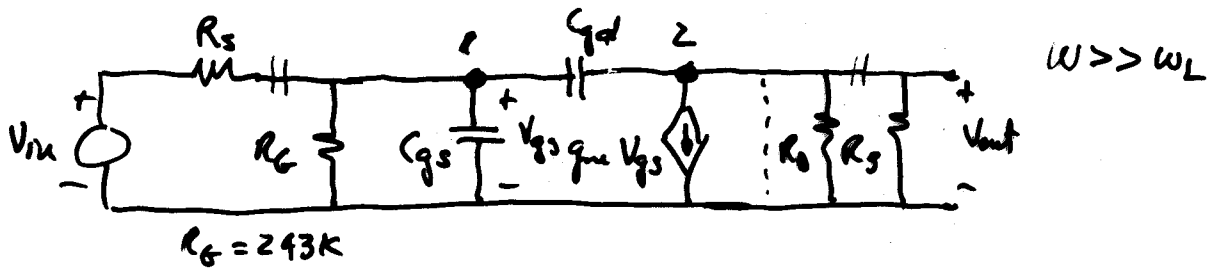

Direct analysis -

Model equations

$$\left(\frac{1}{R_s} + \frac{1}{R_G} + sC_{gs} + sC_{gd}\right)V_{gs} - sC_{gd}V_{out} = \frac{V_{in}}{R_s} \quad (1)$$

$$sC_{gd}(V_{out} - V_{gs}) + g_m V_{gs} + V_{out}\left(\frac{1}{R_L} + \frac{1}{R_s}\right) = 0 \quad (2)$$