
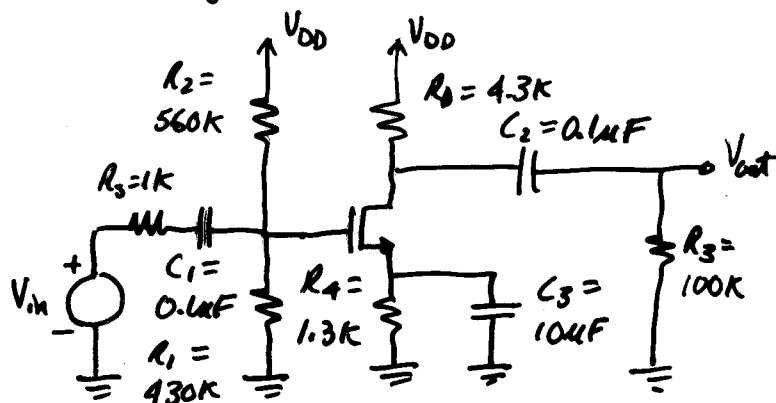


MOSFET High-Frequency Example

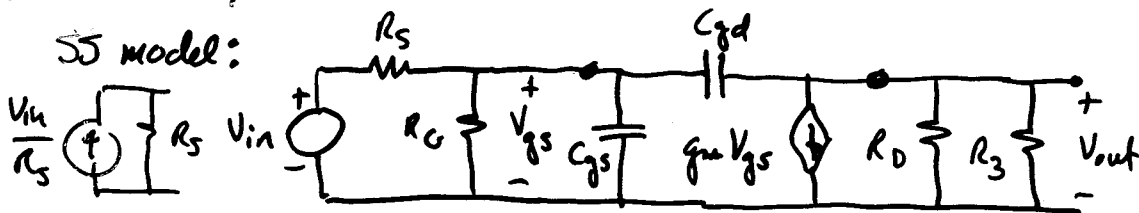

① Direct Analysis -

SS model:



Nodal eqs.

$$\left(\frac{1}{R_s} + \frac{1}{R_G} + sC_{gs} + sC_{gd}\right)V_{gs} - sC_{gd}V_{out} = \frac{V_{in}}{R_s} \quad (1)$$

$$s(C_{gd}(V_{out} - V_{gs}) + g_m V_{gs} + \left(\frac{1}{R_D} + \frac{1}{R_3}\right)V_{out}) = 0 \quad (2)$$


↓ A page of algebra

$$\frac{V_{out}}{V_{in}} = \frac{-G_s(g_m - sC_{gd})}{(G_s + G_G)(G_D + G_3) + s[C_{gs}(G_D + G_3) + C_{gd}(G_D + G_3 + G_s + G_G) + g_m C_{gd}] + s^2 C_{gd} C_{gs}}$$

↓ Substitute the values

$$\frac{V_{out}}{V_{in}} = \frac{-10^{-3}(1.23 \times 10^{-3} - s2 \text{ pF})}{20 \times 10^{-24} [s^2 + 3.628 \times 10^8 s + 1.165 \times 10^{16}]}$$

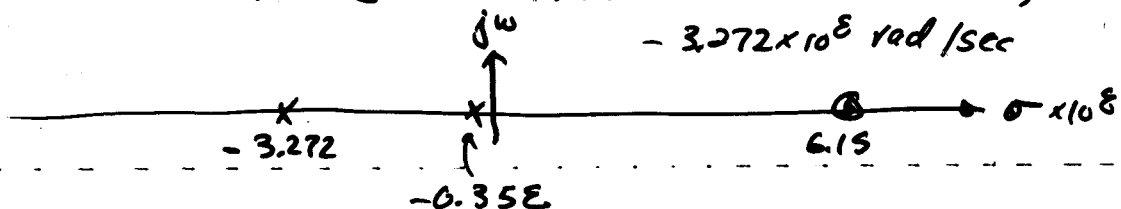
Roots of [] → $P_1, P_2 = -0.358 \times 10^8 \text{ rad/sec}, -3.272 \times 10^8 \text{ rad/sec}$




$\omega_H = ?$ (Dominant pole) $\approx 0.355 \times 10^8$ rad/sec

$f_{3dB}(\text{upper}) = \underline{\underline{5.67 \text{ MHz}}}$

Bode plot -

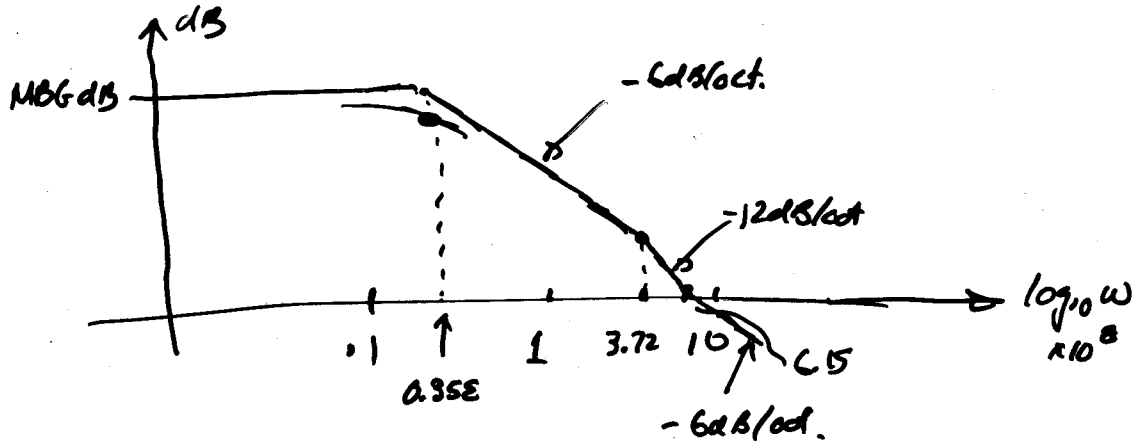

② Miller approach

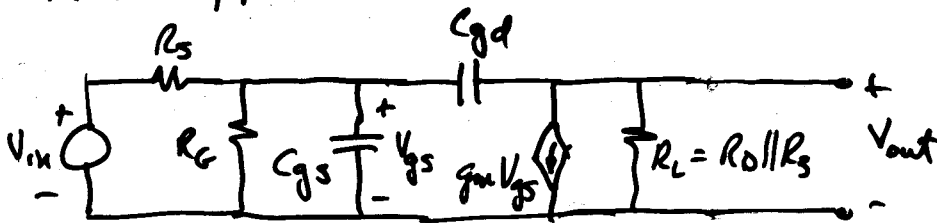


$\frac{V_{out}}{V_{gs}} = K \quad C_{eq} = C_{gd}(1-K)$

Assume $\frac{1}{\omega C_{gd}} \gg R_L \rightarrow K \rightarrow V_{out} \approx -g_m R_L V_{gs}$

$\approx -1.23(491100)$

$\approx -5 \text{ V/V}$


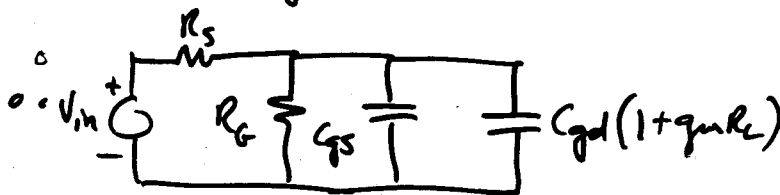


Pole = ? $\frac{1}{R_{eq} C_{eq}} \quad C_{eq} = C_{gs} + C_{gd}(1+g_m R_L)$
 $R_{eq} = R_s || R_g$


$\omega_H \approx \frac{1}{R_{eq} C_{eq}} = \frac{1}{(0.996 \text{ K}) [10 \text{ pF} + 2 \text{ pF} \times 5]} = 45.3 \times 10^6 \text{ rad/sec}$

$\therefore f_H = \frac{\omega_H}{2\pi} = \underline{\underline{7.22 \text{ MHz}}} \quad \frac{1}{45.3 \times 10^6 \times 2 \times 10^{-12}} \approx 10 \text{ K}$

③ Open-Circuit Time Constant

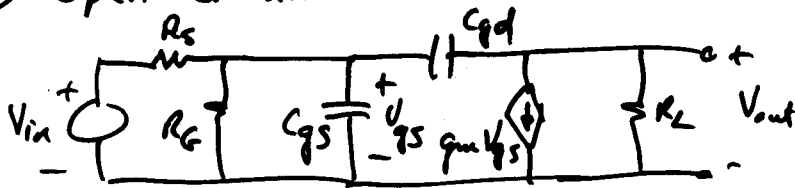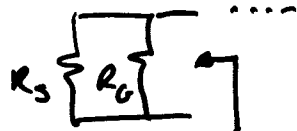 C_{gs} :

$$R_{qso} = R_s \parallel R_G \quad \rightarrow \quad R_{qso} C_{gs} = 0.976k \cdot 2pF$$

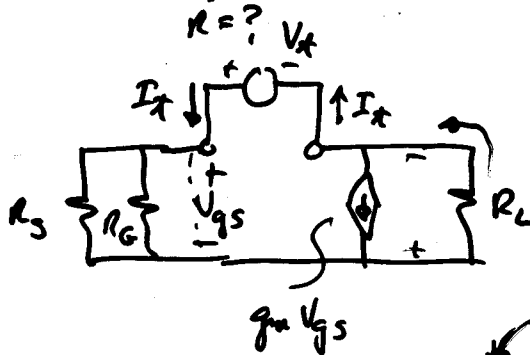 C_{gd} :

$$R_{qdo} = \frac{V_A}{I_A}$$

$$I_A (R_s \parallel R_G)$$

$$V_A = I_A (R_s \parallel R_G) + R_L (I_A + g_m V_{gs})$$

$$V_A = I_A (R_s \parallel R_G) + I_A R_L + I_A g_m (R_s \parallel R_G) R_L$$

$$\therefore \frac{V_A}{I_A} = R_{qdo} = R_s \parallel R_G (1 + g_m R_L) + R_L$$

$$= 0.976k [1 + 5] + 4.022k = 10.16k$$

$$\omega_H = \frac{1}{R_{qso} C_{gs} + R_{qdo} C_{gd}} = \frac{1}{(0.976k)(2pF) + 10.16k(10pF)}$$

$$= 3333 \times 10^6 \text{ rads/sec} \rightarrow \underline{\underline{f_H = 5.3 \text{ MHz}}}$$