
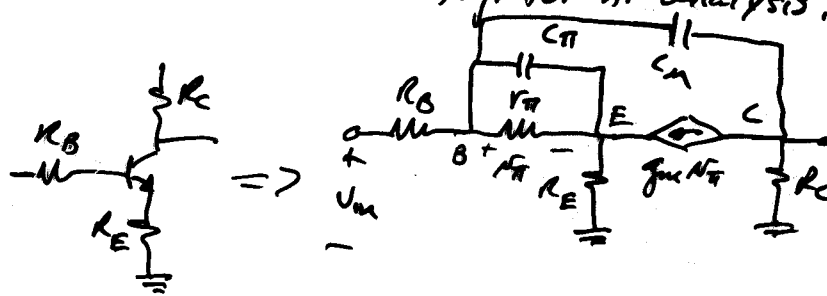


Question: What about non-CE config. for HF analysis?

Answer:

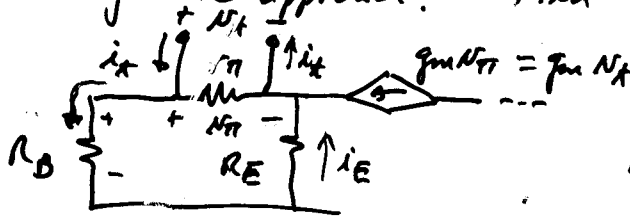

Using OTC approach: Find R_{in} and R_{out}



First ignore r_{π} (it is in || with the answer)

$$i_E + g_m N_{\pi} = i_x$$


$$N_{\pi} = i_x R_B + R_E (i_x - g_m N_{\pi})$$

$$N_{\pi} [1 + g_m R_E] = i_x (R_B + R_E)$$

$$\frac{N_{\pi}}{i_x} = \frac{R_B + R_E}{1 + g_m R_E} \rightarrow R_{in} = r_{\pi} \parallel \left[\frac{R_B + R_E}{1 + g_m R_E} \right]$$


BJT HF Example
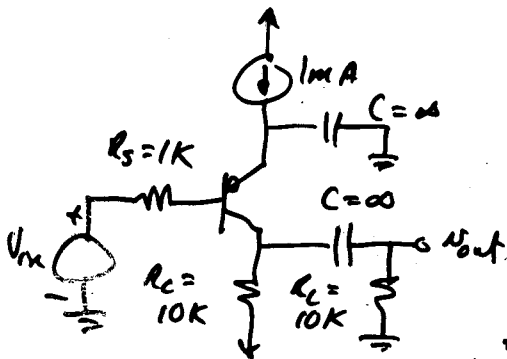
$$C_{\pi} = \frac{2\pi f_T}{g_m} - C_{\mu}$$



$B = 100, C_{\mu} = 2pF, f_T = 500MHz, r_x = 0$
and $r_o = \infty$. If $r_{\pi} = 1k, g_m = 0.01A/V$
and $C_{\pi} = 10pF$, find f_H .

Small-signal model:

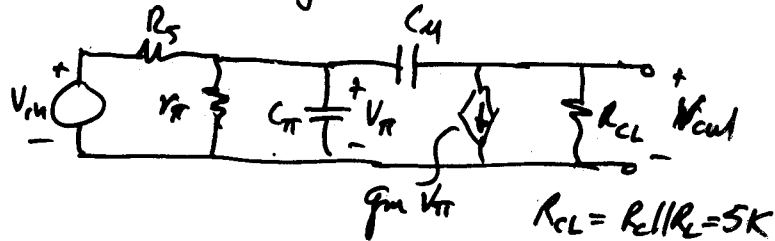

1.) Miller approach



$$K = \frac{V_{out}}{V_{in}} \approx -g_m R_{CL} \text{ if } \frac{1}{4C_{\mu}} \gg R_{CL}$$


Continuing -

$$C_M (1 + g_m R_{CL}) = 2 \text{ pF} (1 + 10.5) = 102 \text{ pF} \quad C_{eq} = 112 \text{ pF}$$


$$\omega_H = \frac{1}{(R_S || r_\pi) C_{eq}} = \frac{1}{500 (112 \text{ pF})} = 17.86 \text{ Mrads/sec}$$

$$f_H = f_{-3dB} (\text{upper}) = \frac{\omega_H}{2\pi} = \underline{\underline{2.892 \text{ MHz}}}$$

2.) OTC

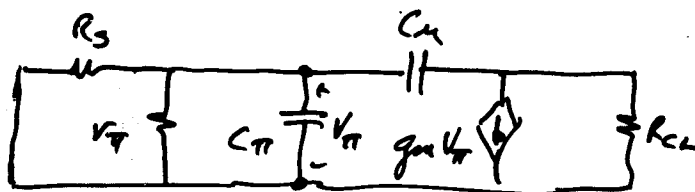

$R_{C\pi 0}$: $R_{C\pi 0} = r_\pi || R_S$

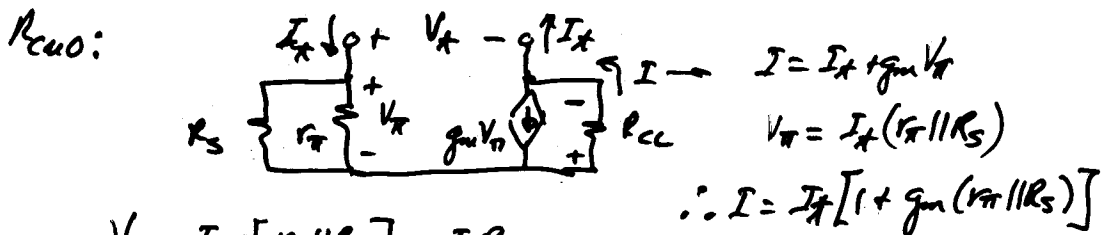

$$V_x = I_x [r_\pi || R_S] + I R_{CL}$$

$$V_x = I_x [r_\pi || R_S] + I_x R_{CL} [1 + g_m (r_\pi || R_S)]$$


$$R_{C\pi 0} = \frac{V_x}{I_x} = (r_\pi || R_S) (1 + g_m R_{CL}) + R_{CL}$$

$$= 5 \text{ k} + (1 + 10.5)(500) = 30.5 \text{ k}\Omega$$

check Assumption:
 $\frac{1}{\omega_H 2 \text{ pF}} = 28 \text{ k}\Omega$
 $28 \text{ k} > 5 \text{ k}$


$$\omega_H = \frac{1}{R_{C\pi 0} C_\pi + R_{C\pi 0} C_M} = \frac{1}{(0.5 \text{ k})(10 \text{ pF}) + (30.5 \text{ k})(2 \text{ pF})} \approx 15 \text{ Mrads/sec}$$
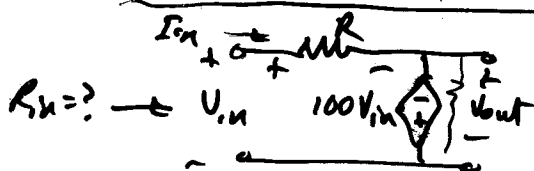
$$f_H = \frac{15 \times 10^6}{2\pi} = \dots$$




$$R_M = \frac{V_{in}}{I_{in}} = \frac{V_{in}}{\frac{V_{in}}{R} - (-100 V_{in})} = \frac{R}{101}$$

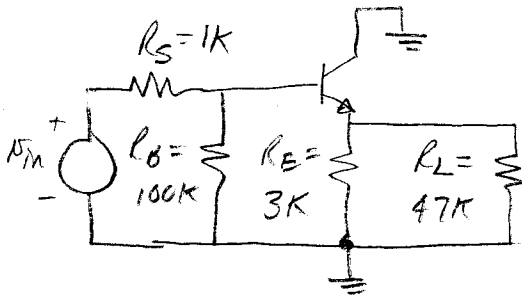Dominant Pole for Emitter Follower (Common Collector)



If $\beta = 100$, $I_C = 1.5\text{mA}$,
 $r_x = 150\Omega$, $C_u = 0.5\text{pF}$ and
 $f_T = 50\text{MHz}$, find the
 midband gain and ω_H .

Midband gain:

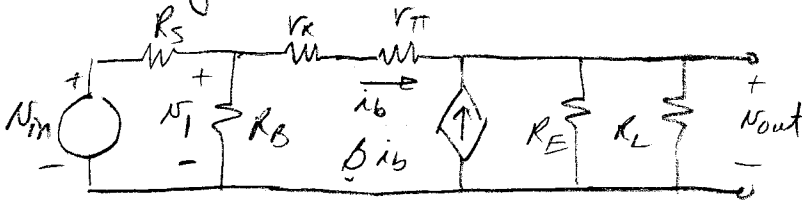

$$g_m = \frac{I_C}{V_T} = \frac{1.5}{25} = 60\text{mS}$$

$$r_{\pi} = \frac{100}{60} \times 10^3 = 1667\Omega$$

$$\frac{v_{out}}{v_{in}} = \left(\frac{v_{out}}{i_B} \right) \left(\frac{i_B}{v_B} \right) \left(\frac{v_B}{v_{in}} \right)$$

$$\frac{v_{out}}{v_{in}} = (1+\beta) R_E \parallel R_L = 101 (3\text{k} \parallel 47\text{k}) = 101 (2.82\text{k}) = 284.82\text{k}$$


$$\frac{i_B}{v_B} = \frac{1}{r_x + r_{\pi} + (1+\beta) R_E \parallel R_L} = \frac{1}{0.15\text{k} + 1.667\text{k} + 101(2.82\text{k})} = \frac{1}{286.69\text{k}}$$

$$\frac{v_B}{v_{in}} = \frac{R_B \parallel \left[\frac{v_B}{i_B} \right]}{R_S + R_B \parallel \left[\frac{v_B}{i_B} \right]} = \frac{100\text{k} \parallel 286.69\text{k}}{1\text{k} + 100\text{k} \parallel 286.69\text{k}} = \frac{74.14\text{k}}{75.14\text{k}}$$

$$\therefore \frac{v_{out}}{v_{in}} = (284.82\text{k}) \left(\frac{1}{286.69\text{k}} \right) \left(\frac{74.14}{75.14} \right) = 0.974 \text{ V/V}$$

ω_H :
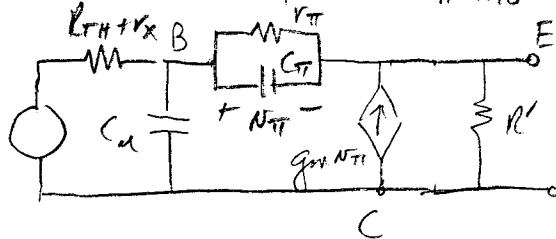
$$C_{\pi} = \frac{g_m}{\omega_T} - C_u = \frac{60 \times 10^{-3}}{\pi \times 10^7} - 0.5\text{pF} = 18.6\text{pF}$$




$$R_{TH} = R_S \parallel R_B = 0.99\text{k}$$

$$R_{TH} + r_x = 1.149\text{k}$$

$$R' = R_E \parallel R_L = 2.82\text{k}$$

$R_{\pi O}$:

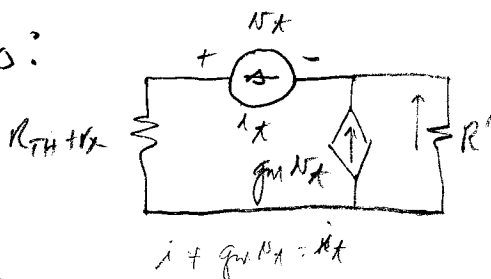


$$i_x = i_x (R_{TH} + r_x) + (i_x - g_m v_{\pi}) R'$$

$$i_x (1 + g_m R') = i_x (R_{TH} + r_x + R')$$

$$R_{\pi O} = r_{\pi} \parallel \frac{R_{TH} + r_x + R'}{1 + g_m R'} \approx \frac{R_{TH} + r_x + R'}{1 + g_m R'} = 22.4\Omega$$

Common-Collector - cont'd

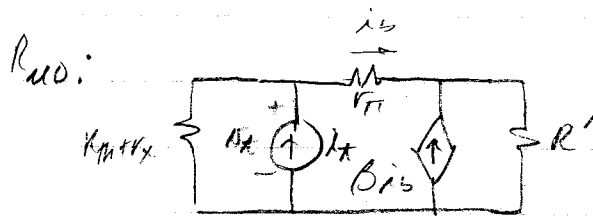


$$i_x = \frac{N_x}{R_{th}} + \frac{N_x}{V_T + (1+\beta)R'} \rightarrow R_{uo} = \frac{N_x}{i_x} = \frac{1}{\frac{1}{R_{th}} + \frac{1}{V_T + (1+\beta)R'}}$$

$$R_{uo} = \frac{1}{\frac{1}{1.144k} + \frac{1}{286.487k}} = 1.144k\Omega$$

$$\therefore \omega_H \approx \frac{1}{R_{uo}C_{\pi} + R_{uo}C_u} = \frac{1}{(0.0224k)(12.66pF) + (1.144k)(0.5pF)}$$

$$= 1.01 \times 10^9 \text{ rad/sec} \rightarrow \underline{\underline{161 \text{ MHz}}}$$

High-Frequency Response of a Diff. Amp.

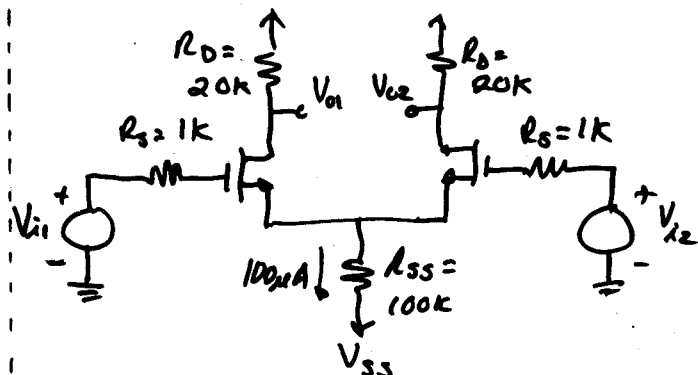


If $K_n' = 1 \text{ mA/V}^2$ and $V_{TN} = 1 \text{ V}$
 find MBG and ω_H for the differential and common mode responses assuming that $C_{gs} = 5 \text{ pF}$ and $C_{gd} = 1 \text{ pF}$.

Differential Mode -

$\frac{V_{o1}}{V_{id}} = ?$ $V_{i1} = \frac{V_{in}}{2}$ $V_{i2} = -\frac{V_{in}}{2}$

s.s model -

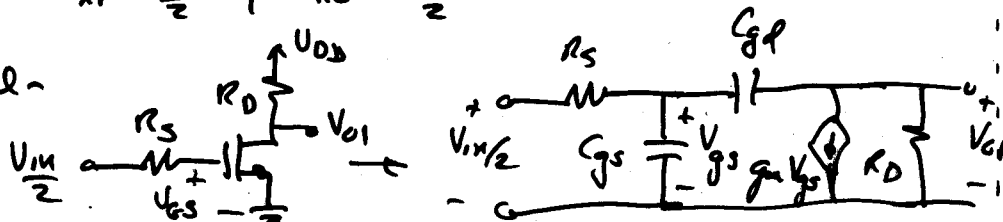

MBG = $\frac{V_{o1}}{V_{in}} = ?$ $V_{o1} = -g_m R_D V_{gs} = -g_m \frac{R_D}{2} V_{in}$

MBG = $-\frac{g_m R_D}{2} = ?$ $g_m = \sqrt{2 \cdot k_n' \cdot I_{D1}} = \sqrt{2 \cdot 1 \text{ mA/V}^2 \cdot 50 \mu\text{A}}$

$= -\frac{316 \times 10^{-6} \cdot 20 \times 10^3}{2} = -3.162 \text{ V/V}$ $g_m = 316 \mu\text{S}$


ω_H (Miller Approach) -

$\omega_H \approx \frac{1}{C_{eq} R_s}$, $C_{eq} = C_{gs} + C_{gd}(1 + g_m R_D)$ if $\frac{1}{\omega_H C_{gd}} \gg R_D$


$C_{eq} = 5 \text{ pF} + 1 \text{ pF}(1 + 6.32) = 12.3 \text{ pF}$

$\omega_H = \frac{1}{(1 \text{ k})(12.3 \text{ pF})} = 81.2 \times 10^6 \frac{\text{rad}}{\text{sec}} \Rightarrow \underline{f_H = 12.9 \text{ MHz}}$

Common-Mode Analysis:

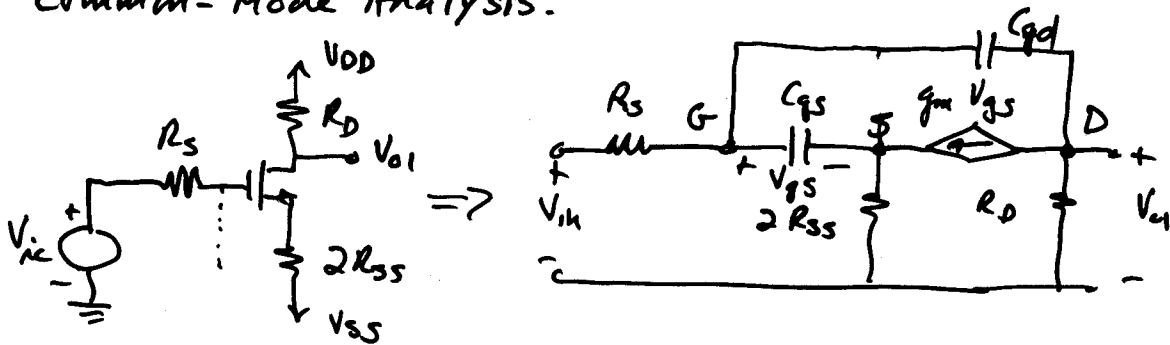


R_{eqs0} :

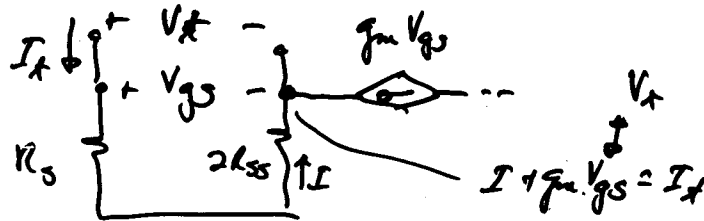

$$V_x = I_x R_s + (I_x - g_m V_x) 2R_{ss}$$

$$\frac{V_x}{I_x} = R_{eqs0} = \frac{R_s + 2R_{ss}}{1 + g_m 2R_{ss}} = 3.13 \text{ k}$$

R_{eqd0} :

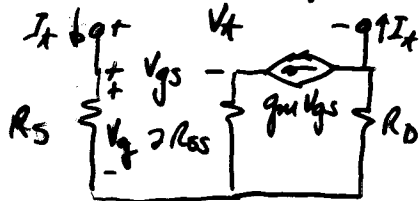

$$V_x = I_x R_s + (I_x + g_m V_{gs}) R_D$$

$$V_{gs} = V_g - V_s = V_g - g_m 2R_{ss} V_{gs}$$

Thus, $V_x = I_x R_s + I_x R_D + g_m R_D \left(\frac{R_s I_x}{1 + 2g_m R_{ss}} \right)$ $\therefore V_{gs} = \frac{V_g}{1 + g_m 2R_{ss}} = \frac{I_x R_s}{1 + g_m 2R_{ss}}$

or $\frac{V_x}{I_x} = R_{eqd0} = R_s + R_D + \frac{g_m R_D R_s}{1 + 2g_m R_{ss}} = 21 \text{ k} + \frac{6.32 \text{ k}}{69.2} = 21.1 \text{ k}$

$$\omega_H = \frac{1}{R_{eqs0} C_{gs} + R_{eqd0} C_{gd}} = \frac{1}{1.565 \times 10^8 + 4.22 \times 10^8} = 17.29 \text{ Mrads/sec}$$

$f_H = \underline{\underline{2.75 \text{ MHz}}}$

$MBG = \frac{g_m R_D}{1 + 2g_m R_{ss}} \approx \frac{g_m R_D}{2g_m R_{ss}} = \frac{20}{200} = \underline{\underline{0.1 \text{ V/V}}}$

$CMRR? \rightarrow 31.6 \left(\frac{\frac{3}{\omega_H(\text{com})} + 1}{\frac{3}{\omega_H(\text{diff})} + 1} \right)$

Chap. 18 next