

Note: Homework 11 due Wednesday (3/31)


CHAPTER 13 - FEEDBACK, STABILITY AND OSCILLATORS

- Introduction
- Series-shunt
- Shunt-shunt
- Shunt-series
- Series-series

What can feedback do?

- Increase or decrease the resistance at a port
- Increase the accuracy of an amplifier.
- Remove nonlinearity
- Increase  $f_H$  and decrease  $f_L$
- Create oscillators

Classical Single-Loop Feedback

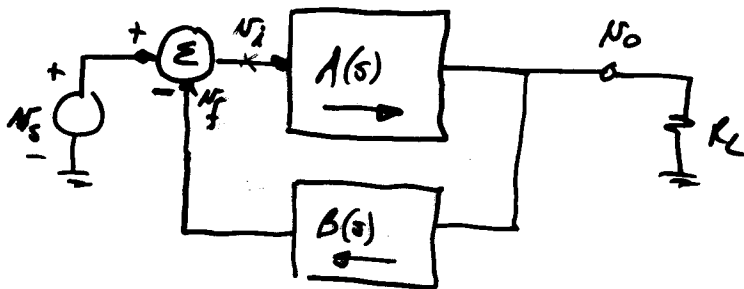


$\frac{N_o}{N_s} = ?$  Closed-loop gain

$$N_o = A(s) N_i = A(s) [N_s - N_f] = A(s) N_s - A(s) [B(s) N_o]$$

$$\frac{N_o}{N_s} = \frac{A(s)}{1 + A(s)B(s)} = \frac{A(s)}{1 + T(s)} \quad \text{where } T(s) = \text{Loop gain}$$

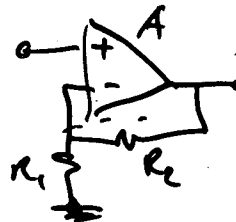Assume the loop gain  $\gg 1 \rightarrow \frac{N_o}{N_s} \approx \frac{A(s)}{A(s)B(s)} = \frac{1}{B(s)}$



$A = A_{nd}$

$B = \frac{R_i}{R_i + R_f}$

$N_{gs} = N_g - N_s$




Positive feedback:  $T(s) > 0$

Negative feedback:  $T(s) < 0$

$\frac{N_{gs}}{N_g} = \frac{1}{1 + g_m R_s}$

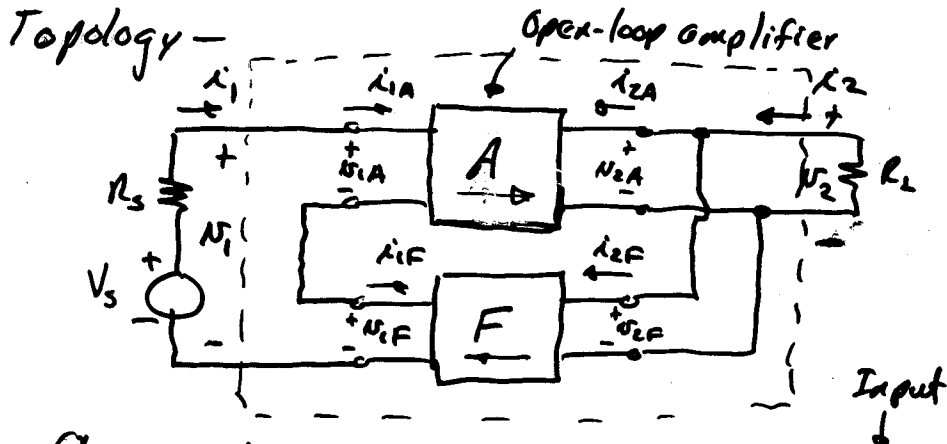Voltage Amplifiers - Series-Shunt Feedback



Choosing h-parameters to model the series-shunt fb.

$$v_1 = h_{11T} i_1 + h_{12T} v_2$$

$$i_2 = h_{21T} i_1 + h_{22T} v_2$$

A network:

$$\begin{bmatrix} v_{1A} = h_{11A} i_{1A} + h_{12A} v_{2A} \\ i_{2A} = h_{21A} i_{1A} + h_{22A} v_{2A} \end{bmatrix} + \begin{bmatrix} v_{1F} = h_{11F} i_{1F} + h_{12F} v_{2F} \\ i_{2F} = h_{21F} i_{1F} + h_{22F} v_{2F} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$v_1 = (h_{11A} + h_{11F}) i_1 + (h_{12A} + h_{12F}) v_2$$

$$i_2 = (h_{21A} + h_{21F}) i_1 + (h_{22A} + h_{22F}) v_2$$

If  $h_{21A} \gg h_{21F}$  and  $h_{12F} \gg h_{12A}$ , then

$$v_1 = h_{11T} i_1 + h_{12F} v_2$$

$$i_2 = h_{21A} i_1 + h_{22T} v_2$$

⋮