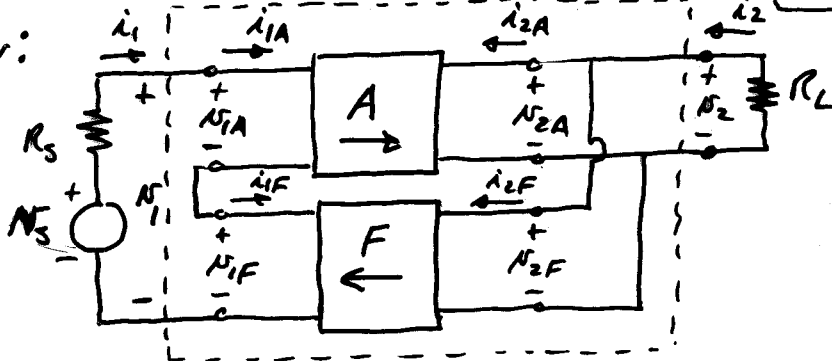


Voltage Amplifiers - Series-Shunt Feedback

HW#11 Due 3/31

Topology:



$$\left. \begin{aligned} N_1 &= (h_{11A} + h_{11F}) i_1 + (h_{12A} + h_{12F}) N_2 \\ i_2 &= (h_{21A} + h_{21F}) i_1 + (h_{22A} + h_{22F}) N_2 \end{aligned} \right\} \begin{aligned} N_1 &= h_{11T} i_1 + h_{12F} N_2 \\ i_2 &= h_{21A} i_1 + h_{22T} N_2 \end{aligned}$$

where  $h_{11T} = \left. \frac{N_1}{i_1} \right|_{N_2=0}$ ,  $h_{12F} = \left. \frac{N_1F}{N_2F} \right|_{i_1=0, i_1F=0, i_1F=0}$ ,  $h_{21A} = \left. \frac{i_2A}{i_1A} \right|_{N_2A=0, N_2=0}$

and  $h_{22T} = \left. \frac{i_2}{N_2} \right|_{i_1=0}$

What is the closed-loop transfer function including  $R_s$  &  $R_L$ ?

- (1)  $N_s = i_1 R_s + N_1 = i_1 R_s + h_{11T} i_1 + h_{12F} N_2 = i_1 (R_s + h_{11T}) + h_{12F} N_2$
- $N_2 = -i_2 R_L \rightarrow -\frac{N_2}{R_L} = h_{21A} i_1 + h_{22T} N_2 \rightarrow 0 = h_{21A} i_1 + (h_{22T} + G_L) N_2$
- 2nd eq.  $\rightarrow i_1 = -\frac{(h_{22T} + G_L) N_2}{h_{21A}}$
- Substitute into eq. (1) to get

$$N_s = -(R_s + h_{11T}) \left( \frac{h_{22T} + G_L}{h_{21A}} \right) N_2 + h_{12F} N_2$$


$$\frac{N_2}{N_s} = \text{Closed loop T.F.} = \frac{h_{21A}}{-(R_s + h_{11T})(h_{22T} + G_L) + h_{12F} h_{21A}}$$

$$\frac{N_2}{N_s} = A_{VF} = \frac{(R_s + h_{11T})(h_{22T} + G_L)}{1 + \frac{-h_{21A}}{(R_s + h_{11T})(h_{22T} + G_L)} (h_{12F})} = \frac{A}{1 + AB} = \frac{A}{1 + AF}$$

$$A = \frac{-h_{21A}}{(R_s + h_{11T})(G_L + h_{22T})}$$

$$\text{and } \beta = F = h_{12F}$$

Example of Series-Shunt Fb.

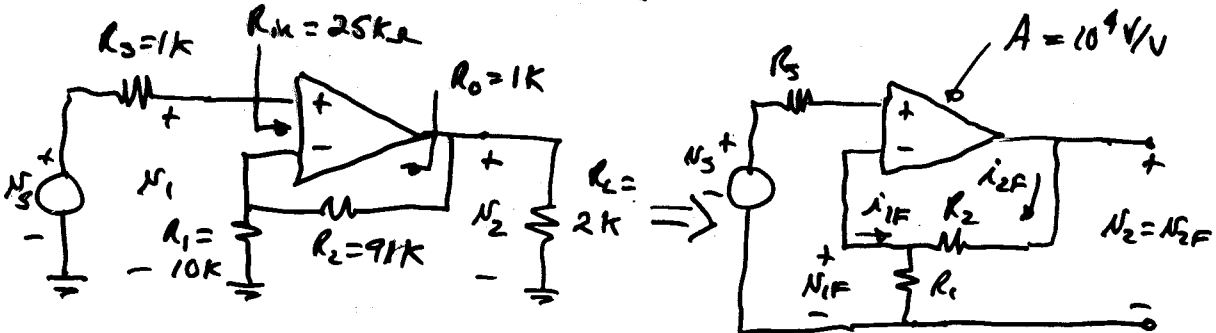

Find  $\frac{N_2}{N_5}$ .


$$h_{11T} = h_{11A} + h_{11F} = 25k\Omega + \left. \frac{N_{1F}}{i_{1F}} \right|_{N_2=0} = 25k\Omega + R_1 || R_2 = 25k + 9.01k$$

$$h_{11T} = 34.01k\Omega$$

$$h_{22T} = h_{22A} + h_{22F}, \rightarrow h_{22F} = \left. \frac{i_{2F}}{N_2} \right|_{i_{1F}=0} = \frac{1}{R_1 + R_2} = \frac{1}{101k}$$

$$h_{12F} = \left. \frac{N_{1F}}{N_2} \right|_{i_{1F}=0} = \frac{R_1}{R_1 + R_2} = 0.099 = F = \beta$$

$h_{21A} = ?$  (Open loop)

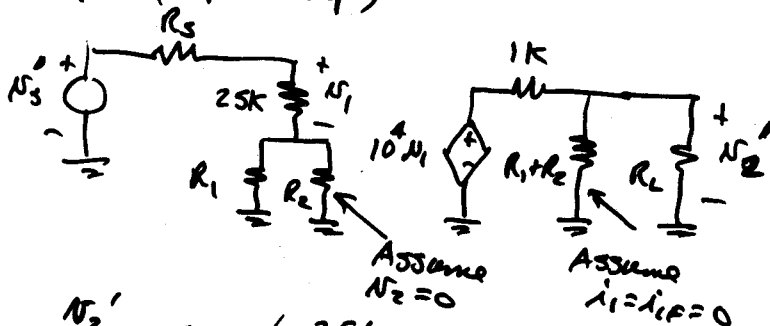

$$\frac{N_2'}{N_5'} = A = \left( \frac{25k}{1k + 25k + 9.01k} \right) (10^4) \left( \frac{(R_1 || R_2) || R_L}{1k + (R_1 || R_2) || R_L} \right)$$

$$= 4730 \frac{V}{V}$$

$$\therefore A_{VF} = \frac{N_2}{N_5} = \frac{A}{1 + \beta A} = \frac{4730}{1 + (4730)(0.099)} = 10.08 \frac{V}{V}$$

Input Resistance

For the voltage amplifier feedback network-

$$R_{inF} = \frac{N_1}{i_1} = (R_s + h_{i1T}) \left[ 1 + \frac{-h_{21A} h_{12F}}{(R_s + h_{i1T})(G_L + h_{22T})} \right]$$

$$= (R_s + h_{i1T}) [1 + AB] = \frac{\text{Input } R}{\text{w/o fb}} (1 + \text{Loop gain})$$

Output Resistance ( $N_2 = 0$ )

$$R_{outF} = \left. \frac{N_2}{i_2} \right|_{N_1=0} = \frac{1}{(h_{22} + G_L) \left[ 1 + \frac{-h_{21A} h_{12F}}{(R_s + h_{i1T})(G_L + h_{22T})} \right]}$$


$$= \frac{1}{(h_{22} + G_L)(1 + AB)} = \frac{\text{Output Resistance w/o fb}}{1 + \text{Loop Gain}}$$

General Approach to Analyzing a fb. Amplifier is:

- 1.) Find  $h_{i1F}$  (input resistance to the F network with the output short-circuited)
- 2.) Find  $h_{22F}$  (output conductance of the F network with the input O.C.)
- 3.) Find  $h_{12F} = F = B$  (voltage gain of F network from output to input with the input O.C.)
- 4.) Use the amplifier ckt. to find  $A$  (including  $h_{i1F}$  and  $h_{22F}$ )
- 5.)  $A_F = \frac{A}{1 + AB}$
- 6.)  $R_{inF} = (R_s + h_{i1T})(1 + BA)$
- 7.)  $R_{outF} = \frac{1}{(G_s + h_{22T})(1 + AB)}$

This the next lecture page (to be covered 3/31/04). It should help to work the homework.

### Example

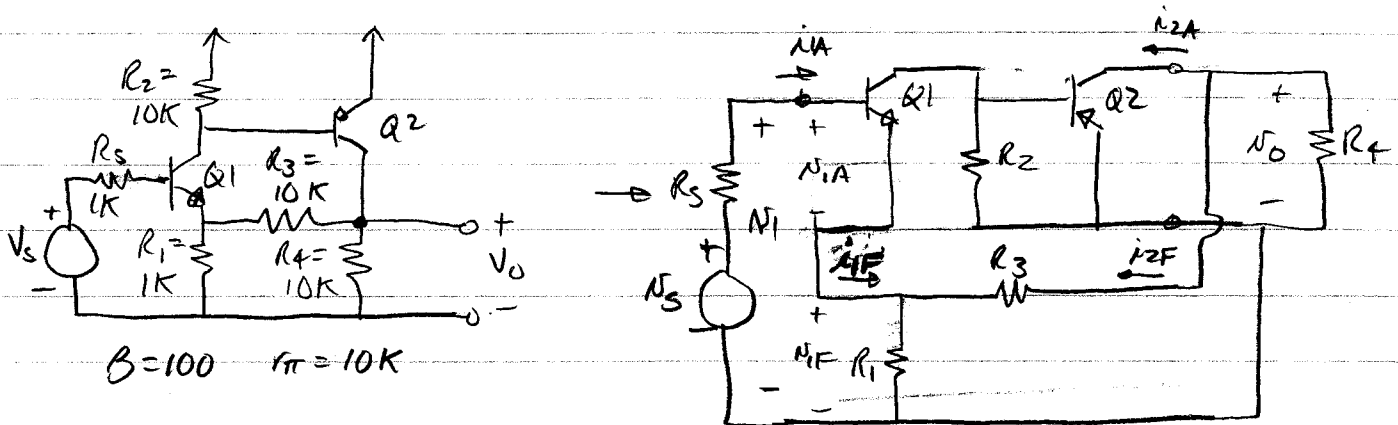


$$\beta = 100 \quad r_{\pi} = 10K$$

$$1.) \quad h_{11F} = \left. \frac{N_{1F}}{i_{1F}} \right|_{N_6=0} = R_1 || R_3 = 0.91K$$

$$2.) \quad h_{22F} = \left. \frac{i_{2F}}{N_6} \right|_{i_{1F}=0} = \frac{1}{R_1 + R_3} = \frac{1}{11K}$$

$$3.) \quad h_{12F} = \left. \frac{N_{1F}}{N_6} \right|_{i_{1F}=0} = \frac{1}{11}$$

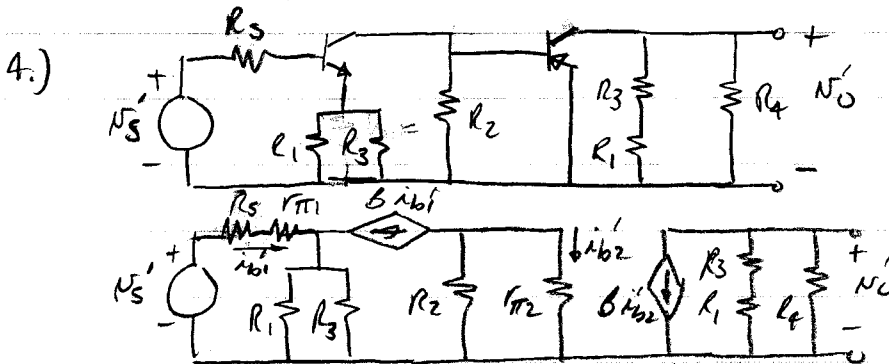

$$A = \frac{N'_o}{N'_s} = \left( \frac{N'_o}{i_{b2}} \right) \left( \frac{i_{b2}}{i_{b1}} \right) \left( \frac{i_{b1}}{N'_s} \right) = \left[ -\beta R_4 || (R_1 + R_3) \right] \left[ -\beta \frac{R_2}{R_2 + r_{\pi 2}} \right] \left[ \frac{1}{R_s + r_{\pi 1} + (1+\beta) R_1 || R_3} \right]$$

$$A = [-100(5.24K)] \left[ -100 \frac{10}{20} \right] \left[ \frac{1}{102.8K} \right] = +255 \text{ V/V}$$

$$5.) \quad A_F = \frac{N_o}{N_s} = \frac{255}{1 + \left( \frac{1}{11} \right) (255)} = \frac{255}{1 + 23.17} = \underline{\underline{10.54 \text{ V/V}}}$$

$$6.) \quad R_{s+th_{11T}} = R_s + r_{\pi 1} + (1+\beta) R_1 || R_3 = 102.8K$$

$$\therefore R_{INF} = 102.8K (1 + AB) \approx 102.8K (24.17) = \underline{\underline{2.485M\Omega}}$$

$$7.) \quad h_{22T} + G_L = h_{22A} + h_{22F} + G_L = \frac{1}{11K} + \frac{1}{\infty} + \frac{1}{10K} = \frac{1}{5.23K}$$

$$\therefore R_{OUTF} = \frac{5.23K}{1 + AB} = \frac{5.23K}{24.17} = \underline{\underline{216\Omega}}$$