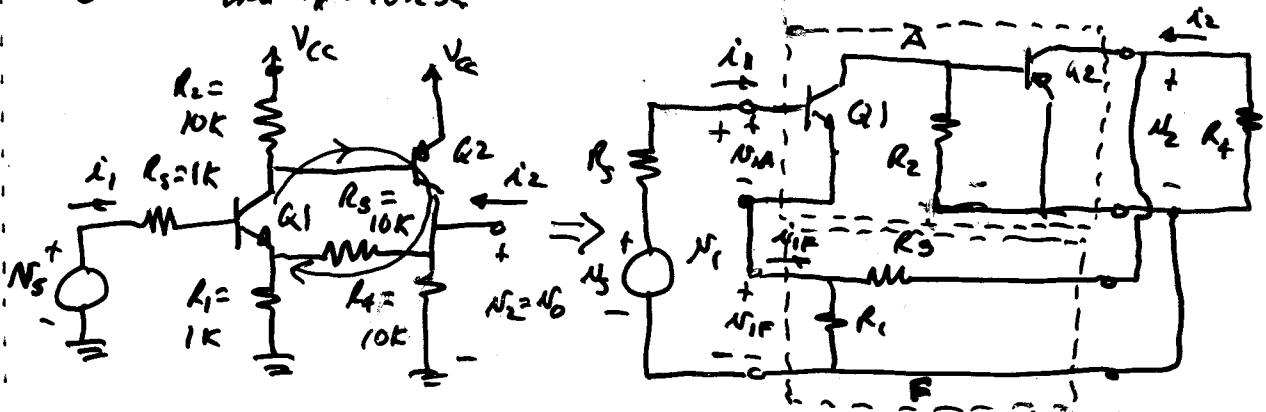


Quiz #10 - High Frequency Response

Vote results: 21 Yes 7 No

Example of Series-Shunt

Find  $\frac{N_o}{N_s}$ ,  $\frac{N_s}{i_i}$ , and  $\frac{N_o}{i_i}$  for the following circuit where  $\beta = 100$  and  $r_F = 10k\Omega$




$$h_{iLT} = h_{iA} + h_{iF} \quad h_{z2T} = h_{z2A} + h_{z2F} \quad h_{iZF} = \left. \frac{N_{iF}}{i_{iF}} \right|_{i_{iF}=0} = \frac{R_1}{R_1 + R_3} = \frac{1}{11}$$

$$h_{iF} = \left. \frac{N_{iF}}{i_{iF}} \right|_{N_2=0} = R_1 \parallel R_3 = 0.91k\Omega$$

$$h_{z2F} = \left. \frac{i_{z2F}}{N_{z2F}} \right|_{i_{iF}=0} = \frac{1}{R_1 + R_3} = \frac{1}{11k}$$


F network:

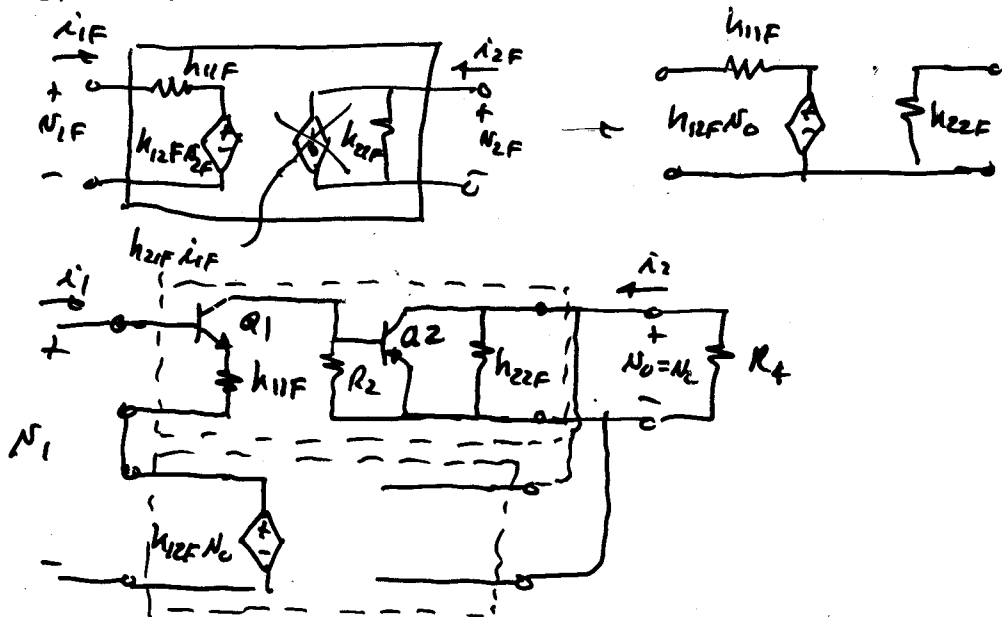


Continuing -

Next find  $A$ , the open-loop amplifier gain ( $h_{22F} = 0$ )

Prime variables  
↓

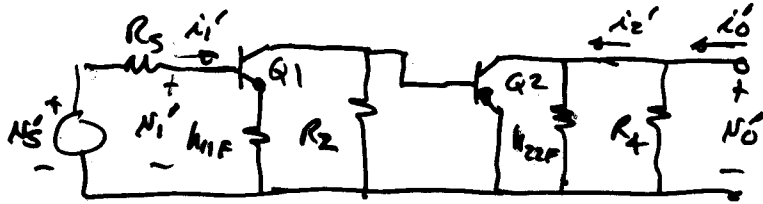

$$A = \frac{N_0'}{N_5'}$$

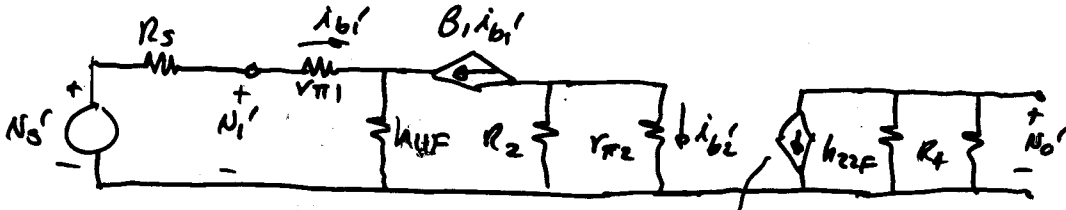

$$\begin{aligned} \frac{N_0'}{N_5'} &= \left(\frac{N_0'}{i_{02}'}\right) \left(\frac{i_{02}'}{i_{b1}'}\right) \left(\frac{i_{b1}'}{N_5'}\right) \\ &= \left(-B_2 R_4 \parallel \frac{1}{h_{22F}}\right) \left(\frac{-B_1 R_2}{r_{\pi 2} + R_2}\right) \left(\frac{1}{R_5 + r_{\pi 1} + (1+B_1)h_{11F}}\right) \\ &= \left(-100 \cdot 10K \parallel 11K\right) \left(\frac{-100 \cdot 10K}{20K}\right) \left(\frac{1}{1K + 10K + (101)(0.91K)}\right) = 1255 \text{ V/V} \end{aligned}$$

$$A_F = \frac{N_0}{N_5} = \frac{A}{1+A} = \frac{1255}{1+1255} = \frac{1255}{1256} = 0.9952 \text{ V/V}$$

$\frac{N_5}{i_1}$  = Input resistance = ?

$$\frac{N_5'}{i_1'} = R_5 + r_{\pi 1} + (1+B_1)h_{11F} = 102.8K\Omega$$

$$\frac{N_5}{i_1} = \frac{N_5'}{i_1'} (1+A_F) = (R_5 + h_{11F}) \left[ 1 + \frac{-h_{21A} h_{12F}}{(R_5 + h_{11F})(G_L + h_{22F})} \right]$$

Input resistance =  $\frac{N_5}{i_1} = (102.8K\Omega)(1+23.17) = 1.695M\Omega$

Output resistance =  $\frac{N_0}{i_0} = \frac{N_0'/i_0'}{1+A_F} = \frac{2.955M\Omega}{1+23.17}$

$$\frac{N_0'}{i_0'} = \frac{1}{h_{22F} + \frac{1}{R_4}} = 11K \parallel 10K = 5.23K$$

∴ Output resistance =  $\frac{5.23K}{1+23.17} = 216\Omega$

## Generalize the Feedback Analysis of Transistor Feedback Amplifiers

All four forms of fba can be analyzed in exactly the same way as done previously.

Let  $x = h, g, y, \text{ or } z$

- 1.) Find  $N_{11F}$
- 2.) Find  $N_{22F}$
- 3.) Find  $N_{12F} = F$  (B)
- 4.) Find  $A$  (the open-loop amplifier gain) incorporating  $N_{11F}$  and  $N_{22F}$  and the correct  $x_{21}$  variables.

$$5.) A_F = \frac{A}{1+AF}$$

$$6.) R_{inF} = \begin{cases} (R_S + N_{11T})(1+AF) & \text{if series} \\ \frac{1}{(G_S + N_{11T})(1+AF)} & \text{if shunt} \end{cases}$$

$$R_{outF} = \begin{cases} \frac{1}{(G_L + N_{22T})(1+AF)} & \text{if shunt} \\ (R_L + N_{22T})(1+AF) & \text{if series} \end{cases}$$

Feedback Topology	Two-Port Parameters
Shunt-shunt (Transresistance amplifier)	$i_1 = y_{11} v_1 + y_{12} v_2$ $i_2 = y_{21} v_1 + y_{22} v_2$
Shunt-series (Current amplifier)	$i_1 = g_{11} i_1 + g_{12} i_2$ $v_2 = g_{21} v_1 + g_{22} i_2$
Series-series (Transconductance amplifier)	$v_1 = z_{11} i_1 + z_{12} i_2$ $v_2 = z_{21} i_1 + z_{22} i_2$
Series-shunt (Voltage Amplifier)	$v_1 = h_{11} i_1 + h_{12} v_2$ $i_2 = h_{22} i_1 + h_{22} v_2$