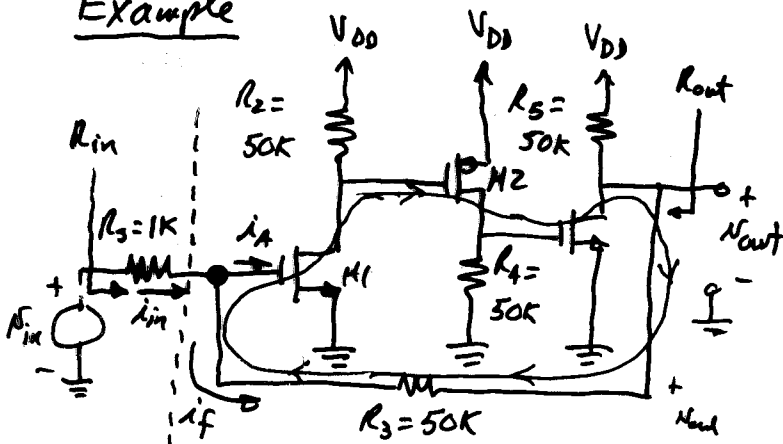


Shunt-Shunt Feedback (Transresistance Amplifiers)

- 1.) Find $y_{i1F} = \left. \frac{i_{1F}}{v_{1F}} \right|_{N_{2F}=0}$ (input conductance of fb. ntwk. w. output SC)
- 2.) Find $y_{o2F} = \left. \frac{i_{2F}}{v_{2F}} \right|_{N_{1F}=0}$ (output conductance of fb. ntwk. w. input SC)
- 3.) Find $y_{12F} = \left. \frac{i_{1F}}{v_{2F}} \right|_{N_{1F}=0}$ (transconductance of the fb. ntwk. from output to input w. input SC)
- 4.) Find A (units of Ω)


Etc.

Example



Find $\frac{v_{out}}{i_{in}}$, R_{in} & R_{out}
 if $g_{m1} = g_{m2} = g_{m3} = 0.2 \text{ mS}$
 and $r_{ds} = \infty$.

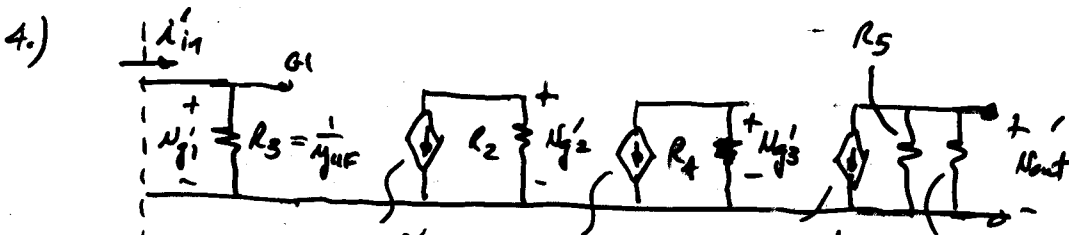1.) $y_{i1F} = \frac{1}{R_3} = \frac{1}{50k}$ 2.) $y_{o2F} = \frac{1}{R_3} = \frac{1}{50k}$ 3.) $y_{12F} = \frac{-1}{50k} = F$



$$A = \frac{v_{out}}{i_{in}} = \left(\frac{v_{out}}{i_{g3}} \right) \left(\frac{i_{g3}}{v_{g2}} \right) \left(\frac{v_{g2}}{i_{g1}} \right) \left(\frac{i_{g1}}{i_{in}} \right)$$

$$A = (-g_{m3} R_3 // R_5) (-g_{m2} R_4) (-g_{m1} R_3) = -25 \text{ M}\Omega$$


AF is ALWAYS positive

Continuing -

$$A_F = \frac{V_{out}}{i_{in}} = \frac{A}{1+A_F} = \frac{-25M\Omega}{1+(-25k\Omega)(\frac{1}{500})} = \frac{-25M\Omega}{1+500} = -49.9k\Omega$$

$$R_{inF} = \frac{R_{in}}{1+A_F} = \frac{R_3}{501} = 99.8\Omega$$
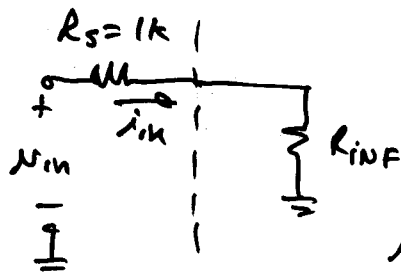
$$R_{outF} = \frac{R_{out}}{1+A_F} = \frac{R_3 \parallel R_5}{501} = \underline{\underline{49.9\Omega}}$$



$$\frac{V_{in}}{i_{in}} = \underline{\underline{R_s + R_{inF} = 1099.8\Omega}}$$

$$\frac{i_{in}}{V_{in}} A_F = \frac{V_{out}}{i_{in}} \times \left(\frac{i_{in}}{V_{in}} \right) = \frac{V_{out}}{V_{in}} = \frac{A_F}{R_s + R_{inF}}$$

$$= \underline{\underline{-455 \frac{V}{V}}}$$

Download the 2 page handout on comparing the 2 approaches to solving the shunt input feedback problem.