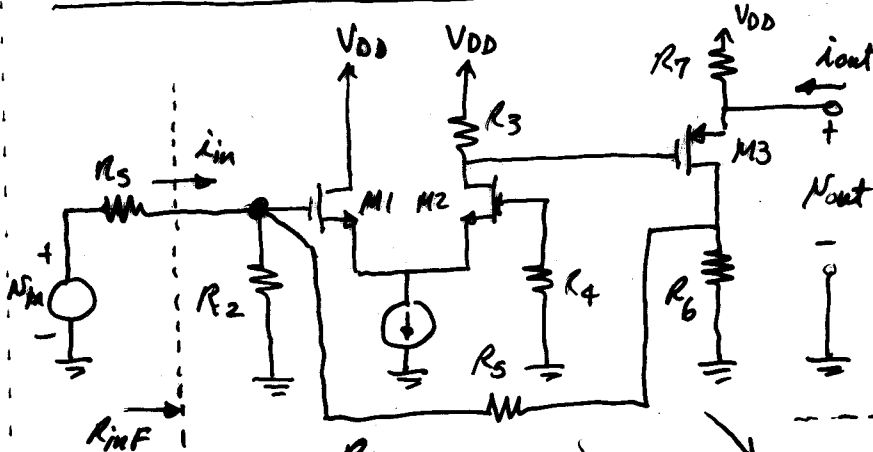



Shunt-Series Feedback Example - Cont'd

Quiz 11 shunt series feedback



$$R_{inF} = \frac{R_{in}}{1+AF}$$
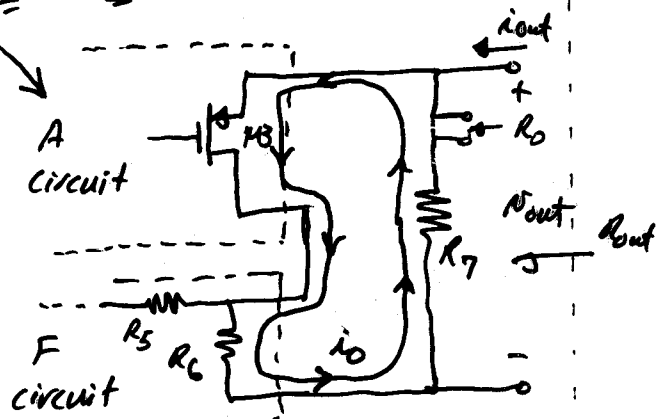
$$\frac{N_{in}}{R_{in}} = R_5 + R_{inF} = 1301 \Omega$$



What is the output resistance of a series output fb. amplifier? (Note: The example wants N_{out}/i_{out} .)

R_0 is the resistance that the fb formulas apply to:


R_0 = resistance in series with the output loop with the fb. loop open.

$$R_{oF} = R_0 (1+AF)$$

R_{oF} = " R_0 " when the fb. loop is closed.

The example requires $R_{out} = \frac{N_{out}}{i_{out}}$


Output SS model:

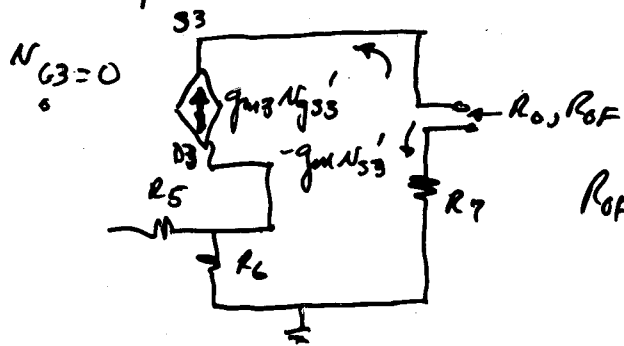


$$R_0 = \frac{1}{g_{m3}} + R_7$$

$$R_0 = 1.1 \text{ K}$$
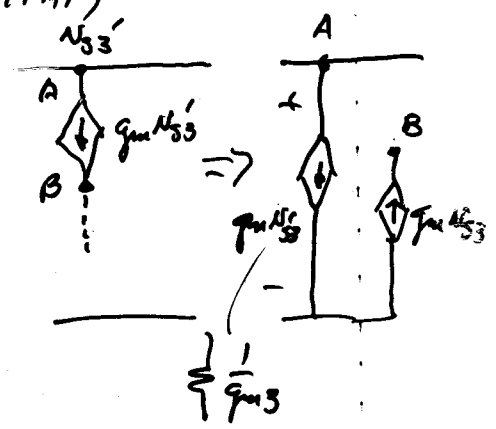
$$R_{oF} = R_0 (1+AF) = 1.1 (3.164) \text{ K} = 3.45 \text{ K} \Omega$$



How do you get R_{out} from all this?

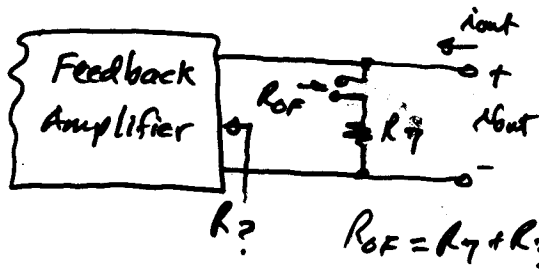

$$R_{out} = \frac{v_{out}}{i_{out}} = R_L \parallel (R_{OF} - R_7)$$

$$R_{OF} = R_7 + R_? \Rightarrow R_? = R_{OF} - R_7$$

$$R_{out} = R_L \parallel (R_{OF} - R_7) = 100 \Omega \parallel (3950 - 100) = \underline{\underline{97.92 \Omega}}$$

A simpler Approach to fb amplifier analysis

1.) Find A_{12F}

2.) Find A by the following:

At the input:

~~The~~ The loading of the fb. network on the amplifier is found by looking in the fb. network and shorting the output (output shunt) or opening the output (output is series).


At output:

The loading of the fb. network on the amplifier is found by looking back into the fb. network with the input s.c. (short input) or a.c. (series input)

Series-Series - Transconductance Amplifier

$$Z_{i2F} = \frac{N_1 F}{i_{2F}} \Big|_{i_1 = i_2 = 0} \quad A \left(\frac{A}{V} \right)$$


Example

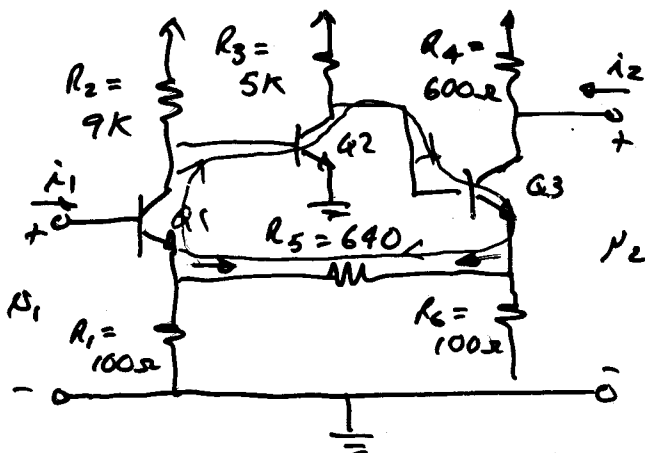

If $\beta = h_{fe} = 100$ and $I_{C1} = 0.6mA$, $I_{C2} = 1mA$ and $I_{C3} = 4mA$, find $\frac{N_2}{N_1}$, $\frac{N_1}{i_1}$, and $\frac{N_2}{i_2}$ using fb. analysis methods.

$r_{\pi 1} = 4.16K, r_{\pi 2} = 2.5K, r_{\pi 3} = 625\Omega$


Open-loop -

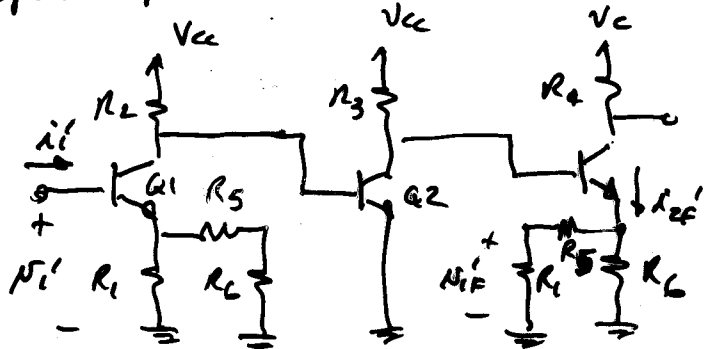

$$F = \frac{N_1 F'}{i_{2F}'}$$

$$N_1 F' = \frac{R_6}{R_1 + R_5 + R_6} \cdot R_1 \cdot i_{2F}'$$
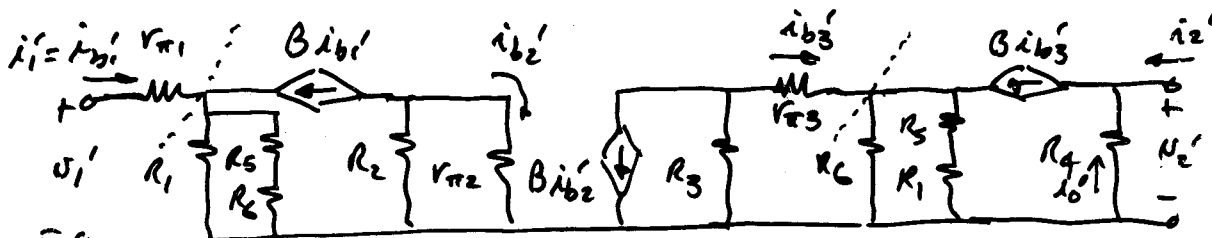
$$F = \frac{R_6 R_1}{R_1 + R_5 + R_6} = 11.9\Omega$$



$$A = \frac{i_o2'}{N_1 i_i'} = \left(\frac{i_o2'}{i_b3'} \right) \left(\frac{i_b3'}{i_b2'} \right) \left(\frac{i_b2'}{i_i'} \right) \left(\frac{i_i'}{N_1 i_i'} \right) =$$

$$= (\beta) \left(\frac{-\beta R_3}{R_3 + r_{\pi 3} + (1+\beta)[R_6 || (R_1 + R_5)]} \right) \left(\frac{-\beta R_2}{R_2 + r_{\pi 2}} \right) \left(\frac{1}{r_{\pi 1} + (1+\beta)[R_1 || (R_5 + R_6)]} \right)$$

$$= (100) (-3443) (-783) \left(\frac{1}{12.97K} \right) = 20.78 \frac{A}{V}$$

$$\frac{\lambda_o}{N_1} = A_F = \frac{A}{1+AF} = \frac{20.78}{1+(20.78)(169)} = \frac{20.78}{1+2472} = 0.00837 \text{ V/V}$$

$$\frac{N_1}{\lambda_i} = R_{inF} = R_{in}(1+AF) = 12.97\text{k}(1+2472) = \underline{\underline{3.22\text{M}\Omega}}$$

$$\frac{N_2}{N_1} = \left(\frac{\lambda_o}{N_1}\right) \left(\frac{N_2}{\lambda_o}\right) = -\frac{\lambda_o}{N_1} R_f = \underline{\underline{-50.2 \text{ V/V}}}$$

$$\frac{N_2}{\lambda_2} = R_f = 600\Omega \quad ???$$

R_f is not in the fb. loop so it is not influenced by feedback.