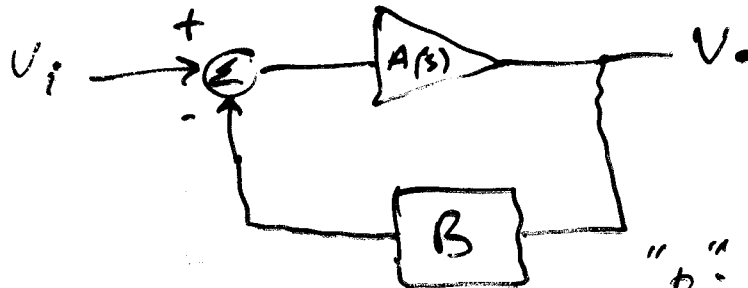


FEEDBACK APPLICATIONS

- USING FEEDBACK TO CONTROL FREQUENCY RESPONSE

Let us determine the influence of negative feedback on the Amplifier frequency response.



"B" is not a function of frequency

$$A(s) = \frac{A_0 \omega_H \cdot s}{(s + \omega_L)(s + \omega_H)} \quad \because \omega_L \ll \omega_H$$

① LOW FREQUENCY ($\omega \ll \omega_H$)

$$A(s) = \frac{s \cdot A_0}{(s + \omega_L)} \quad A_F(s) = \frac{A}{1 + AB}$$

$$\Rightarrow A_F(s) = \frac{s A_0 / (s + \omega_L)}{1 + s A_0 B / (s + \omega_L)}$$

$$A_F(s) = \left(\frac{A_0}{1+A_0B} \right) \left[\frac{s}{s + \frac{\omega_L}{1+A_0B}} \right]$$

$$\omega_{LF} = \frac{\omega_L}{1+A_0B}$$

2) HIGH FREQUENCY ($\omega \gg \omega_L$)


$$A(s) = \frac{A_0 \omega_H}{s + \omega_H} \quad \therefore A_F(s) = \frac{A}{1+A_0B}$$

$$\Rightarrow A_F(s) = \frac{A_0 \omega_H / (s + \omega_H)}{1 + A_0B \omega_H / (s + \omega_H)}$$

$$A_F(s) = \left(\frac{A_0}{1+A_0B} \right) \cdot \left[\frac{\omega_H (1+A_0B)}{s + \omega_H (1+A_0B)} \right]$$

$$\omega_{HF} = \omega_H (1+A_0B)$$

FREQ. RESPONSE (APPLICATIONS) CONT.

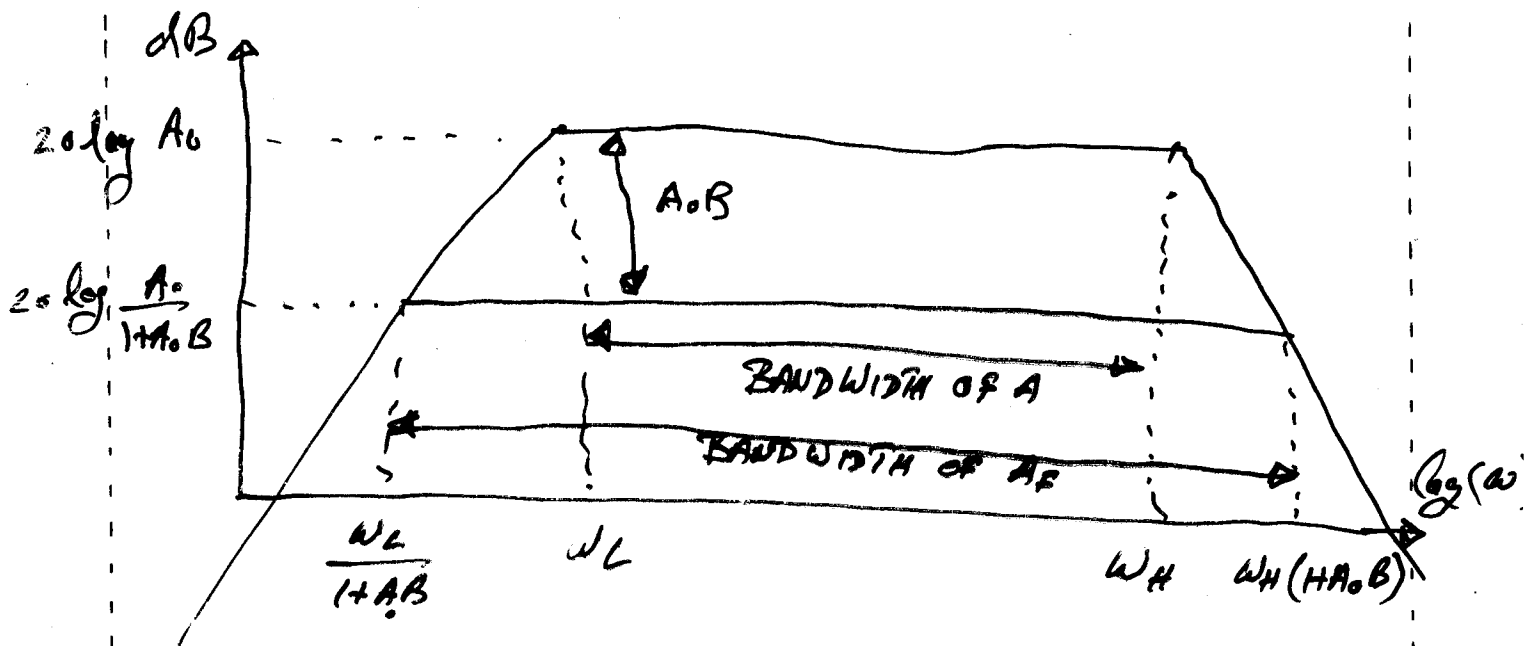

NOTE: TRADEOFF OF BANDWIDTH ∇
GAIN

CALCULATION OF THE LOOP GAIN

Why do we need loop gain?

- 1) Can estimate the influence of negative feedback on K_{in} & R_{out}

$$\text{Sumit: } R_{in} = \frac{R_{in}}{1 + \text{Loop Gain}}$$

$$R_{out} = \frac{R_{out}}{1 + \text{Loop Gain}}$$

$$\text{SERIES: } R_{if} : R_{in} (1 + \text{LOOP GAIN})$$

$$R_{of} : R_{out} (1 + \text{LOOP GAIN})$$

2) To find the stability of "-ve" F.B.

There are two Methods to
Calculate the LOOP GAIN :

i) DIRECT METHOD

ii) SUCCESSIVE VOLTAGE & CURRENT
INJECTION METHOD