

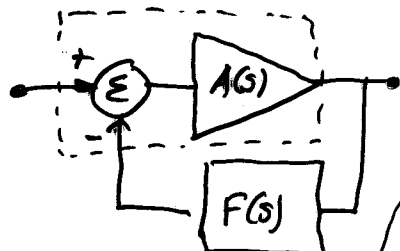
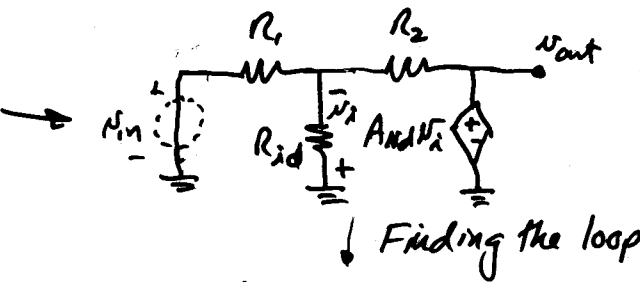


Stability of a feedback network -

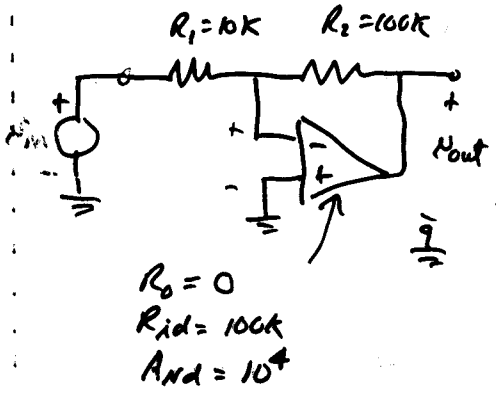

Loop gain = $-A(s)F(s)$
 $= -A(j\omega)F(j\omega)$

Find the loop gain -

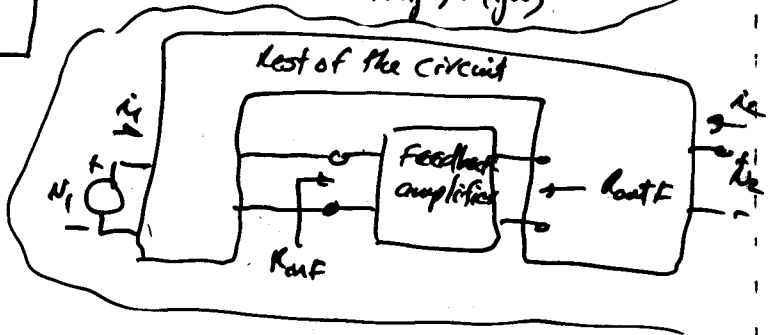

Loop gain = $T = -\frac{N_r}{N_i} = -\frac{N_r'}{N_i'}$


$N_r = -A_{md} N_i \left(\frac{R_{id} || R_1}{R_2 + R_{id} || R_1} \right)$ $\rightarrow T = -\frac{N_r}{N_i} = \frac{10^4 (100K || 10K)}{100K + (100K || 10K)}$

T = 83.33


Stability of Feedback Amplifiers

$A_f(s) = \frac{A(s)}{1+A(s)F(s)} = \frac{A(s)}{1+T(s)} = \frac{A(s)}{1+LG(s)}$


1.) Nyquist Plot

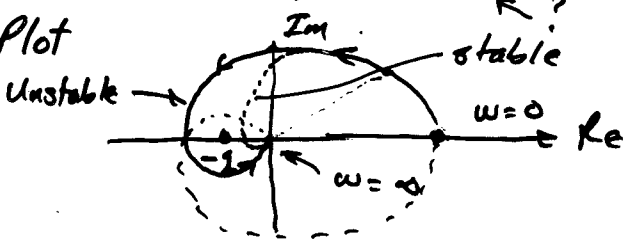

2.) Bode Plot

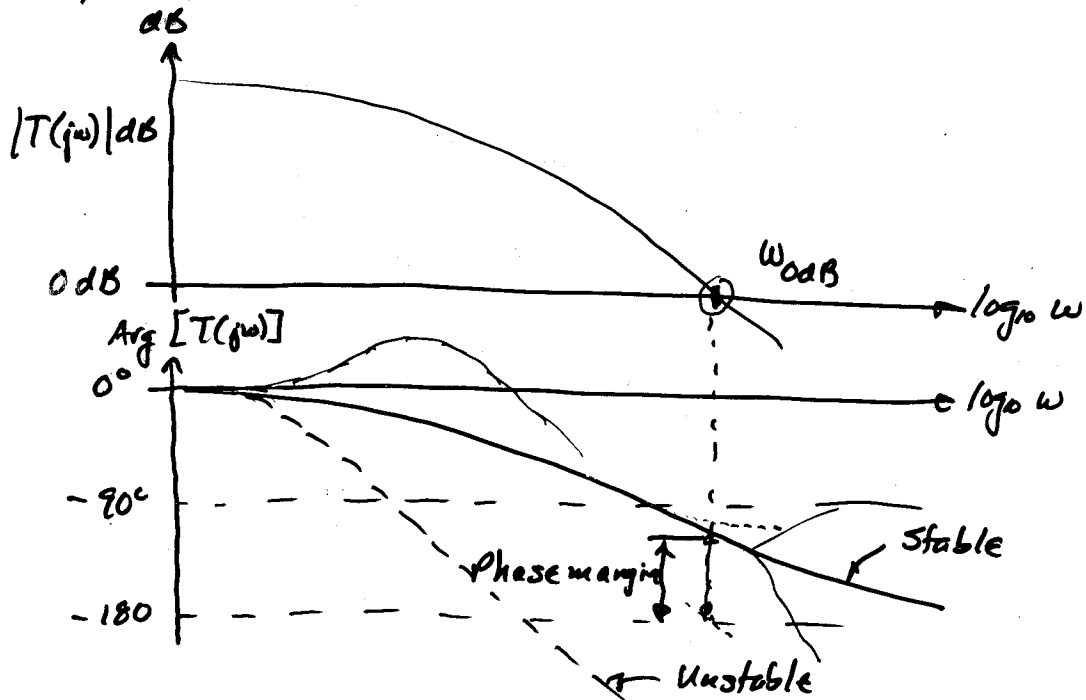
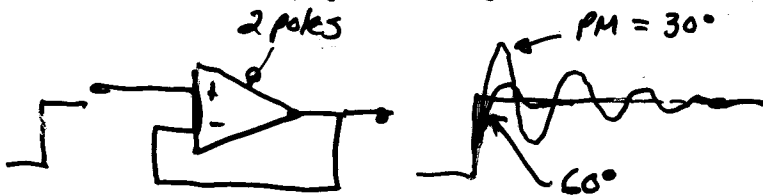
$$\text{Phase margin} = \text{Arg}[T(j\omega_{0dB})] + 180^\circ$$




Example -

$$\text{Assume } A(s) = \frac{1000}{\left(\frac{s}{100} + 1\right)\left(\frac{s}{10} + 1\right)} \quad \& B(s) = 1$$

Find the phase margin.

Next page



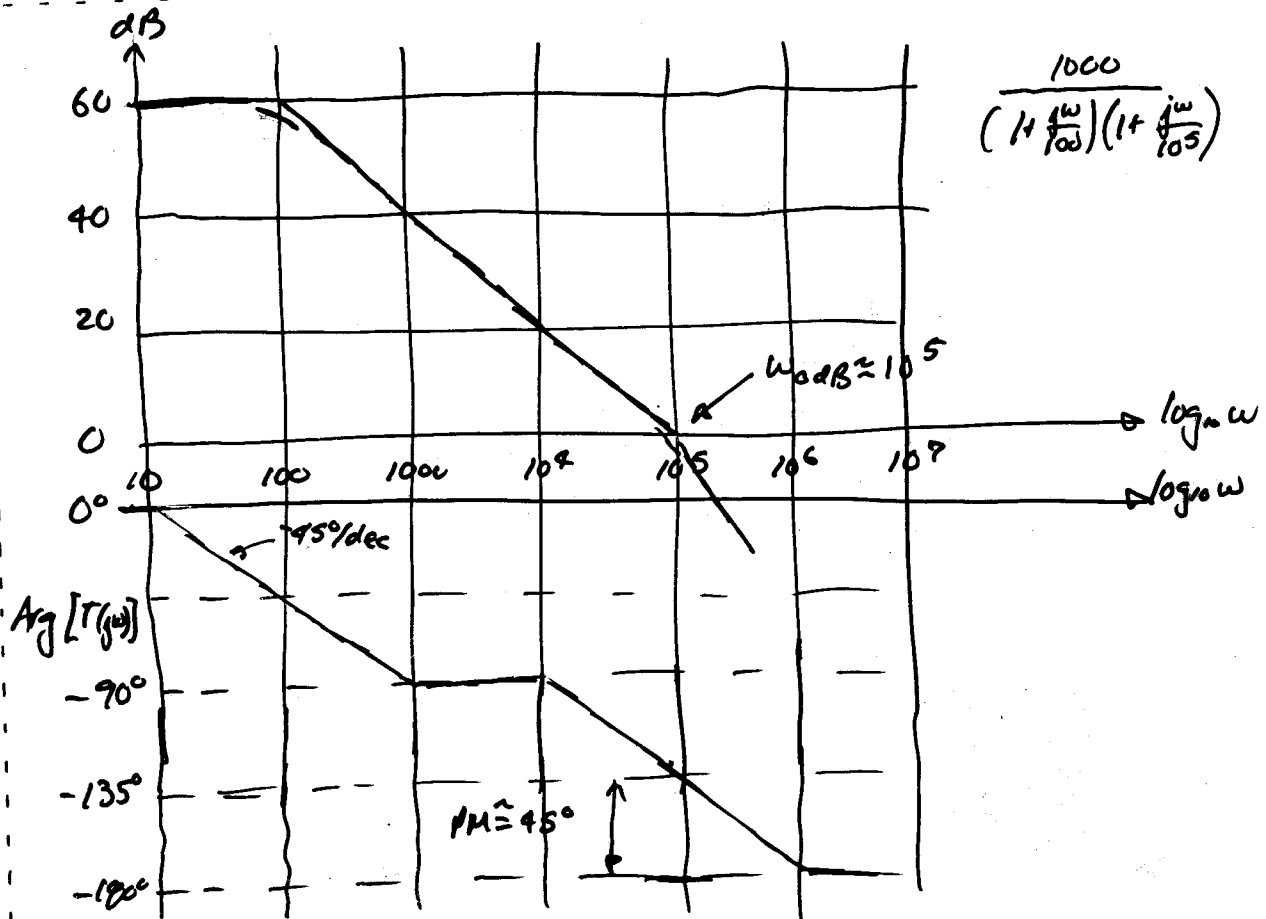

Summary of Feedback Stability (After lecture)

A feedback amplifier is stable if -

a.) $\text{Arg}[T(j\omega_{dB})] > -180^\circ$ i.e. the loop phase shift is more positive than -180° when the loop magnitude is unity

b.) $|T(j\omega_{-180^\circ})| < 1$ i.e. The magnitude of the loop gain is less than unity at the frequency where the loop phase shift is -180° .